

101 SHORT WAVE HOOK=UPS

By the Editors of "SHORT WAVE CRAFT"

Including —

Battery and A.C. Type Receivers

Regenerative Sets

Superheterodynes

Super-Regenerators

T.R.F. Receivers

Everything from 1 to 8 Tube Sets

Published by SHORT WAVE CRAFT

99 Hudson Street, New York City

1935

PREFACE

● This book has been prepared in response to many requests for a compilation of short-wave circuit diagrams which have appeared in SHORT WAVE CRAFT magazine during the past few years. Wherever possible, complete parts lists have been given with the diagrams and, in some cases photographs of the equipment are also included. Further, where it was deemed advisable, due to peculiarities in the construction of the receivers, additional data on special points of construction have been included. Coil-winding data has also been included for most of the sets.

For the convenience of the reader of this book, we have arranged the sets according to several well-known types, as will be observed by examining the

table of Contents. The so-called, "straight receivers", are either regenerative sets or regenerative sets with R.F. amplification. The other classes are: superheterodynes, super-regenerators, and transmitters. There is also a section devoted to A.C.-D.C. receivers. Under the heading "Miscellaneous" are included several sets which do not fall into the general classifications mentioned above.


On many of the diagrams it will be noticed that there is a shield, stating that this set has been tested and approved by SHORT WAVE CRAFT magazine. This simply means that working models of these sets have been tried out and have proved successful.

—The Editor.

CONTENTS

Straight S-W Receivers		
2-Tube A.C. Band-Spreader	6	A 3-Tube Band-Spreader
A Real 3-Tube Receiver	6	The Tetradyne 5-Tube Set
A 1-Tuber	3	Master Composite—4
Ham-Band "Pee-Wee" 3 Tuber	8	A Dual Regeneration Control Set
2-Tube All-Wave Receiver	8	The "Wyeth All-Wave 6"
The Pentaflex	4	Duo R.F. 4-Tube Receiver
A Good Short-Wave Receiver	7	The "Beginner's Twin" Receiver
The 2-Tube "Old Reliable"	7	An Advanced 5-Tube Receiver
Duo-Amplidyne Receiver	5	The "RGH"—5 Receiver
The "19" Twinplex: 1 Tube Performs as		The Original "Doerle" Set
2	5	Doerle "Signal Gripper 3"
The "Mono-Coil 2"	9	"19" Twinplex
The Constant Band-Spread Twinplex	10	A 4-Tube "Doerle" Set
The 2-Tube Pentaflex: 2 Tubes=4	10	Doerle 3-Tube "Signal Gripper" Electri-
The Pocket-Size Short-Wave Set	11	fied
4000 Mile Reception on 3 Tubes	11	The "Clip-Coil Two" Rolls 'Em In!
A DeLuxe T.R.F. Receiver	12	
A 3-Tube "Dx-er"	12	S-W Superheterodynes
Denton "Stand-By" Electrified	13	This 3-Tube "Super" Has "It"!
An "All-Purpose" Receiver	13	Short-Wave Thrills on 2 Tubes
The Minidyne Works on "Loop"	14	Victor 2-Tube Superheterodyne
The "Pal" 2-Tube Portable	15	A 4-Tube Super-Het
The 2-Tube "Champ": 2 Tubes=3	16	The Denton S-W Plugless Superhetero-
The Triplex 2: It Works Speaker!	16	dyne
2-Tube A.C.-D.C. Short-Wave Master	17	The "Globe Girdler 7"
Picking Up Europe on a Loop	17	The "Rex" Portable Super-Het
New "Stand-By" Receiver	18	A South American 7-Tube Super-Het
The Victor "Easy-Tune" 2-Tube Band-		Mitchell 7-Tube Super-Het
Spreader	19	"Ultra Seven" Portable All-Wave Super-
Modernized Meyers 3-Tube Set	19	Het
A 3-Tube Receiver of Quality	20	
Unitrol Simplifies Band-Spread	20	Super-Regenerative Receivers
The Electrodyne 1-Tube Set	21	The Short-Wave "Megadyne"
2 R. F. Pentode S-W Set	22	An Improved Super-Regenerator
The "RGH"—4 All-Wave	23	"Improved" 5-Meter Super-Regenerator
		The 5-Meter Super-Regenerator
		The "53" 1-Tube Twinplex
		Building a 2-Tube Oscillodyne
		Armstrong "Super" 1-Tuber
		The "Easy-Build" S-W Super-Regenera-
		tor
		A Balanced-Detector Super-Regenerator
		The Short-Wave Superregenode
		A 5-Tube A.C. Oscillodyne Set
		The "Bear Cat—3" 5-Meter Super-Regen-
		erative Receiver
		A 5-Meter Super-Regenerator
		A German S-W Set
		A 4-Tube "5 and 10" Meter Receiver
		With Optional Super-Regenerator
		3 in 1 Monotube Super-Regenerator
		The Regenerative-Oscillodyne
		The Oscillodyne
		5-Meter "Bear-Cat" Receiver
		Auto Tube Receiver
		The A.C. Superregenode
		English Super-Regenerator Four
		A "Symmetrical Input" Super-Regenera-
		tor
		A 2-Volt, 3-Tube "Ham" Set
		A.C.-D.C. Receivers
		The "Overseas" 1-Tube 110-220 Volt
		A.C.-D.C. Receiver
		4-Tube S-W "Space Explorer"
		1-Tube "Baby-Radio" Set
		Miscellaneous
		An A.C. S-W Converter
		A 2-Tube Portable "All-Wave" Receiver
		Transmitters
		5-Meter Transmitter and Receiver
		5-Meter Pigmy Transmitter
		A Medium-Power Transmitter

A 1-Tuber

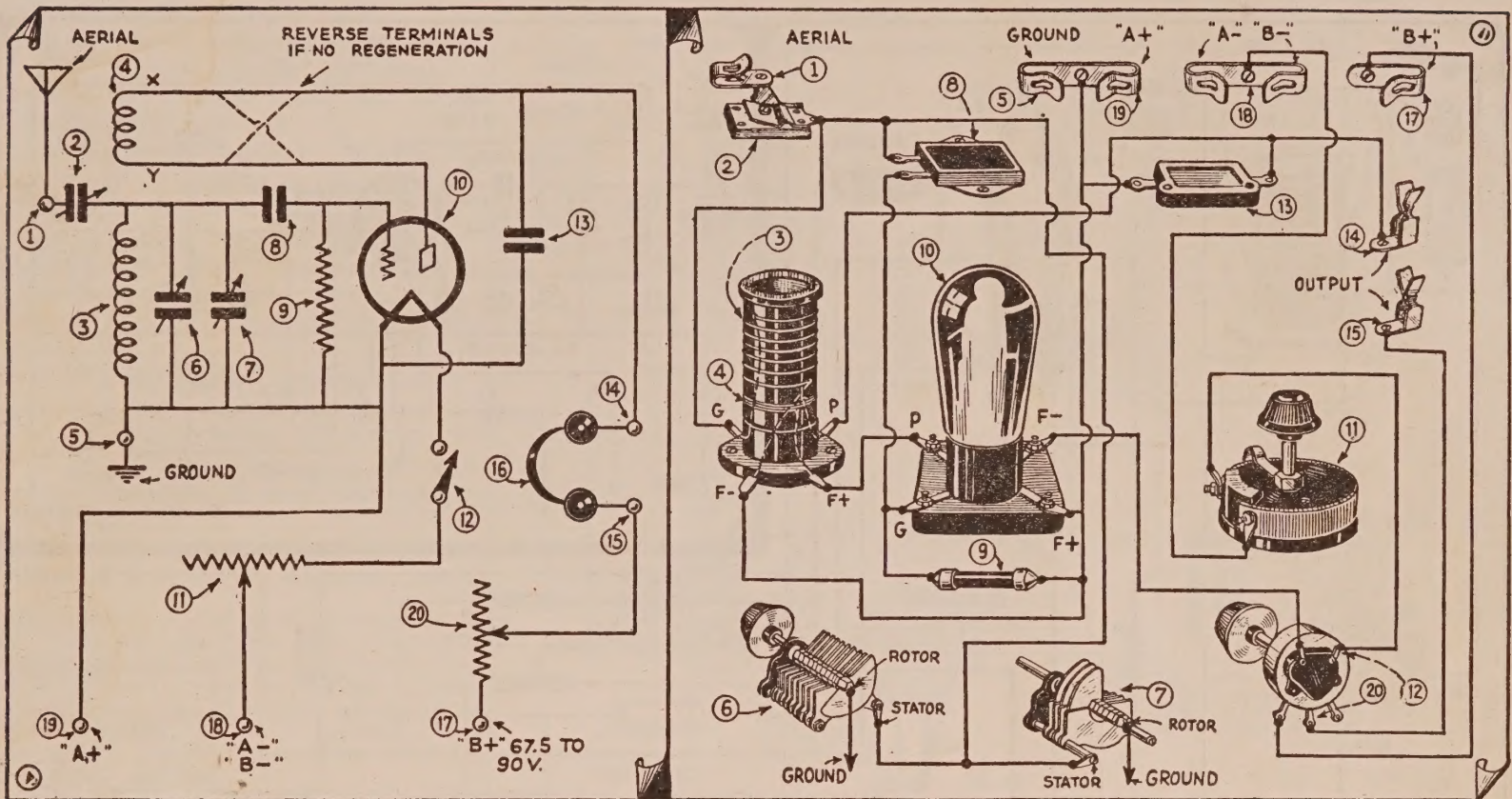

PARTS LIST

- 6—Fahnestock clips (1, 5, 14, 15, 17, 18, 19).
- 1—Pilot 4-prong socket for the plug-in coils.
- 1—Air-gap 4-prong socket for the type 30 detector tube (10).
- 1—Pilot 23-plate midget condenser (6).
- 1—Pilot 7-plate midget condenser (7).
- 1—Flechtheim midget condenser, .00025-mf. (8).
- 1—International Resistance Co. 3-megohm resistor (9).
- 1—Pacent 10-ohm rheostat (11).

- 1—Hammarlund equalizing condenser EC80 (2).
- 1—Alden Mfg. Co. set of short-wave coils (3, 4). 3 is the large winding and 4 is the small winding on all four coils.
- 1—Frost 100,000-ohm potentiometer with power switch (20, 12).
- 1—Aerovox mica condenser, .001 mf. (13).
- 1—Pair of good phones (16).
- 1—Wooden baseboard, 11 x 4½ x ½ inch thick.
- 1—Aluminum front panel, 6 x 11 x 1/16 inch thick. Wood screws solder, soldering lugs, wire, etc.
- 1—Type 30 tube (RCA).

DATA ON ALDEN PLUG-IN COILS

	Number of turns	6 Pitch No. 22 D.S.C.	Primary
(1)	4¾	12 Pitch No. 22 D.S.C.	4 turns No. 31 D.S.C.
(2)	10¾	16 Pitch No. 22 D.S.C.	6 turns No. 31 D.S.C.
(3)	22¾	40 Pitch No. 22 D.S.C.	7 turns No. 31 D.S.C.
(4)	51¾	Close wound No 28 D.S.C.	15 turns No. 31 D.S.C.
(5)	68¾	Bank wound, 2 layers, No. 32	28 turns No. 36 D.S.C.
(6)	131¾	(Optional Litz)	Primary 32 turns No. 36 D.S.C.

WAVE BANDS:

- (1) Blue—10 to 20; (2) Red—20 to 40; (3) Yellow—40 to 80; (4) Green—80 to 200; (5) White—200 to 350; (6) Orange—350 to 550.

D.S.C.—double silk covered. Pitch—turns per inch

—Short Wave Craft, Nov. 1932.

[illegible]

Short Wave Craft, Sept. 1933.

er TICK SEC.


Parts List

- 1—Metal Chassis. Try-Mo Radio.
- 1—set of Plug-in Coils, 15 to 200 meters. Na-Ald (I.C.A.; Bruno; Gen-Win.).
- 1—.00014 mf. Variable Condenser. (Hammarlund; I.C.A.).
- 1—.01 mf. Fixed Condenser. Polymet.
- 1—.1 mf. Fixed Condenser. Polymet
- 1—.0001 mf. Fixed Condenser. Polymet.
- 1—.002 mf. Fixed Condenser. Polymet.
- 2—50,000 ohm 1-watt Resistors. Lynch.
- 2—1-meg. Fixed Resistors. Lynch.
- 1—50,000 ohm Potentiometer, with switch. Acratex.
- 1—10 ohm Rheostat or Amperite 2H-1.
- 1—6-prong Wafer Socket. Na-Ald.
- 1—4-prong Wafer Socket. Na-Ald.
- 1—Antenna Trimmer Condenser (low minimum capacity); 35 mmf. max.); Hammarlund.
- 1—Antenna Ground Terminal Strip. I.C.A.
- 1—Type 19 Tube, R.C.A. Radiotron (Arco.)

The receiver shown is a combination of the Twinplex and the Oscillodyne. It makes use of the type 19 twin tube. One set of elements is used as a super-regenerative detector and the other set as a resistance-coupled audio amplifier. This combination results in a very sensitive "one-tube" receiver.

As for results actually obtained during tests made with this receiver, we can safely say that all of the "foreign" stations can be brought in with good earphone volume, and without any real fussy adjustments to make or hold.

—*Short Wave Craft, June, 1934.*

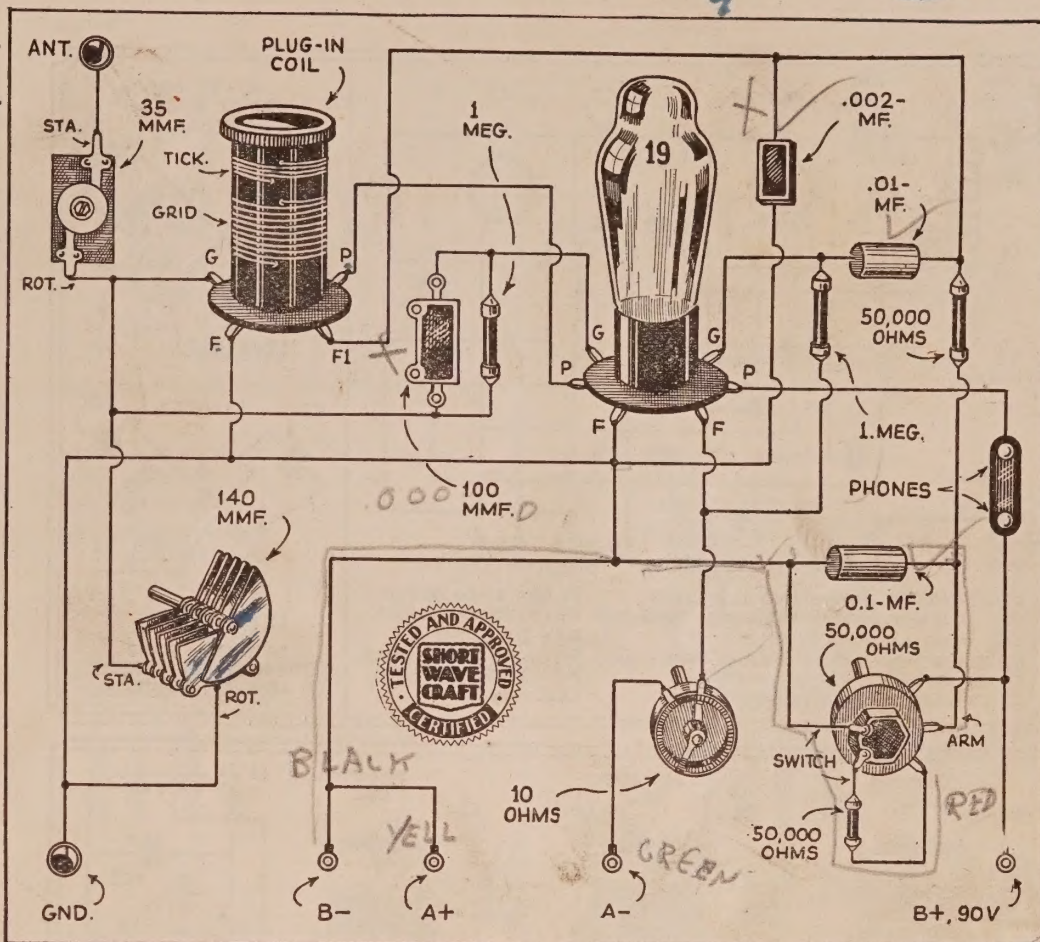


The "19" Twinplex: 1 tube performs as 2


Parts List

- L1, L2—Alden (Na-Ald) Short Wave Coils, 15-200 meters.
- C1—Equalizing condenser 3-35 mmf. EC-35; Hammarlund (National, Cardwell).
- C2—Isolantite midget condenser, 140 mmf. MC-140-M; Hammarlund (National; Cardwell).
- C3—.0001 mf. moulded mica condenser.
- C4, C7—.5 mf. tubular by-pass condenser, 200 DCWV.
- C5—.01 mf. tubular by-pass condenser, 200 DCWV.
- C6—.0005 mf. moulded mica condenser.
- R1—3 meg. metallized resistor; Lynch.
- R2—400 ohm metallized resistor; Lynch.
- R3—20 ohm rheostat (Amperite 2H-1).
- R4—.025 meg. metallized resistor; Lynch.
- R5—100,000 ohm resistor; Lynch.
- R6—50,000 ohm potentiometer; Acratest.
- 1—Aluminum panel, 7"x5"x1/16"; Blan.
- 1—Aluminum subpanel 14 ga., 7"x3 1/4"x1"; Blan.
- 1—3" vernier dial; National.
- 1—4-prong isolantite socket; Hammarlund (National).
- 1—6-prong wafer socket; Alden.
- 1—Ant.-ground binding-post strip.
- 1—Twin speaker jack assembly.
- 1—Type "19" tube RCA (Arco.).


—*Short Wave Craft*, March, 1934.

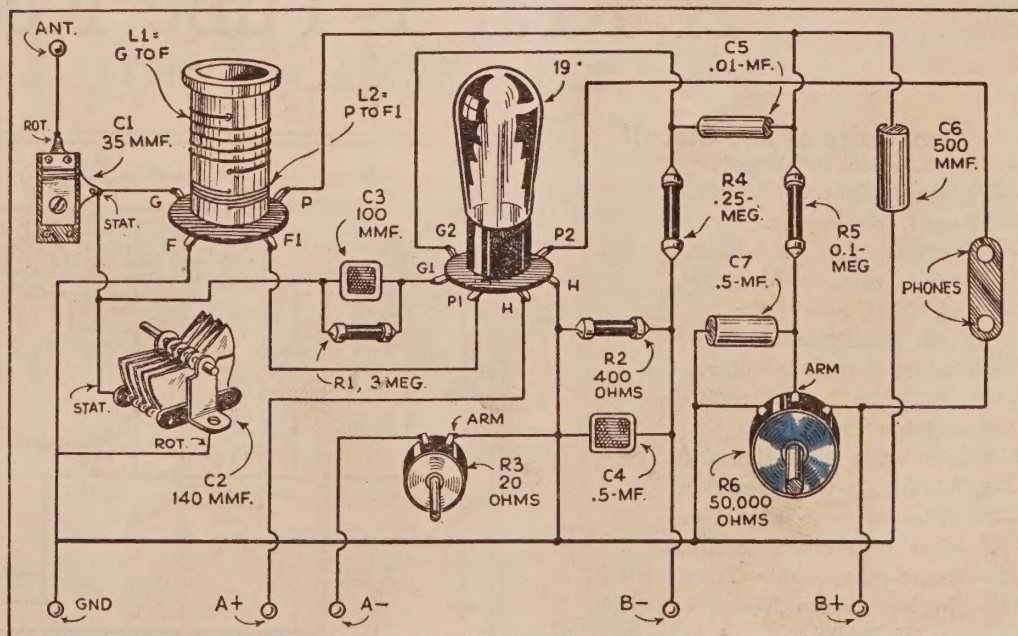

List of Parts

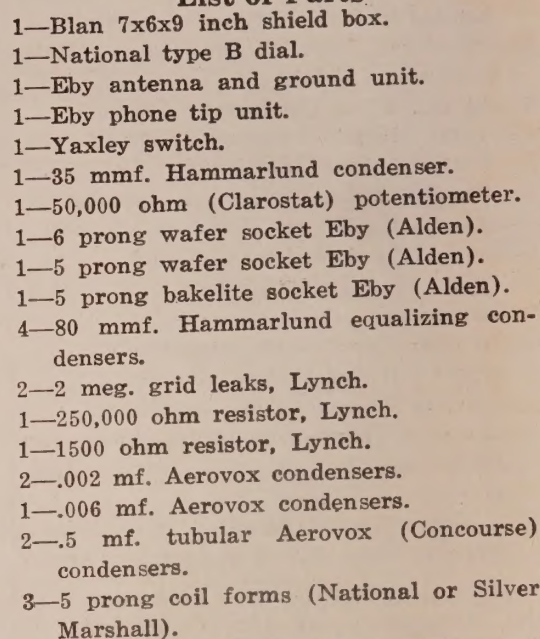

—*Short Wave Craft*, Feb., 1933.

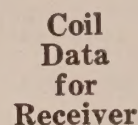

ANTENNA TO USE


The antenna that was found best for this receiver was a long low wire. This type gives considerably less background noise. However, this receiver will pull in "foreign" stations with an antenna only ten feet long and the coupling condenser adjusted closer.

A Real 3-Tube Receiver

Constants of the Circuit

- C—.006-mf. mica condenser.
- C1—3-plate midget condenser.
- C2—50-mm.f. condenser.
- C3—100-mm.f. mica condenser.
- C4—40-mm.f. mica condenser.
- C5—1-mf. fixed condenser.
- C6—.01-mf. fixed condenser.
- R1—500-ohm, 1-watt resistor.
- R2—100,000-ohm 1-watt resistor.
- R3—5-megohm grid leak.
- R4—500,000-ohm potentiometer.
- R5—1,000-ohm, 1-watt resistor.
- R6—50,000-ohm potentiometer.
- R7—30-ohm center tap resistor.
- SW1—Single-pole double-throw switch.
- SV 2—Single-pole single-throw switch.
- L4—Aero Hi-Peak.
- L5—National S-101 coupler.

—*Short Wave Craft*, Oct., 1932.



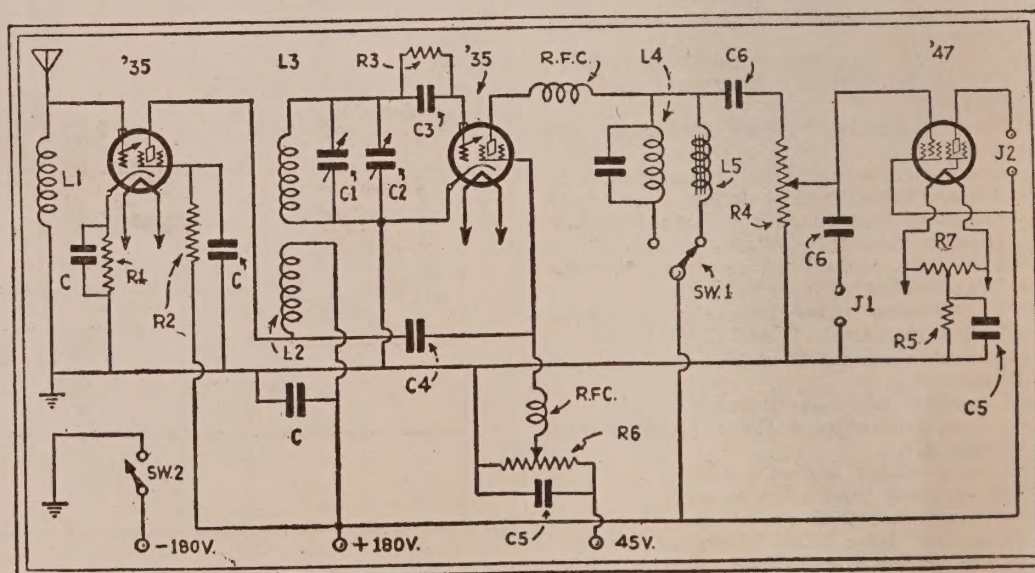


A Good Short-Wave Receiver

List of Parts

- 1—set of 6 prong det. coils.
- 1—set of antenna coils.
- 1—Filament transformer, 2½ inches high, with a 2.5-volt secondary, T3.
- 1—5,000-ohm volume control, R2.
- 1—Frost 100,000-ohm potentiometer, R5.
- 2—Acratest 600-ohm resistors, 1-watt, R1, R9.
- 3—I. R. C. .1-meg. resistors, 1-watt, R3, R4, R6.
- 1—I. R. C. .5-meg resistor, 1-watt, R7.
- 1—20-ohm center-tapped resistor, R8.
- 1—Acratest .006-mf. condenser, C1.
- 1—Acratest .02-mf. condenser, C2.
- 1—Acratest .1-mf. condenser, C3.
- 1—Acratest .1-mf. condenser, C4.
- 1—Micamold .001-mf. condenser, C5.
- 1—Sprague .03-mf. condenser C6.
- 1—Acratest 25-mf. dry electrolytic condenser, C7.
- 1—Hammarlund two-gang "tuning" condenser, type MCD-140M, 140-mmf., C8, C9.
- 2—R.F. chokes, 100 turns No. 38 enameled wire on a spool ¼-inch in diameter and ¼-inch long.
- 1—Special panel and chassis by Blan-the-radio-Man.
- 2—Special tube shields by Blan-the-Radio-Man.
- 1—Eby antenna and ground strip.
- 1—Eby loud speaker strip.
- 2—Eby 6-prong sockets.
- 1—Eby 5-prong socket.
- 1—Eby 4-prong socket.
- 1—Hammarlund 4-prong isolantite socket, type S-4, for T1.
- 1—Hammarlund 6-prong isolantite socket, type S-6, for T2.
- 1—Three-wire cable.
- 1—Power cable with plug.
- 1—National type N, 0-100 vernier dial.
- 1—Best or Magnavox "magnetic" loud speaker.

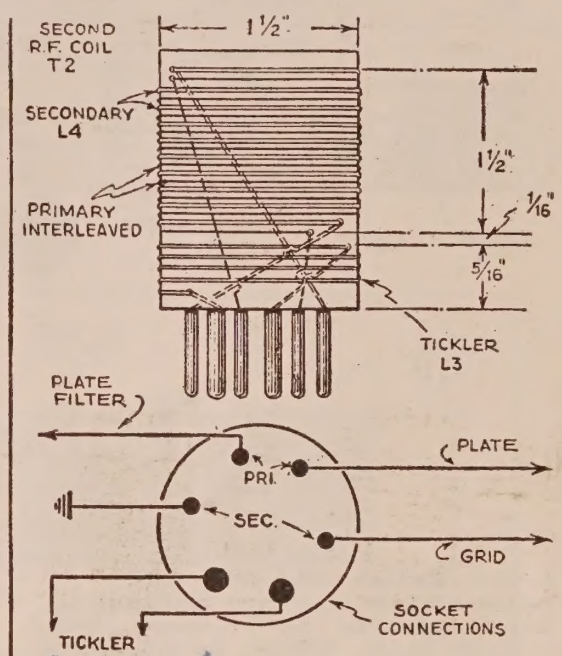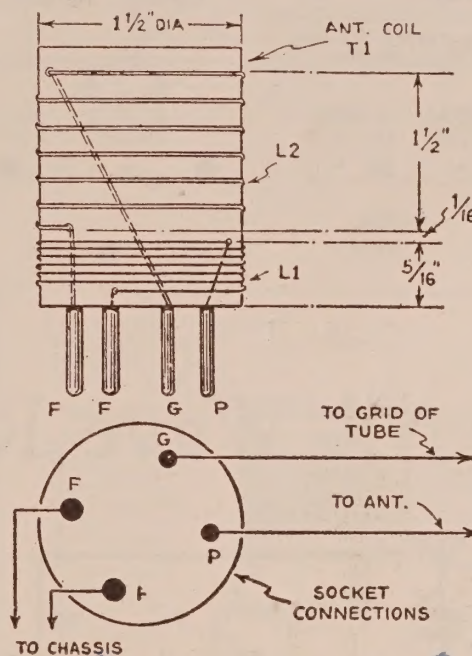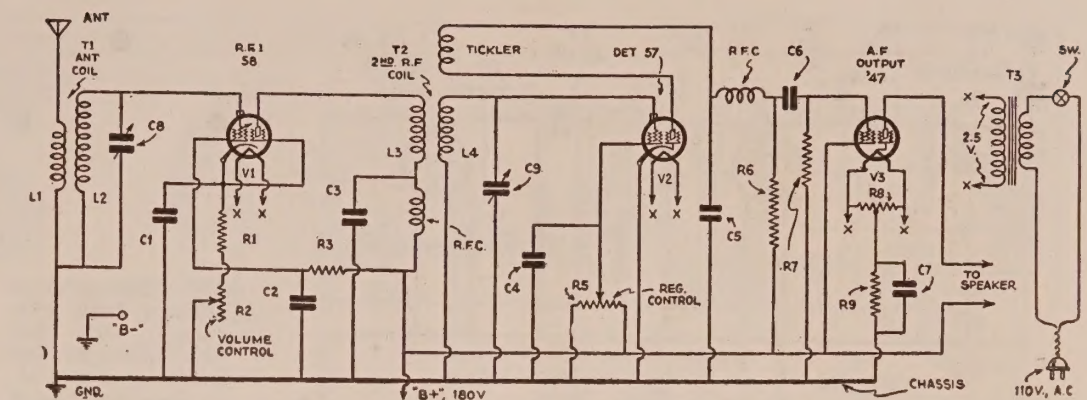A resistor-inductor filter C5 and R.F.C. in the detector plate is very important. The screen-grid lead in this tube also has a resistor-capacitor filter C4, R4, and con-



nects to the regeneration control R5. R4 is in series with shield grid and R5.

An interesting feature of this regeneration control is the fact that as regenera-


tion is advanced or retarded, the tuning of the receiver does not change to an appreciable extent.

—Short Wave Craft, Sept., 1932.

The 2 Tube "Old-Reliable"

List of Parts

- 1—Wearever cooky sheet 12x15½"
- 1—dial, 4 inch.
- 2—knobs.
- 1—filament switch.
- 1—single circuit jack.
- 1—Pilot (Hammarlund) 23 plate midget (Cap. .0001 mf.).
- 1—Pilot (Hammarlund) 7 plate midget (Cap. .000025 mf.).
- 1—tuning condenser 7 plate .00014 mf. (Hammarlund).
- 1—Sub-base transformer Stromberg Carlson 4-1; a 6-1 size will result in more volume.
- 2—wafer sockets (Na-ald).
- 1—Pilot socket (Na-ald).
- 1—Grid condenser .0001 mf. Aerovox (Polymet).
- 1—5 megohm grid-leak Aerovox (Polymet).
- 1—5 megohm grid-leak Aerovox (Lynch).
- 4—fibre washers.

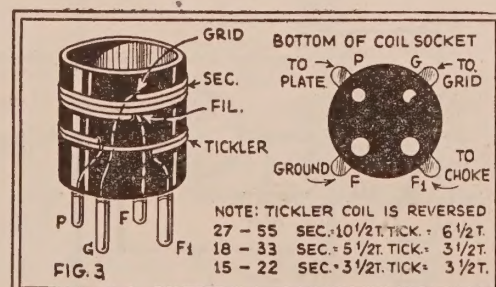

3—tube bases, some No. 18 wire plus hook-up wire.

1½ dozen nickel brass screws (not steel).


1—pair of good phones large size Brandes 2000 ohms.

2—type 30 tubes.

2—"B" batteries 45 volt.

1—"A" battery.



1—Antenna system.

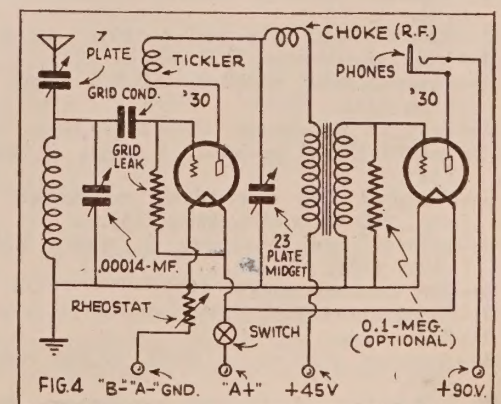

1—ground.
Coil data (see drawing)

—Short Wave Craft, March, 1933.

Ham-Band "Pee-Wee" 3 Tuber

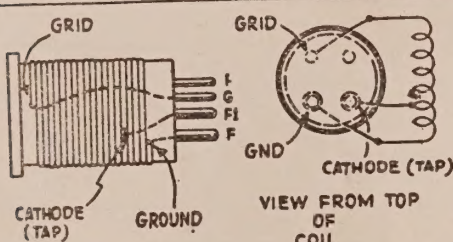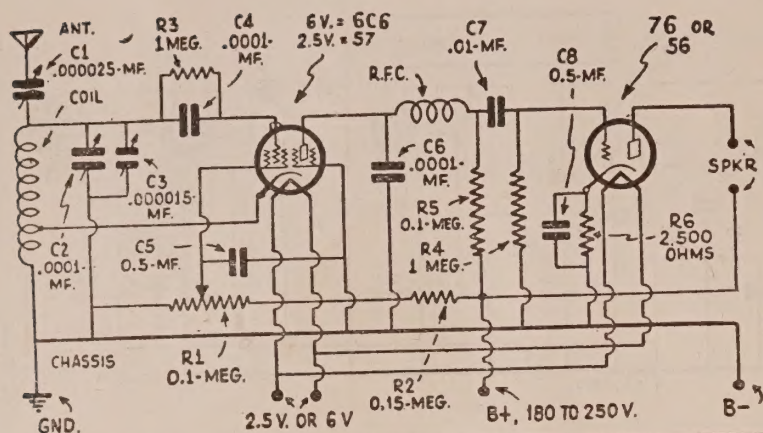

CATHODE TAPPED 1/3 WAY UP FROM GROUND.

20 METERS	5 TURNS
40 "	12 "
80 "	28 "

~ COIL DATA ~

Parts List


- C1-1—.000025 mf. variable midget condenser.
- C2-1—.0001 mf. variable midget condenser.
- C3-1—.000015 mf. variable (cut down 3-plate unit).
- C4, C6—.0001 mf. fixed mica condenser.
- C5, C8—.5 mf.-250 volt bypass (paper).
- C7-1—.01 mf. bypass condenser.
- R1-1—100,000 ohm potentiometer; Acratest.
- R2-1—150,000 ohm, 1 watt carbon resistor, Lynch.
- R3, R4—1 meg., 1 watt carbon resistor.
- R5-1—100,000 ohm, 1 watt carbon resistor.
- R6-1—2500 ohm, 1 watt carbon resistor.
- RFC—Radio frequency choke, 30 to 85 millihenry. Hammarlund or National.
- 1—6-prong socket, Eby (Na-ald, Hammarlund, National).
- 1—5-prong socket, Eby (Na-ald, Hammarlund, National).
- 1—4-prong power supply socket, Eby (Na-ald, Hammarlund, National).

—Short Wave Craft, Nov., 1933.

2-Tube All-Wave Receiver

Parts List


- 1—Eby antenna-ground strip (1, 2).
- 1—Hammarlund equallizing condenser (3).
- 1—set Octo-Coils (4). (Ranges: 16-30, 29-58, 54-105, 100-200, 200-510 meters. See Page 5 "19 Twinplex" set, for coil winding data; the broadcast coil has a secondary of 126 turns of No. 28 enameled wire on a 1 1/2-inch diameter tube. The tickler has 28 turns No. 34 enameled wire.)
- 2—Pilot midget condensers, .00015 mf. each (5A, 5).
- 1—Acratest .5-watt, 3-meg. resistor (6).
- 1—Micamold mica condenser, .00015 mf. (7).
- 1—Acratest resistor, 7,500 ohms, .5 watt (8).
- 1—Acratest resistor, 500,000 ohms, .5 watt (9).
- 1—Eby 6-prong tube socket (10).
- 1—Blan short-wave R.F. choke (11).
- 1—International resistor, 200,000 ohms, 1 watt (12).
- 1—Sprague condenser, .075 mf. (13).
- 1—International resistor, 1 meg., 1 watt (14).
- 1—Acratest dry electrolytic condenser, 1 mf., 200 volts, No. 6662 (15).
- 1—International resistor, 1 watt, 2,500 ohms (16).
- 1—Eby 5-prong socket (17).
- 1—Frost short jack (18).
- 1—Eby phone jack (19).
- 1—Acratest resistor, 5 watt, 25,000 ohms (20).
- 3—Acratest electrolytic condensers, one 4 mf. and two 8 mf., No. 6493 and 6495 (21, 22, 23).
- 2—Acratest chokes, 30-henry, No. 2505 (24, 25).
- 1—Eby 4-prong socket, marked 280 (26).

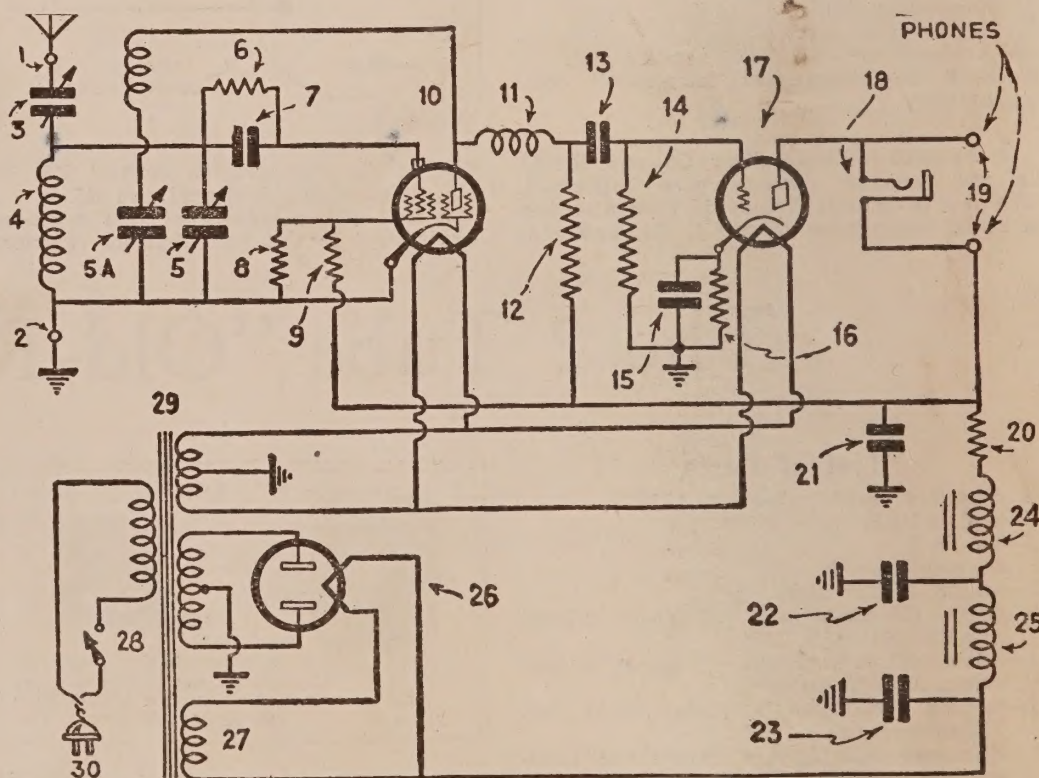

- 1—Acratest power transformer, No. 6027 (27).
- 1—H. & H. filament switch, No. 4122 (28).
- 1—G. E. power cable and plug (30).
- 1—Micamold condenser, .005 mf. (29).
- 1—Blan aluminum chassis, folded and drilled.
- 1—K. K. port dial.
- 1—National screen-grid clip.
- 1—Raytheon '80 tube.
- 1—Raytheon '56 tube.
- 1—Raytheon '57 tube.


—Short Wave Craft, Sept., 1932.

The "Mono-Coil 2"

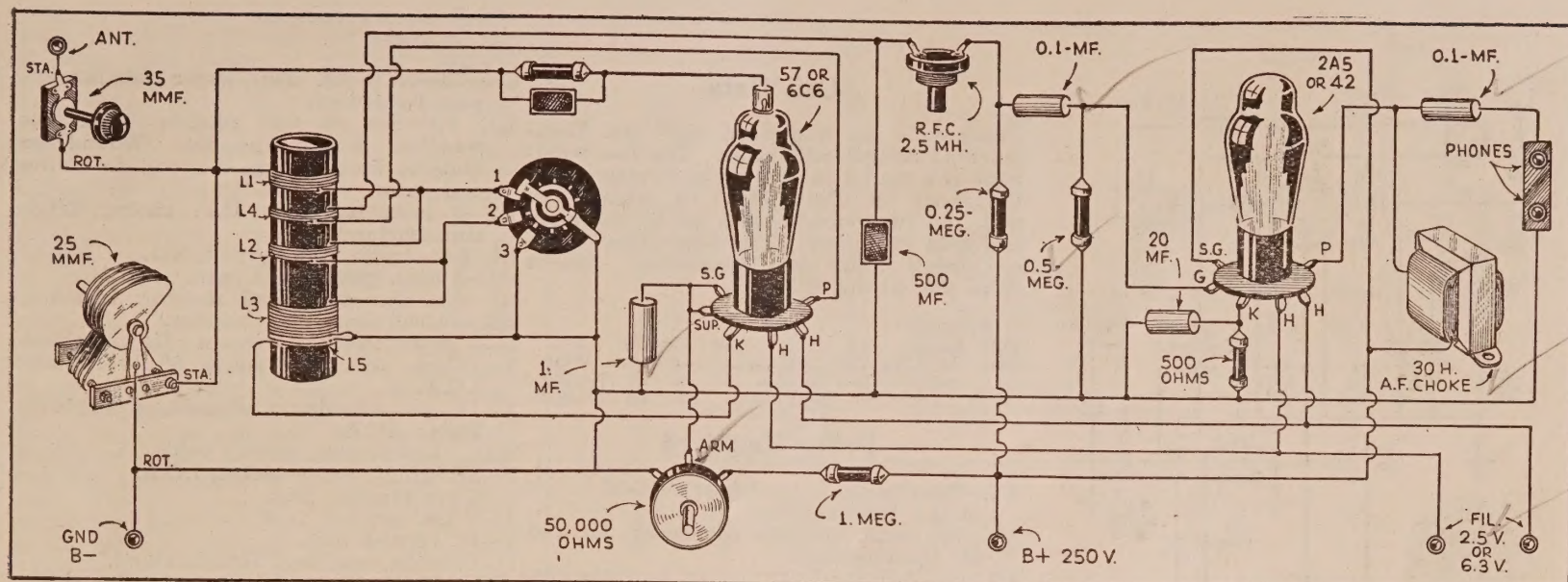

NO MORE PLUG-IN COILS!

The "plug-in" coil has been a sore spot in the realm of short-wave receivers for a long time — at last this great "bugaboo" of pulling out and pushing in short-wave coils has been wiped out by a single stroke of masterly genius — thanks to the extensive researches of George W. Shuart, who here describes the "Mono-Coil," which permits changing of bands even more efficiently than by the use of plug-in coils! Only one very simple single-pole switch is required for changing the bands with the "Mono-Coil".

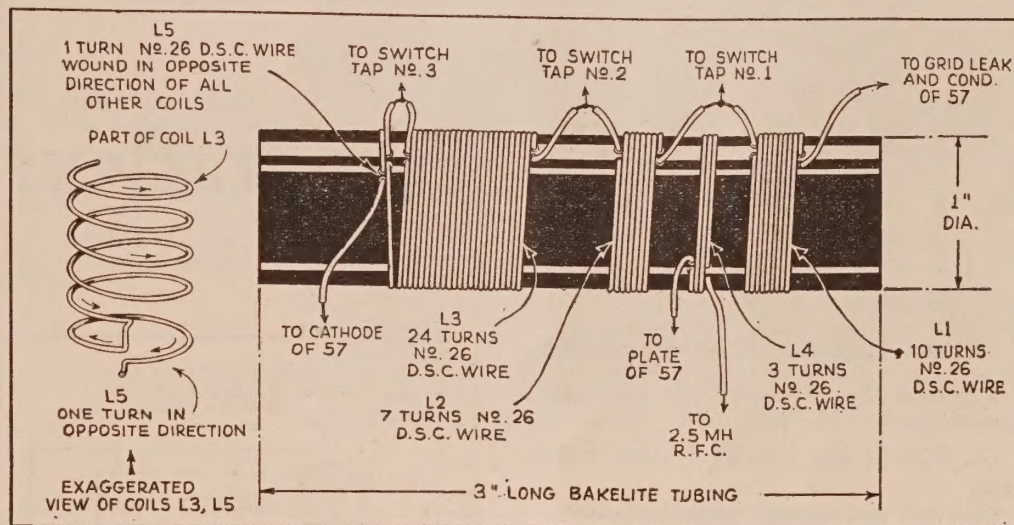

Constructional details of the "Mono-Coil"

Here is a real solution to the problem of "how to eliminate plug-in coils." The "Mono-Coil 2" is a 2-tube receiver which will cost only a nominal amount to build; it covers the short-wave "broadcast" bands, 19-25, 25-38, and the 49 meter channels by merely turning a switch. The benefits of "band-spread" are included! Uses 2.5 Vt. or 6.3 Vt. tubes.

When the switch is set on contact No. 3 the entire grid coil is in use with the three-turn plate tickler and the one-turn cathode coil providing just the proper amount of feed-back when the screen voltage of the tube is set for maximum sensitivity. Set on point No. 2 the switch shorts out L3, the cathode coil now becomes more or less inactive, which is just what we want. The plate coil is then left

to work with L1 and L2. The range of each tap of the coil is of course affected by the adjustment of the antenna condenser but their approximate tuning range is as follows: tap-1, 16 to 28 meters, tap-2, 25 to 38 meters and tap-3, 45 to 55 meters. The drawing clearly shows the construction of the coil and the number of turns. For best results follow the specifications exactly.


List of Parts for "Mono-Coil-2"

- 1—Chassis 5"x8"x1". Blan.
- 1—Panel 7"x9". Blan.
- 1—Mono-Coil—see drawing.
- 1—4 pt. single pole switch. Blan.
- 1—35 mmf. Var. Antenna condenser.
- 1—25 mmf. condenser; tuning 270 degrees. National.
- 1—.0001 mmf. fixed condenser (mica).

- 1—1 mf. (paper).
- 1—.0005 mf. fixed (mica).
- 2—.1 fixed (paper).
- 1—20 mf. 25 volts (electrolytic).
- 1—3 meg. resistor ($\frac{1}{2}$ watt). Lynch.
- 1— $\frac{1}{4}$ meg. ($\frac{1}{2}$ watt). Lynch.
- 1— $\frac{1}{2}$ meg. ($\frac{1}{2}$ watt). Lynch.
- 1—1 meg. ($\frac{1}{2}$ watt). Lynch.
- 1—500 ohms 1 watt.
- 1—50,000 ohm potentiometer Acra-test.
- 1—J30 H. midget choke (iron core).
- 2—6 prong sockets. Na-Ald.
- 1—Antenna ground terminal strip. Na-Ald.
- 1—Phone terminal strip. Na-Ald.
- 1—57 or 6C6 tube. RCA Radiotron. (Ar-co).
- 1—2A5 or 42 tube. RCA Radiotron. (Ar-co).

—Short Wave Craft, Aug., 1934.

The Constant Band Spread Twinplex

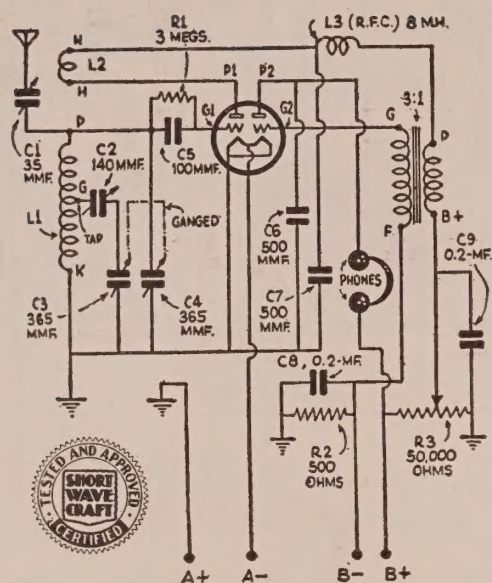

Coil Data

These coils are wound on 1 1/8" dia. Hammarlund Midget coil forms. The two windings are wound in the same direction and separated by about 1/8". In wiring the coil, the two outside leads go to the plate and grid condenser. The disposition of the remaining leads is immediately evident from the wiring diagram.

Coil	Frequency Range	L1	L2
No. 1	6-18 MC.	10 No. 22en	4 12 No. 30dsc
No. 2	1.5-6	27 No. 22dsc	27 18 No. 30dsc

Parts Required

- C1—Equalizing condenser—EC-35 (35 mmf.) Hammarlund.
 C2—140 mmf. variable condenser, MC-140-M. Hammarlund.
 C3, C4—365 mmf. two-gang variable condenser, Tru-test.
 C5—.0001 mf. mica condenser.
 C6, C7—.0005 mf. mica condenser.

C8, C9—.2-.2 mf. dual paper tubular by-pass condenser.

L1, L2—Set of two plug-in coils. See winding details opposite. Wound on Hammarlund Midget 5-prong Isolantite coil forms, CF-5-M.

L3—8 m.h. isolantite R.F. choke, CH-8, Hammarlund.

L4, L5—Audio transformer, 3:1.

R1—3 meg. grid-leak, Lynch.

R2—500 ohm metallized resistor, Lynch.

R3—50,000 ohm potentiometer.

1—5-prong isolantite socket, Hammarlund.

1—14 ga. aluminum panel, 5"x10", Blan; I.C.A.

1—14 ga. aluminum chassis, 6"x12"x1", Blan; I.C.A.

4 ft.—4-conductor battery cable.

1—Six-prong wafer socket, I.C.A.

1—Twin binding post.

1—Twin speaker jack.

1—3" vernier dial.

1—Flexible coupling, Hammarlund.

4 in.—Hard rubber 3/4" dia. extension shaft.

1—R.C.A. "Radiotron" type 19 tube.

—Short Wave Craft, July, 1934.

The 2 Tube Pentaflex: 2 Tubes=4

Parts List—2 Tube Pentaflex

C1, C5—.5 mf. tubular by-pass condensers.

C2, C7—.01 mf. tubular by-pass condensers.

C3—.005 mf. molded mica condenser.

C4—.0001 mf. molded mica condenser.

C6—.0005 mf. molded mica condenser.

C8—Hammarlund midline midget variable condenser—140 mmf.—Type MC-140-M.

L1, L2, L3—One set Alden (Na-Ald) 3 winding 6 prong plug-in short wave coils, 15-200 meters.

R1—10,000 ohm metallized resistor, Lynch (International).

R2—200 ohm wire-wound resistor, Lynch (International).

R3, R4, R7, R9—.25 meg. metallized resistor, Lynch (International).


R5—50,000 ohm resistor, Lynch (International).

R6—3 meg. resistor, Lynch (International).

R8—50,000 ohm Potentiometer (Acra-test).

1—S.P.S.T. switch.

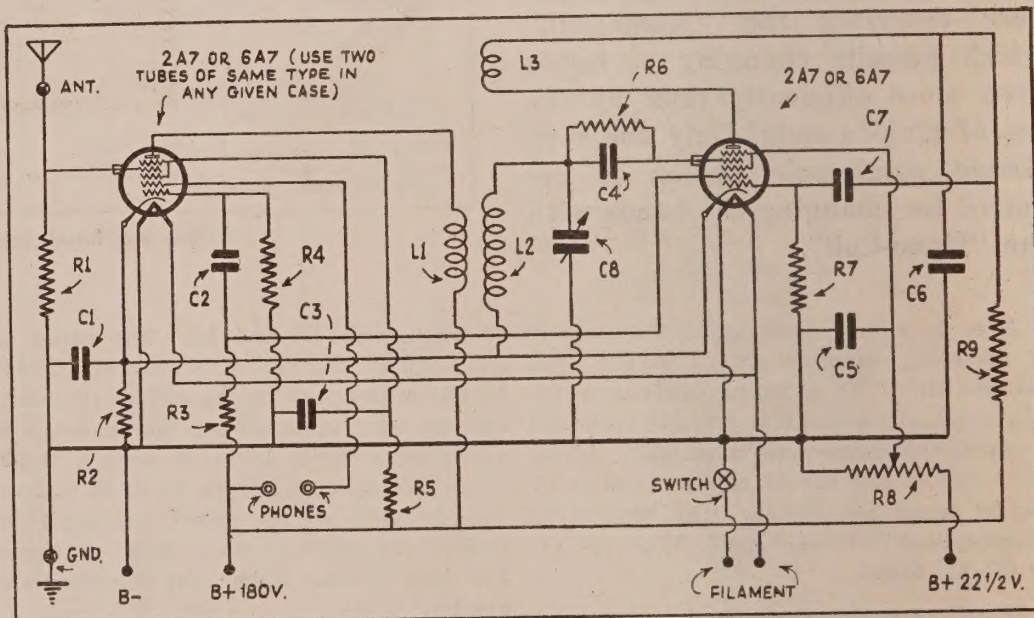2—Eby 7 prong (.75" pin circle diameter) wafer sockets (Alden).



1—National 6 prong Isolantite socket.

1—National Type "BM" Vernier dial.

2—National Grid clips, Type 24.

1—Eby twin binding post strip (Laminated).

1—Eby twin speaker jack assembly (Laminated).

2—ft. battery cable, 5-conductor.

1—Roll hook-up wire.

2—2A7 or 6A7 tubes, Gold Seal, Arco, Van Dyke.


1—Aluminum panel 5" x 7".

1—Aluminum subpanel 7" x 7".

—Short Wave Craft, Nov., 1933.

A Pocket Sized Short-Wave Set

This very cleverly designed pocket short-wave receiver, originally described in the October, 1933 issue of *SHORT WAVE CRAFT* employs but one tube, which may be of the 30 type. This tube may be operated on a flashlight battery or a "C" battery for the filament, while the plate supply of 22½ volts potential may be furnished by flashlight cells, fountain-pen flashlight cells, etc. Instead of using the tuning coil shown, together with book-type tuning condenser, regular standard plug-in coils, data for which will be found elsewhere in this book, may be used in conjunction with a regular rotary variable tuning condenser of the midget type and having a capacity of .00014 mf. Coil data is given below which is useful where a tuning condenser of .0001 mf. or 100 mmf. is to be used. The grid leak for the portable pocket set is of 9 to 10 megohms resistance, and the grid condenser of 250 mmf. capacity. The regeneration control condenser connected between the ground and one of the phone terminals may be a midget 13 plate unit having about 50 mmf. capacity. If the set does not seem to regenerate use a larger condenser and the editor recommends at least a 140 mmf. as the size generally used for this purpose.

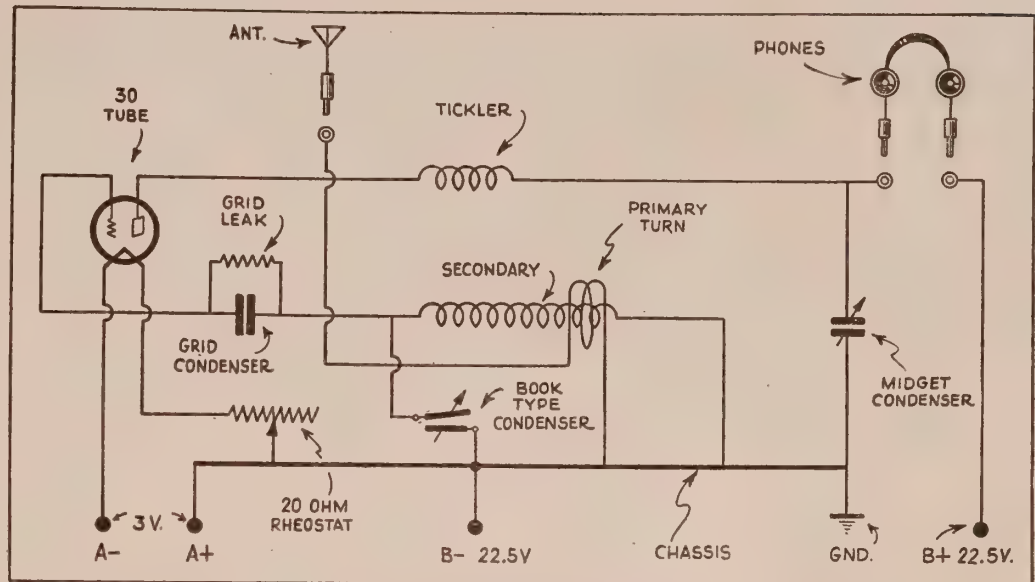

Coil data for .00009 mf. (approximately .0001 mf.)

P.	S.	T.	Wave Length Range in Meters
38T. No. 32	63	T. No. 28	5T. No. 32 200-115 m
22T. No. 34	35	T. No. 24	4T. No. 32 115- 65 m
13T. No. 34	20	T. No. 18	4T. No. 32 70- 40 m
8T. No. 34	12	T. No. 18	3T. No. 32 41- 23 m
4T. No. 34	6½	T. No. 16	3T. No. 32 25-14.5m
2T. No. 34	3	T. No. 16	3T. No. 32 15- 9 m


Dia. form 1½", 6 pin.

T=tickler.

S=secondary or grid coil.

P=primary or antenna coil.

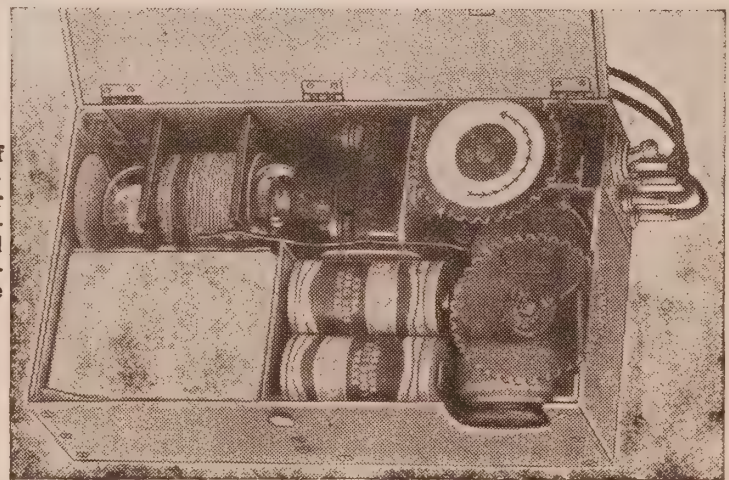Right—A photo of the completed pocket-size receiver showing the interior. Note that all batteries are self-contained in the metal cabinet.




—Short Wave Craft, Oct., 1933.

4000 Mile Reception On 3 Tubes

This fine receiver was constructed by a resident of the Dominican Republic in the West Indies. Using a four-foot wire for an aerial, it pulled in Daventry, England at full loud-speaker strength.


An electron coupled regenerative detector is employed, resulting in excellent stability. All plug-in coils were mounted on the chassis of the receiver and a switching arrangement is employed to change the wavelength. The plug-in coils used were ordinary three-winding 6-pin type coils such as those of the National Company. The detector tuning condenser has a value of 160 mmf. The set is "all-electric." The suppressor grid of the detector, it should be noted, is connected directly to ground, rather than to the cathode of the tube. The impedance, L1, in the plate circuit of the detector tube consists of an audio transformer with the primary and secondary connected in series. The "G" terminal of the secondary of this transformer was connected to the R.F. choke 1, and "P" and "F" were tied together. "F" connects to the plate voltage supply.

—Short Wave Craft, Aug., 1933

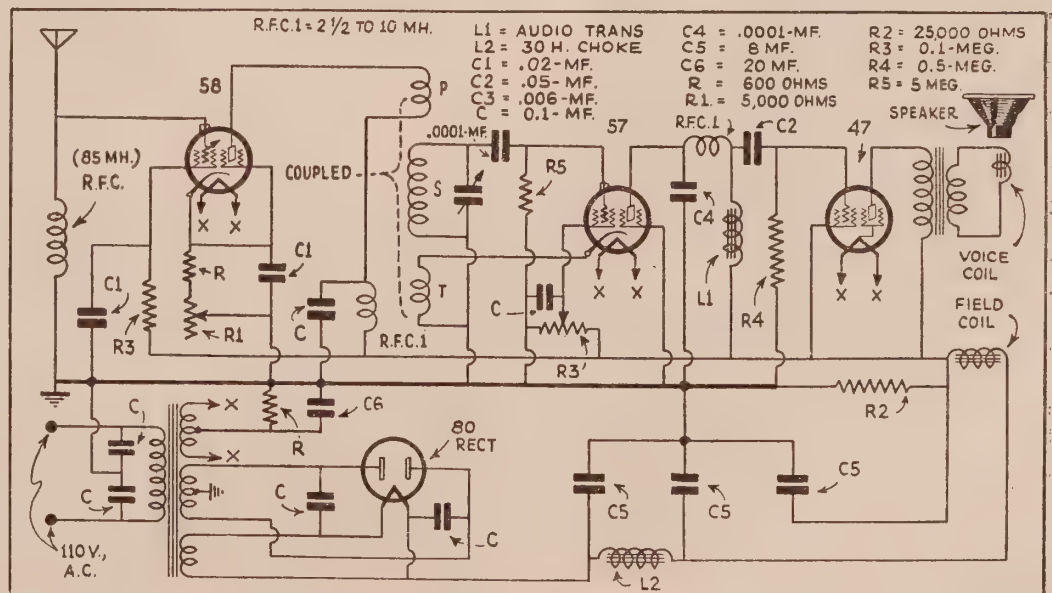

A De Luxe T.R.F. Receiver

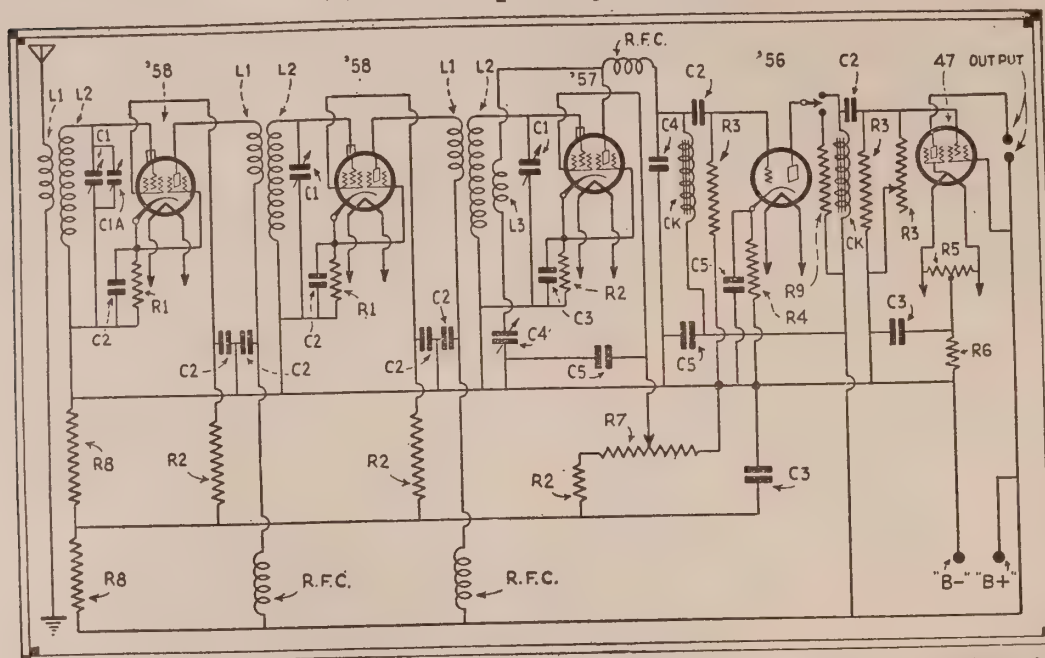With the modern high-mu tubes now available one of the most interesting types of receivers is the T. R. F. or tuned radio frequency design.



Here's the diagrams, boys, showing just how the "5 T.R.F." short-wave receiver job is hooked up. Two "high duty" R.F. amplifier stages build up the weak signals and feed them to the detector. Note the clever audio stage design.

Coil Winding Data FOR AMATEUR USE			
7 PLATE TUNING CONDENSER			
	Ant. L1	Sec. L2	Tick L3
14,000 KC	3	8	5
7,000 KC	4	15	7
3,500 KC	7	31	11
GENERAL SHORT WAVE USE			
23 PLATE TUNING CONDENSER			
	Ant. L1	Sec. L2	Tick L3
20,000—9650 KC	2	5	4
9700—4700 KC	3	11	6
4800—2500 KC	6	21	9
Use No. 22 D. S. C. on secondaries.			
Use No. 28 D. S. C. on primaries and Tickler.			
Spacing between windows 3/16".			

Parts for Receiver

- C1—.0001 mf. tuning condenser.
- Cla—2 Plate midget ant. compensator.
- C2—.02 mfd. condenser.
- C3—1 mf. condenser.
- C4—.0001 mf. condenser.
- C5—.5 mf. condenser.
- R1—400 ohm resistor.
- R2—10,000 ohm resistor.
- R3—.5 meg. resistor.
- R4—2000 ohm resistor (heavy duty type).
- R5—20 ohm center tap resistor.
- R6—360 ohm resistor (heavy duty).
- R7—50,000 ohm resistor.
- R8—25,000 ohm resistor (heavy duty).
- R9—25,000 ohm resistor.

—Short Wave Craft, Jan., 1938.

A 3-Tube "Dx'er"

Coil Data

L1	L2	L3	L4	
16	32	32	18	100-200 Meters
10	15	15	8	50-100 Meters
6	7	7	5	28- 60 Meters
5	4	4	5	13- 30 Meters

Parts List for 3-Tube DX'er

One aluminum bent and drilled base. (Blan.)

3—Subpanel sockets, (two six, one five prong). (Na-Ald)

2—Na-Ald Universal mount sockets (For raising coils).

1—75,000 Ohm potentiometer, (Centralab) (Clarostat).

1—5 plate vernier midget (Pilot or Hammarlund).

1—Two gang .00015 mf. tuning condenser.

4—.1 mf. bypassing condensers (Aerovox).

3—Radio Frequency chokes (Home-made or bought).

1—400 Ohm bias resistor (Lynch).


1—2000 Ohm bias resistor (Lynch).

1—.0001 mf. Grid condenser (Aerovox) (Polymet).

1—.0001 mf. Regeneration condenser (Hammarlund).

1—.002 mf. coupling condenser (Micamold) (Polymet).

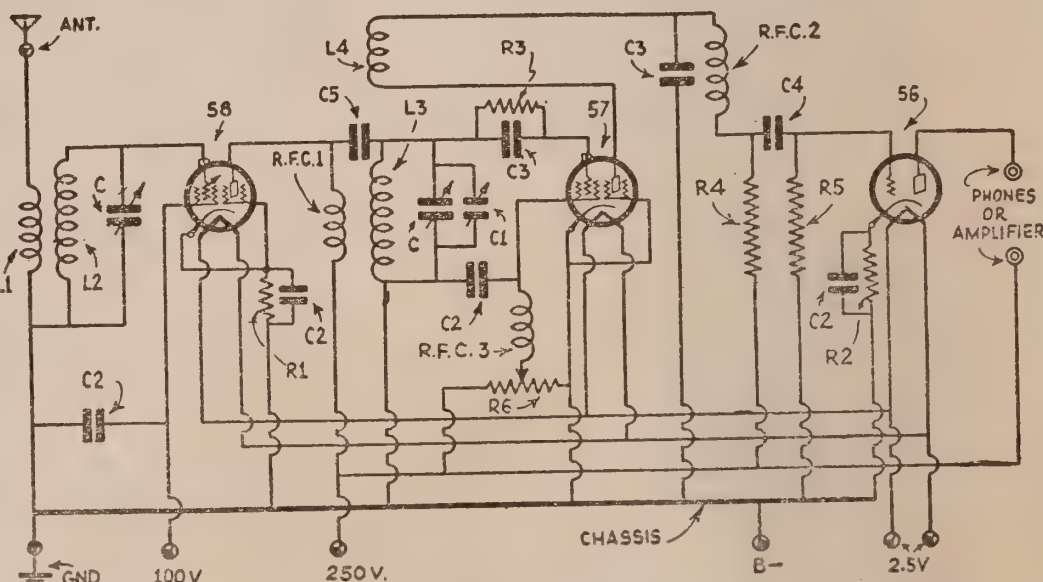1—.006 mf. coupling condenser (Sprague) (Polymet).



L1, L2, L3, L4 = SEE TEXT.
C = .00015-MF (GANGED)
C1 = .00005-MF MIDGET
C2 = .1-MF BYPASS

C3 = .0001-MF
C4 = .006-MF
C5 = .002-MF

R1 = 400 OHMS
R2 = 2, 00 OHMS
R3 = 5 MEG.

R4 = 250,000 OHMS
R5 = 500,000 OHMS
R6 = 75,000 OHM POT
R.F.C. = SEE TEXT

1—250,000 Ohm det. plate resistor (Lynch).

1—500,000 Ohm grid resistor (Lynch).

1—phone plug.

1—ant.-gnd. post.

1—58, 1-57, 1-56 tube.

Two Trutest (or other) tube shields.
1—vernier dial (preferably Pilot "Art").
Volume control and vernier knobs.

—Short Wave Craft, May, 1938.

The "Stand-By" Electrified



Parts List (Power Supply)

- 1—Acratest No. 6027 power transformer.
- 2—Eby socket, '80 type.
- 3—Mica-mold .005 m.f. condenser.
- 4—400-ohm, 5-watt resistor, Acratest.
- 5—25 mf. 25-volt dry electrolytic condenser.
- 6, 7—30-henry choke No. 2505 (Acratest).
- 8—8 mf. dry electrolytic condenser, Acratest.
- 9—8 mf. dry electrolytic condenser, Acratest.
- 10—8 mf. dry electrolytic condenser, Acratest.
- 11, 12, 13, 14—4-wire cable and plug connecting to chassis at 25.
- 15—Filament switch on "Stand-by" Receiver.

Parts List for Denton "Stand-by" Receiver

- 1—set of Octo coils (4).
- 1—XL variodens (3).
- 1—Eby '37 type wafer socket (8).
- 1—Eby '36 type wafer socket (17).
- 1—Eby '38 type wafer socket (21).
- 1—Eby antenna ground B, poststrip (1, 2).
- 1—Eby dial phone tip connector (23).
- 1—Eby L.S. tip connector (22).
- 1—G.E. power toggle switch (18).
- 1—S.P.P.T.—toggle switch (24).
- 1—Frost 50,000 ohm potentiometer (1) with insulated washers.
- 1—Carter 200-ohm potentiometer (9) with insulated washers.
- 1—Pilot midget condenser (5A) (J5).
- 1—Pilot ART dial.
- 2—International Durham $\frac{1}{2}$ -watt, 0.25-meg. resistors (18, 20).
- 1—International Durham $\frac{1}{2}$ watt .5 meg. resistor (15).
- 1—International Durham 1-watt, 25-meg. resistor (13).
- 1—1-watt, 10,000-ohm resistor (12).
- 1—1-watt, 3,000-ohm resistor (16).
- 2—Dubilier .01-mf. mica condensers (14, 19).
- 1—Eby 5-contact wafer male connector unit (25) with female receptacle and wire cable.
- 1—.001-mf. mica Aerovox condenser (10).
- 1—.000125-mf. mica Illini grid condenser (6).
- 1—5-meg. International Durham grid leak (7).
- 1—National .0005-mf. condenser cut down to .00015-mf. (5).
- 1—"Blan" aluminum box and chassis cut and drilled to specifications, with special coil cover "cap" and bakelite coil mounting assembly.
- 12—Insulated eyelets.
- 2—Grid grip screen-grid clips.
- 15 feet rubber-covered (push-back) wire. nuts, bolts, lockwashers, soldering lugs, etc.


—Short Wave Craft, June, 1932.

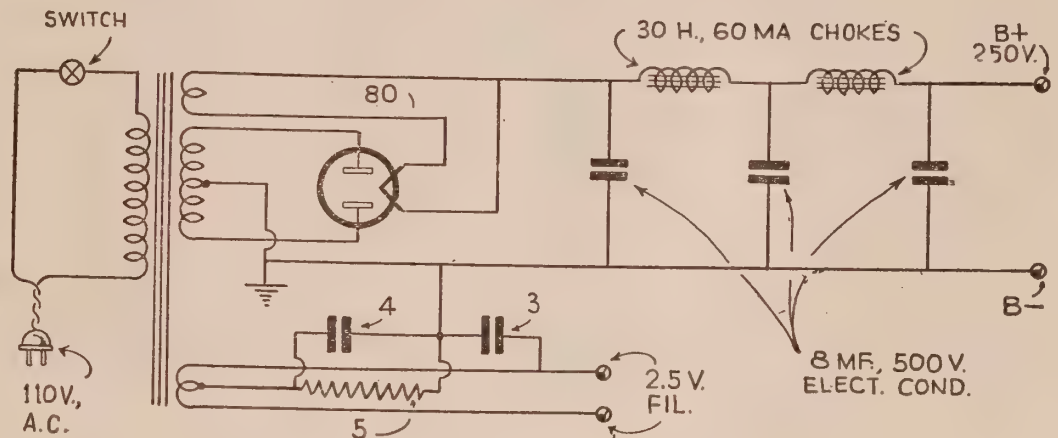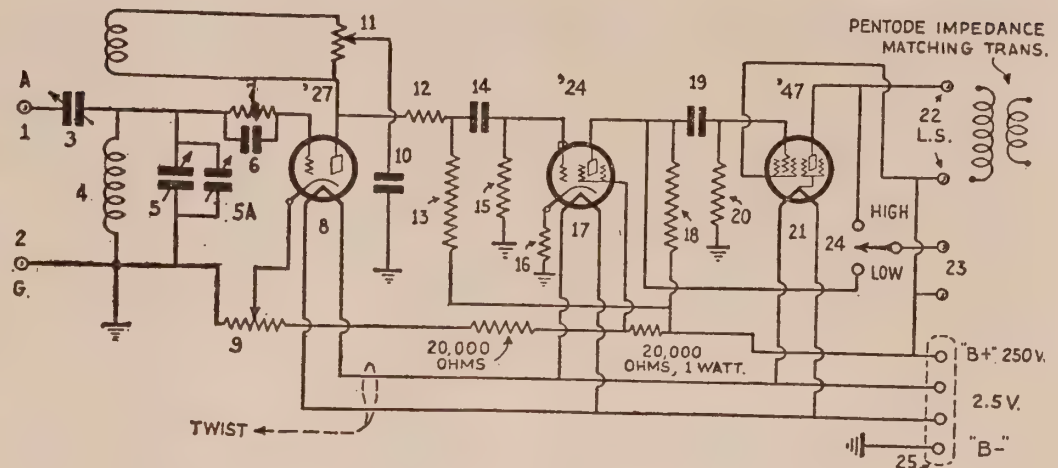

An All Purpose Receiver

List of Parts


- 1—.0002 mf. Hammarlund Midget variable condenser.
- 1—.0001 mf. Sangamo fixed condenser with clips.
- 1—Grid-leak two to seven megohms.
- 1—.00035 mf. fixed regeneration by-pass condenser.
- 1—0.1 mf. by-pass condenser.
- 1—80 mmf. Hammarlund "equalizer" condenser.
- 1—50,000 to 100,000 ohm Centralab variable resistor (Clarostat).
- 1—10 to 50 ohm filament rheostat.
- 1—short-wave R.F. choke.
- 1—Hedgehog audio transformer (1 to 4 ratio).
- 1—Pilot five-prong socket (or Na-ald).
- 2—Pilot four-prong sockets (or Na-ald).
- 4—Pilot five-prong plug-in coil forms (Gen-Win).
- 1—Bud five-prong plug-in coil form (Gen-Win).
- 1—Five-prong tube base.
- 1—5"x6 $\frac{1}{2}$ " bakelite panel.
- 1—Wooden cabinet 5"x6 $\frac{1}{2}$ "x2 $\frac{1}{2}$ " (inside dimensions).
- 1—Wafer adaptor (grid to filament).
- 1—3" dial for tuning condenser.

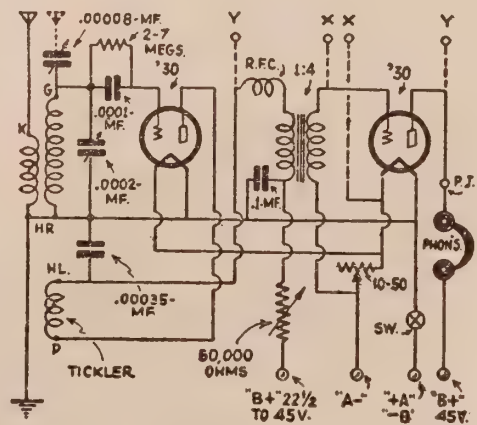

- 2—knobs for rheostat and regeneration control.
- 1—Flashlight bulb and socket.
- 1—Phone tip and jack.
- 1—Small battery clip.
- 2—10 to 15 mh. R.F. chokes.
- 2—Fahnestock clips.
- Tubes, batteries, hook-up wire, and hardware wind up the list of parts.
- Standard coils are used.

—Short Wave Craft, April, 1933.

The Minidyne Works on "Loop"

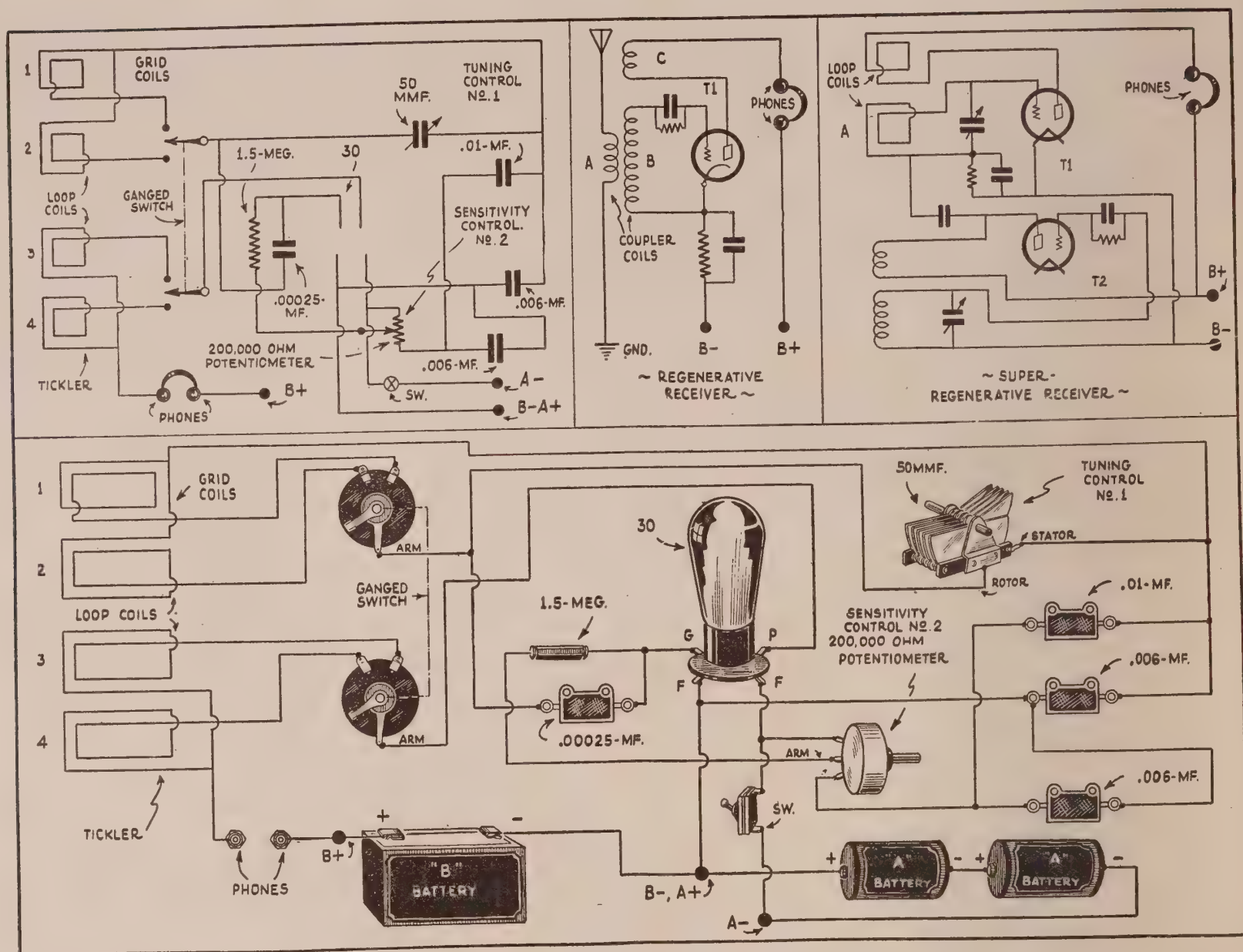

Coil Data and Parts List for "Minidyne"

The loop and aerials used on the "Minidyne" are wound in slots extending around the cabinet. The mean size of these slots

are $4\frac{1}{4}$ by $5\frac{3}{4}$ inches, the slots being about $\frac{3}{16}$ inch deep and $\frac{3}{16}$ inch wide. For the 80 meter band, the grid coil consists of 5 turns of No. 32, double silk covered (D.S.C.) magnet wire; the tickler coil consists of four turns of the same sized wire, wound in the same slot.

In the model shown, the coils were not wound in even layers, but they may be if the builder so desires.



For covering the 160 meter band, the grid coil is made up of 10 turns of No. 28 D.S.C. wire (or No. 10-30 Litz wire may be used.) The tickler coil comprises 5 turns of No. 32 D.S.C. magnet wire.

The experimenter can easily wind other loop coils for this set to cover any desired bands, by simply using a smaller or greater number of turns of wire on the loop.

List of Parts—Minidyne

- 2—Loop coils as specified.
- 1—Wooden cabinet.
- 1—Earphone, preferably new miniature 2,000 ohm earphone (or pair of light weight phones) No. 118. Name and address of manufacturer furnished on receipt of stamped, addressed envelope.

(Continued on next page)

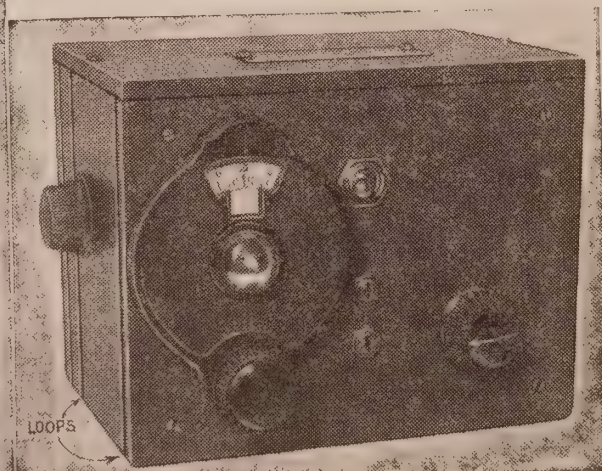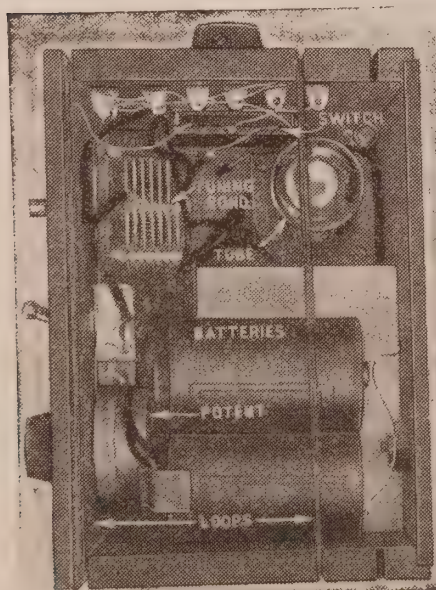

The "Pal" 2-Tube Portable

Complete List of Parts Required

- 1—Hammarlund Dual Midget Condenser, .00014 mfd. per section, type MCD-140-M (3, 15).
- 1—75,000 ohm Volume Control Potentiometer, type RI-202-P (10) with switch (31).
- 1—400 ohm, 50 watt Wire Wound Resistor, type C-4, with sliding clip set at 340 ohms (30).
- 1—Set of Alden Plug-in Coils—four coils to set—covering short wave band from 15 to 200 meters, type 704 SWS (2).
- 1—Alden Plug-in Coil Covering Broadcast band, type 704 SWO (2).
- 1—Set of Alden Plug-in Coils, type 705 SWS, with primary changed as explained below (16).
- 1—Plug-in Coil, type 704SWO with primary changed as explained below (16).
- 1—Mica Condenser, .00005 mfd. (13).
- 4—Mica Condensers, .0001 mfd. (4, 6, 7, 18).
- 2—Cartridge Condensers, .006 mf. (1, 26).
- 2—Cartridge Condensers, .01 mf. (11, 20).
- 1—Cartridge Condenser, .1 mf. (14).
- 1—Electrolytic Cartridge Condenser, 4 mf., 150 volt (28).
- 2—Electrolytic Condensers, Cardboard Container, 4 mfd. (17, 29).
- 1—Cartridge Electrolytic Condenser, 10 mfd., 25 volt (22).
- 1—I. R. C. 1000 ohm, $\frac{1}{2}$ watt Metallized Resistor, type F $\frac{1}{2}$ (23).
- 2—I. R. C. 5000 ohm, $\frac{1}{2}$ watt Metallized Resistors, type F $\frac{1}{2}$ (14-A, 25).
- 3—I. R. C. 50,000 ohm $\frac{1}{2}$ watt Metallized Resistors, type F $\frac{1}{2}$ (1, 12, 13-A).
- 1—I. R. C. 100,000 ohm, $\frac{1}{2}$ watt Metallized Resistor, type F $\frac{1}{2}$ (19).
- 1—I. R. C. 200,000 ohm, $\frac{1}{2}$ watt Resistor, type F $\frac{1}{2}$ (21).
- 1—I. R. C. 1 meg., $\frac{1}{2}$ watt Metallized Resistor, type F $\frac{1}{2}$ (8).
- 2—Alden Seven-Prong Molded Sockets, type 437-A (5, 24).
- 1—Lafayette 6F7 Tube (5).
- 2—Alden 4-Prong Molded Sockets (2, 16).
- 1—Lafayette 12A7 Tube (24).
- 1—Lafayette Magnetic Speaker, Small Size (27).
- 1—Roll Hook-up Wire, Solid Core.
- 1—Drilled Metal Chassis $9\frac{1}{4}'' \times 4\frac{1}{4}'' \times 1\frac{3}{4}''$ high; Blan.
- 1—Noise Eliminating Aerial Lead-in System; Lynch.


(Numbers in parentheses refer to corresponding numbers on diagram.)

Alden 4-Pin Plug-in Coil Data

Meters Wave-length	Grid coil turns	Tickler turns	Distance between 2 coils
200-80	52 T. No. 28 En. Wound	19 T. No. 30 En. Close wound (CW)	$\frac{1}{8}''$
80-40	32 T. per inch	11 T. No. 30 En. C. W.	$\frac{1}{8}''$
40-20	23 T. No. 28 En. Wound	9 T. No. 30 En. C. W.	$\frac{1}{8}''$
20-10	16 T. per inch	7 T. No. 30 En. C. W.	$\frac{1}{8}''$
	3-32" between turns		
	5 T. No. 28 En.	7 T. No. 30 En.	
	3-16" between turns		

Coil form— $2\frac{1}{8}''$ long by $1\frac{1}{4}''$ dia. 4-pin base.

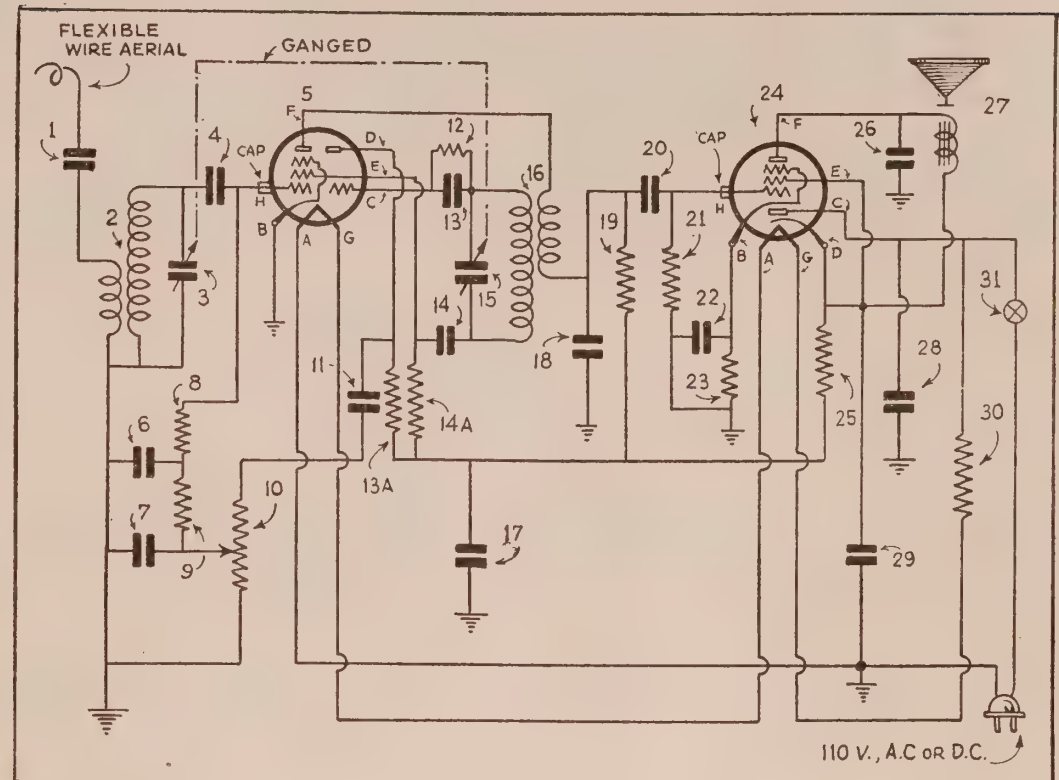Before it can be used at (16), the standard Alden four-prong coil must be altered as follows: First remove the small wind-



ing on the bottom of the form. Then wind an interwinding between the turns of the secondary. The number of turns should equal two-thirds of the particular coil being changed. Number 34 to 36 enamelled wire should be used. The new winding should be connected to the prongs in place of the one which was removed.

Using only two tubes to obtain loud speaker operation, the new "Pal" Portable represents a distinct innovation in receiver design. In this set, the trend towards compactness and simplification has been followed to its logical conclusion. Each one of the tubes used possesses the ability to perform several different functions.

The 6F7 tube consists of two separate units, one a pentode and the other a triode. The pentode unit serves as the first r.f. tube, while the triode unit is used as the detector. By means of a reflex circuit, the pentode unit is again utilized—this time as a first audio tube.

The 12A7 tube combines the functions of a power output pentode and a rectifier unit. As in the case of the 6F7 tube, the two units are both mounted within the

same envelope. There is a separate 6.3 volt heater for each unit, the heaters being connected in series internally. Hence, this tube has a rated heater voltage of 12.6 volts.

It can thus be seen that these two tubes are made to perform the same functions which would ordinarily call for the use of five separate tubes.

The "Pal" gives loud speaker operation with only two tubes. Local stations come in at "room" volume, using only an indoor aerial. Two of the newest tubes, the 6F7 and the 12A7 are used in the unique circuit whereby the 6F7 functions as a r.f. stage, while the 12A7 acts as a second audio (output) stage and a rectifier. The utilization of the "Cisin" A.C.-D.C. circuit permits operation on any house lighting circuit without changes in tubes or wiring. While the present design is that of a standard "sub-midget", this receiver may be built up in such compact size that it will fit into a coat pocket! Alden plug-in coils enable this set to bring in short wave and broadcast stations. Both coils are tuned by a compact dual Hammarlund variable condenser.

—Short Wave Craft, March, 1934.

The MINIDYNE

(Continued from last page)

- 1—Set of 2 pin jacks.
- 1—200,000 ohm potentiometer, Acratest.
- 1—1.5 megohm grid leak, Lynch, (International).
- 1—.00025 mf. condenser.
- 2—.006 mf. condensers.
- 1—.01 mf. condenser.
- 1—50 mmf. variable condenser, Hammarlund, (National).

- 1—2-gang single-pole, double-throw switch, Eby.
- 1—4 prong tube socket, Eby, (Na-ald, Hammarlund, National).
- 1—30 type tube; Gold-Seal, (Arco, Van Dyke).
- 1—22 $\frac{1}{2}$ volt small "B" battery unit.
- 1 $\frac{1}{2}$ volt flash light cells for "A" battery.


—Short Wave Craft, Oct., 1933.

2 Tube AC-DC Wave-Master

Parts List

- 1—.00015 mf. Variable Tuning Condenser. National (Hammarlund).
- 1—.000025 mf. Midget Variable Condenser. National (Hammarlund).
- 1—.0001 mf. Mica Condenser.
- 1—.00025 mf. Mica Condenser.
- 1—.01 mf. Tubular Condenser, 200 volts
- 1—.1 mf. Tubular Condenser, 200 volts.
- 1—.5 mf. Tubular Condenser, 200 volts.
- 1—Dual 8 mf. Electrolytic Condenser, 200 volts (Find-All).
- 1—1,500 ohm $\frac{1}{2}$ watt Carbon Resistor.
- 1—100,000 ohm $\frac{1}{2}$ watt Carbon Resistor.
- 1—15,000 ohm $\frac{1}{2}$ watt Carbon Resistor.
- 1—.5 megohm $\frac{1}{2}$ watt Carbon Resistor.
- 1—1. megohm $\frac{1}{2}$ watt Carbon Resistor.
- 1—R.F. Choke, $2\frac{1}{2}$ mh. (Find-All).
- 1—Filter Choke, 30 henry, 200 ohm (Find-All).
- 1—350 ohm Line Cord (Find-All).
- 1—100,000 ohm Potentiometer with Switch.
- 1—4-prong Moulded Socket (Na-Ald).
- 1—5-prong Moulded Socket (Na-Ald).

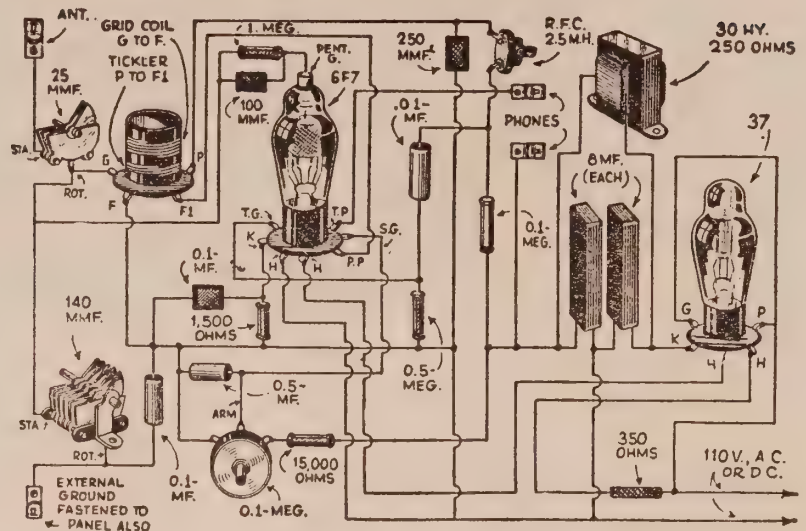Hook-up for 2 Tube A. C.—D. C. Wave-Master



- 1—Small 7-prong Moulded Socket (Na-Ald).
- 1—Piece of Aluminum for panel, 6" x 8".
- 1— $\frac{7}{8}$ " x 6" x 8" Baseboard.
- 1—Dial.
- 1—Antenna and Ground Post.
- 2—Clips for Phones.
- 1—Set of 4-prong S.W. Plug-in Coils (Find-All).

Note space between windings = $\frac{1}{8}$ "

Meters	Grid Coil	Tickler
15-25	3T. No. 26	6T. No. 26
	Enam. Wire	Enam. Wire
25-50	7T. No. 26	8T. No. 26
	Enam. Wire	Enam. Wire
50-100	15T. No. 26	12T. No. 26
	Enam. Wire	Enam. Wire
100-200	40T. No. 32	13T. No. 32
	Enam. Wire	Enam. Wire

—Short Wave Craft, Aug., 1934.


Picking Up Europe On A Loop

How Loop Is Coupled To Detector

The set described here makes use of an untuned R.F. stage, to couple the loop aerial to the detector, the loop being connected in series with the grid circuit of the R.F. stage. The signal-to-noise level is considerably better with the "loop" than that of the regular outdoor antenna. The dimensions of the loop are 7 turns of wire, starting at a diameter of 2 feet with the turns one inch apart.

Parts For Loop Set

- 1—Set of 6-prong coils for 15 to 200 meters; National.
- 1—Hammarlund 35 mmf. Cond.
- 1—Hammarlund 100 mmf. Cond.
- 1—50,000 ohm Variable Resistor.
- 1—R.F. Choke, Value five mh., Radio Trading Co.
- 3—6-prong Wafer Sockets.
- 1—6-prong Bakelite Socket.
- 1—300 ohm Resistor, Lynch.
- 1—100,000 ohm Resistor, Lynch.
- 1—250,000 ohm Resistor, Lynch.
- 1—2 Megohm Resistor, Lynch.
- 1—1 Megohm Resistor, Lynch.
- 4—.01 mf. Cond., Flechtheim.
- 1—.0001 mf. Cond., Flechtheim.
- 1—.005 mf. Cond., Flechtheim.

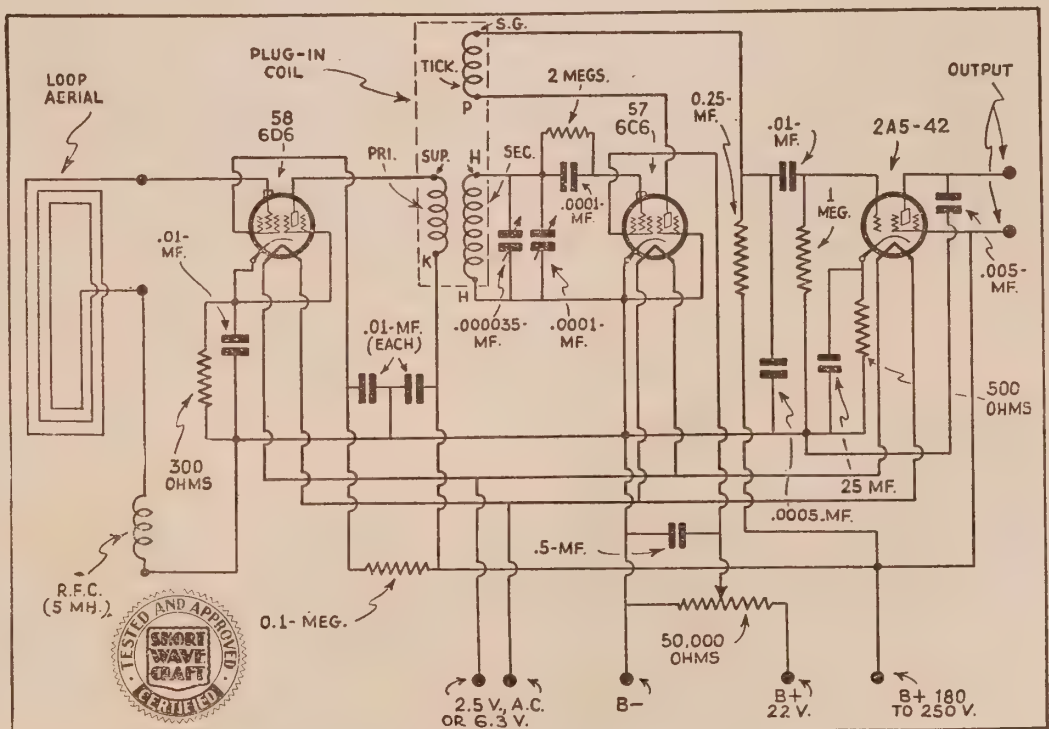

- 1—.0005 mf. Cond., Flechtheim.
- 1—25 mf. Electrolytic Cond.
- 1—500 ohm Resistor, Lynch.
- 1—Type "B" National Dial.
- 1—.5 mf. Cond., Flechtheim.
- 1—Phone Terminal Strip, Eby.

- 1—Antenna Terminal Strip, Eby.
- 1—58 Tube, Triad.
- 1—57 Tube, Triad.
- 1—2A5 Tube, Triad.

—Short Wave Craft, Aug., 1933.

The Victor Easy-Tune 2-Tube Band-Spreader


Parts List for 2-Tube Band-Spreader

- 1—Special set of coils; see table.
- 1—Special R.F. 2.5 mh. choke, (Hammarlund; I. C. A.)
- 1—100 mmf. var. condenser, Hammarlund; I. C. A.)
- 1—25 mmf. var. condenser, (Hammarlund; I. C. A.)
- 2—100 mmf. fixed condensers, I. C. A. (Polymet) (Choose nearest size).
- 1—.005 mf. fixed condenser, I. C. A. (Polymet).
- 1—35 mmf. antenna trimmer, (Hammarlund; I. C. A.)
- 2—.01 mf. bypass condensers, Polymet.
- 1—.001 mf. bypass condenser, Polymet.
- 1—.05 mf. bypass condenser, Polymet.
- 1—2 meg. grid-leak, Lynch.
- 2—0.1 meg. resistors, Lynch. (I. R. C.)
- 2—0.5 meg. resistors, Lynch. (I. R. C.)
- 1—50,000 ohm variable resistor. Acratest I. C. A.)
- 1—4-prong wafer socket, Na-Ald.
- 1—6-prong wafer socket, Na-Ald.
- 1—4-prong Isolantite socket (Hammarlund; I. C. A.)
- 1—dial.

Coils Wound on Tube Bases

The coils are wound on four-prong tube-bases, with number 30 d.c.c. wire. The following is the number of turns for the various bands:

Band	Grid to Fil.	Fil. to Ground
80m.	20 t.	1½ t.
40m.	12 t.	1½ t.
20m.	3 t.	1¼ t.

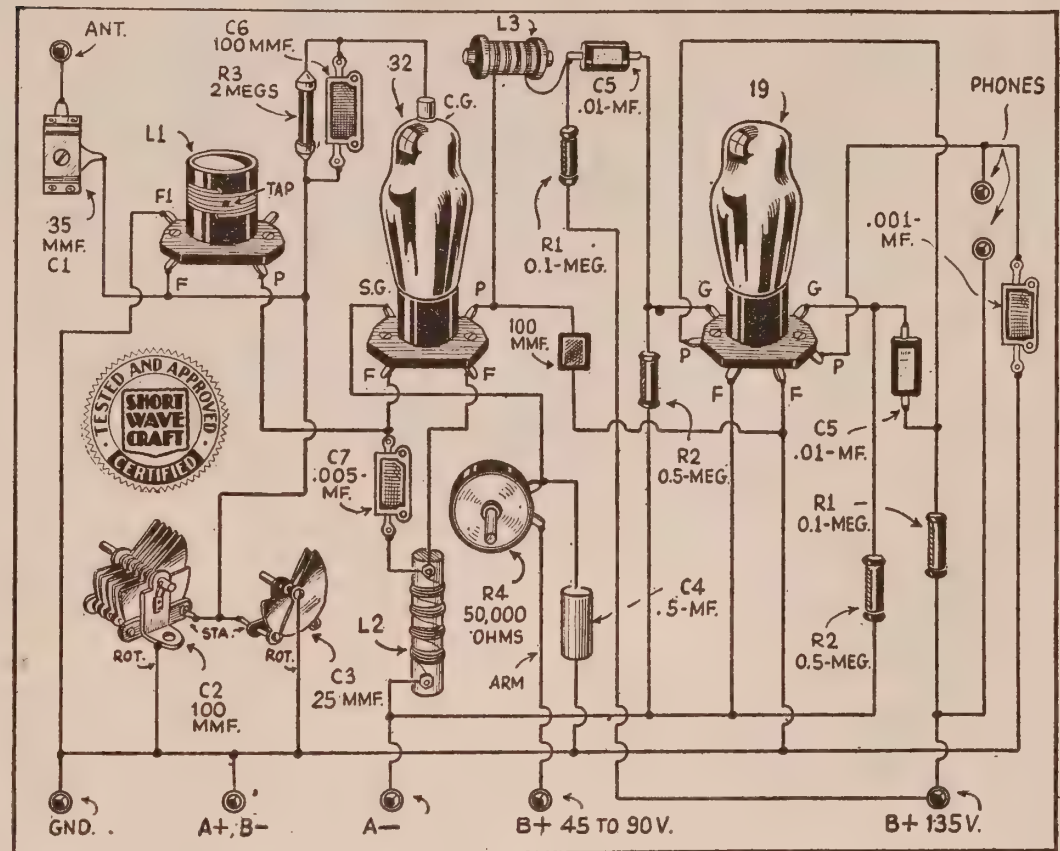

A little juggling with the tickler section of the coil, that is, moving it up and down After the coils are correct, coat them with collodion or Duco, so that they will hold their characteristics.

—Short Wave Craft, June, 1934.

Modernized Meyers 3-Tube Set

Data for Coils in Myers Receiver


Range	L2	L3	L4
18-26 met.	6 turns	1 turn	6 turns
37-63 met.	10 turns	1 turn	15 turns
61-100 met.	15 turns	1 turn	30 turns
100-190 met.	20 turns	2 turns	60 turns

All wound with No. 28 DSC on five-prong forms.

CONSTANTS OF THE CIRCUIT

- C—.006 mf. mica condenser.
 C1—3 plate midget condenser.
 C2—50 mmf. condenser.
 C3—100 mmf. fixed condenser.
 C4—100 mmf. fixed condenser.
 C5—1 mf. fixed condenser.
 C6—.01 mf. fixed condenser.
 R1—300 ohm, 1 watt resistor.
 R2—100,000 ohm, 1 watt resistor.
 R3—5 megohms.
 R4—500,000 ohm potentiometer.
 R5—1,000 ohm, 1 watt resistor.
 R6—50,000 ohm potentiometer.
 R7—30 ohm center tap resistor.
 L1—100 turns on half inch form.
 L5—Aero Hi-Peak coupler.
 L6—National S-101 coupler.

—Short Wave Craft, April, 1933.

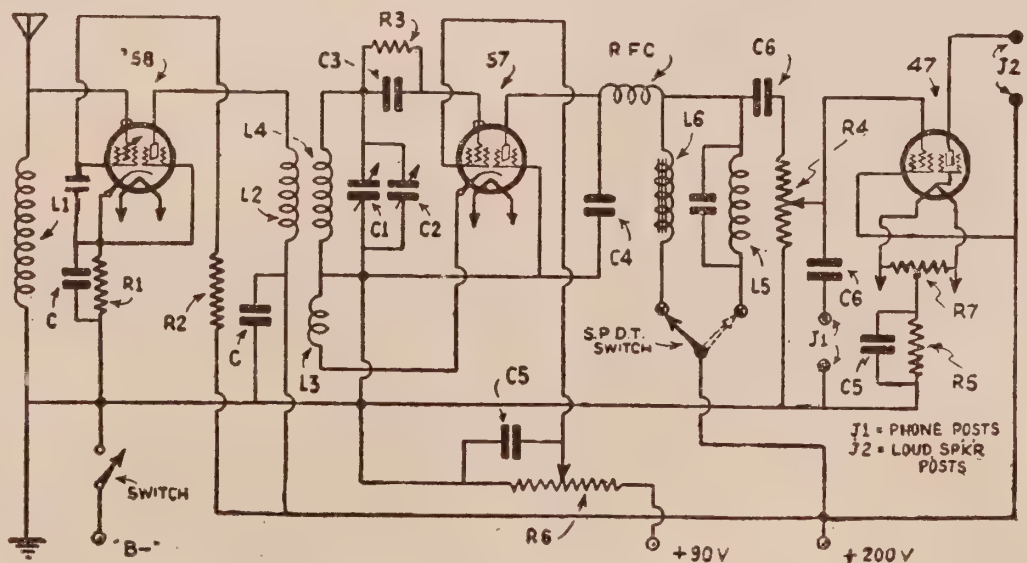

The Electrodyne 1-Tube Set

This attractive one tube receiver, of undoubted interest to every short-wave beginner, employs the latest electron-coupled circuit. Distant short-wave transmitters in practically every country were heard with this receiver.

Parts List for Electrodyne


- 1—35 mmf. antenna trimmer, National (Hammarlund).
- 1—100 mmf. National 270 degrees condenser cut down, see text.
- 1—100 mmf. condenser, variable, National (Hammarlund).
- 1—.005 mf. mica condenser.
- 1—.00015 mf. mica condenser.
- 1—.001 mf. mica condenser.
- 1—.05 mf. by-pass condenser.
- 1—1 meg. half watt resistor, Lynch (I.R. C.).
- 1—100,000 ohm variable resistor, Acratest.
- 1—2.5 to 5 mh. choke, National (Hammarlund).
- 1—filament choke (special), see text.
- 1—3 to 1 audio transformer, National (or other make).
- 2—four prong Isolantite sockets, National (Hammarlund).
- 1—dial, National type B; 270 degree.
- 1—set of coils, see coil table.
- 1—232 type tube, R. C. A. Radiotron Arco).

Coils Wound On Tube Bases

The coils are wound on four-prong tube-bases, with number 30 d.c.c. wire. The following is the number of turns for the various bands:

Band	Grid to Fil.	Fil. to Ground
80m.	20 t.	1½ t.
40m.	12 t.	1½ t.
20m.	3 t.	1¼ t.

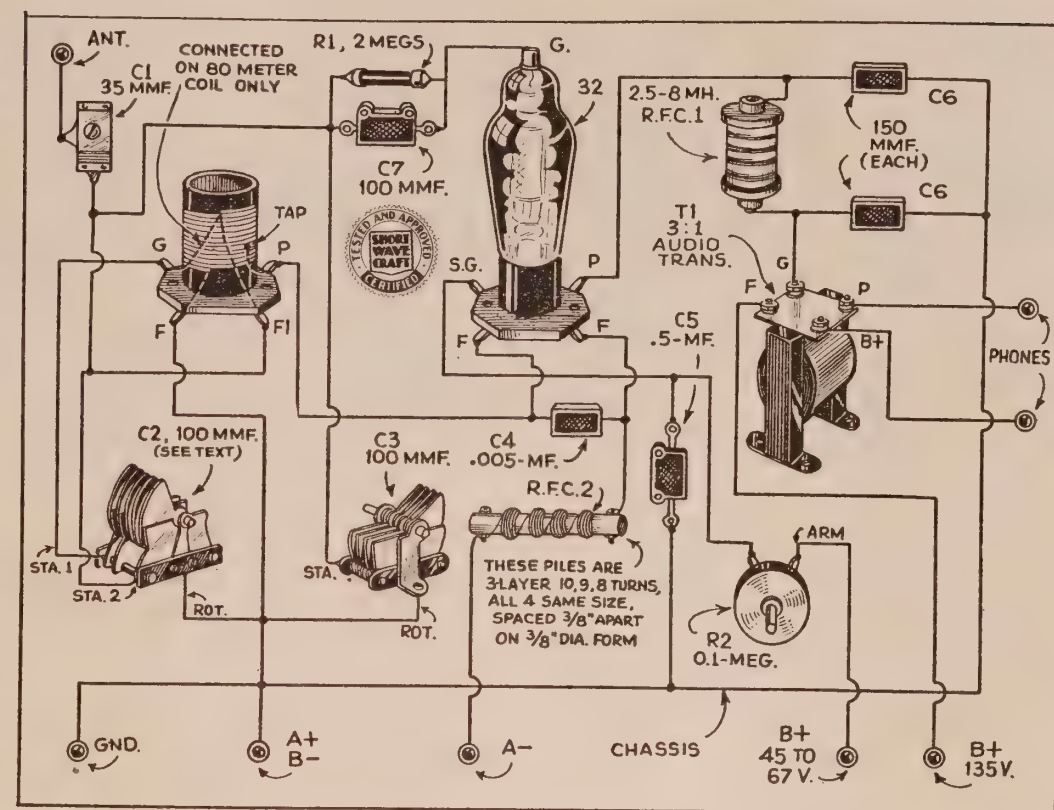A little juggling with the tickler section of the coil, that is, moving it up and down on the tube base, may be necessary to get the set oscillating properly over the entire band with the particular antenna used. After the coils are correct, coat them with collodion or Duco, so that they will hold their characteristics.



This set having been built primarily for the amateur bands, a dual condenser arrangement is used for spreading the crowded amateur bands over a large portion of the dial. A National 100 mmf. variable was cut down into two sections, five plates and two plates. On twenty and forty meters the two plate section is in parallel with the 100 mmf. band-finding condenser, and spreads the bands over most of the dial, allowing easier tuning. On eighty meters the two plate section would not be sufficient to cover the entire band, so the extra five-plate section is thrown in parallel with it. This is accomplished by connecting the five-plate section to the blank prong on the coil socket. In the eighty meter coil a wire is run from the grid prong to the blank prong, and thus when the coil is plugged in, the extra section of condenser is thrown in parallel with the two-plate condenser.

Filament Choke Used

Since the tube is directly heated, and it is necessary to keep the filament above ground R.F. potential, a filament choke is necessary. The .005 mf. condenser across the filament is used to provide a low-impedance path for R.F. so that both sides of the filament may be at the same potential above ground. The filament choke is wound on a piece of 3/8 inch dowel, 4 inches long. There are four pies of number 28 cotton covered wire on it. Each of these pies is wound in three layers. The bottom layer ten turns, the second layer nine turns, and the top layer eight turns. The pies are spaced 3/8ths of an inch apart. After the choke is completed it should be covered with a coat of collodion or clear Duco. With a little care this choke can be properly made, and caution should be taken, as the choke is one of the most important parts of the set.

—Short Wave Craft, May, 1934.

Unitrol Simplifies Band-Spread

(Continued from previous page)

To construct the special tuning condenser shown in the drawing it is necessary to obtain one 20 mmf. and one 140 mmf. Hammarlund tuning condensers. These were chosen because they lent themselves readily to the arrangement.

A one-eighth inch hole is drilled through the center of the shaft of the 20 mmf. condenser unit. It is best, if one does not have a drill-press or lathe, to take it to the local machine shop and have it done accurately. After this is done saw a slot in the front of the shaft to fit a piece of number 14 buss

bar. A similar slot is cut in the front of the 140 mmf. condenser shaft. These slots are used to lock the two condensers together. Now mount the two condensers on a metal strip as shown in the drawing and we are ready to install the shaft.


Procure a length of brass shafting that will fit snugly in the hole drilled in the shaft of the small condenser. Shape the end of the shaft to fit in the slot cut in the large condenser; if a better job is wanted a pin, as used by the author, can be fitted to the end instead. Now insert the shaft and engage it in the large condenser

firmly, so that it can be marked for the front pin. The shaft has two pins, one for the rear and one for the front condenser. Mark the shaft for the pin which engages the small condenser and drill the hole very accurately as there should be no difference in the settings of the two condensers when the shaft is engaged in the two.

Thread the end of the shaft so that a small binding post-knob can be attached for shifting from "regular" tuning to "bandspread."

—Short Wave Craft, April, 1934.

2 R.F. Pentode S-W Set

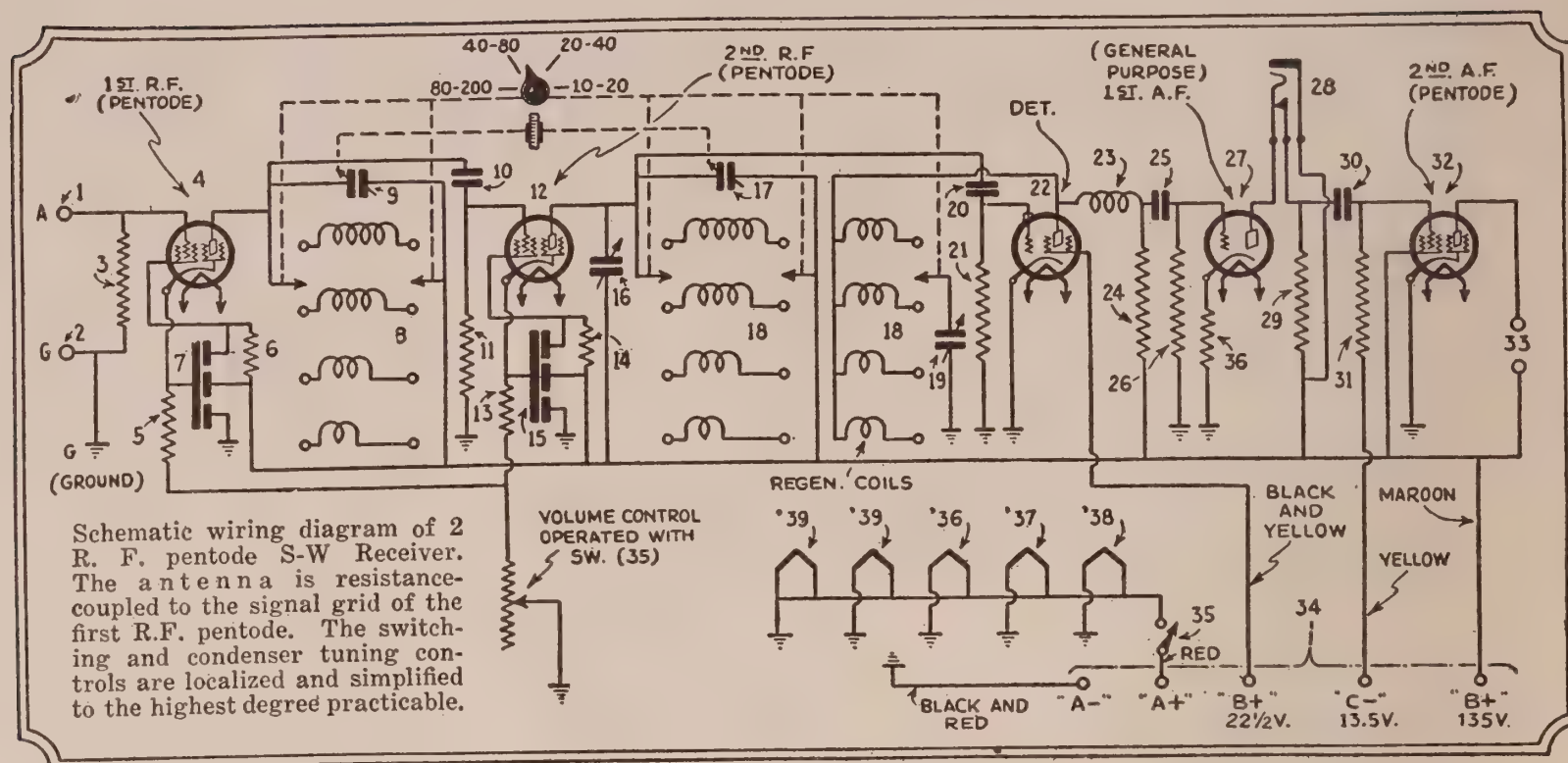

Parts List

- 1—Eby Antenna—Ground Post (1, 2).
- 3—International 1-watt Resistors (3, 6, 14), (50,000 ohms each).
- 2—Eby Wafer Sockets, '39 type (4, 12).
- 1—Eby Wafer Socket, '36 type (22).
- 1—Eby Wafer Socket, '37 type (27).
- 1—Eby Wafer Socket, '38 type (32).
- 1—Hammarlund Dual Condenser, MDC-140M (140 mmf. each section) (9, 17).
- 1—Hammarlund Condenser, MC-250M (260 mmf.) (19).
- 3—Hammarlund Tube Shields.
- 2—Blan By-Pass Condensers, triple 0.1-mf. (7, 15).
- 2—International 1-watt Resistors, 500-ohm. (5, 13).
- 1—Electrad Volume Control RI-202P (35) with power switch.
- 1—Crowe Tuning Dial.
- 1—"Best" Mfg. Co., Multi-Range Inductance Unit (8).
- 1—"Best" Mfg. Co., Multi-tuner Regenerator Unit (18).
- 1—Pilot 5-Plate 15 mmf. Midget Condenser with Insulating Washers (16).
- 2—Illini Mica Condensers, 125 mmf. (10, 20).
- 1—Pilotohm 3 megs. (21).
- 1—Pilotohm 3 megs. (11).
- 1—Blan "Best" Tuner Shield, drilled and folded, with coil mounting brackets.
- 1—Blan R.F. Choke.
- 1—Blan Flexible Coupler, complete with extension shaft and reducing bushing.

Ten to two hundred meters—all the short-waves—At a "twist of the wrist" and with two stages of "working" radio frequency amplification to boot, the receiver incorporates a multi-stage, pentode, R.F. amplifier plus a regenerative detector and a resistance-coupled audio amplifying system. 6.3 volt tubes are used throughout, making it possible to operate the heaters from a storage battery or from an AC transformer.

- 2—Dubilier .015-mf. Mica Metal-Bound Condensers (25, 30).
- 3—International Resistors, one-half watt, 0.25-meg. (24, 26, 31).
- 1—International Resistor, one-half watt, 0.1-meg. (29).
- 1—Eby Speaker Twin Jack (33).
- 1—Frost Closed-Circuit Jack, with insulating washers (28).
- 1—International Resistor, 1-watt, 2,500-ohm. (36).
- 1—Eby 5-Prong Male-Type Wafer Socket, with female plug and cable (34).
- 1—Grid-Grip Screen-Grid Clip.
- 9—Insulating Eyelets.
- Miscellaneous Nuts, Bolts, Soldering Lugs, etc.
- 20 ft. Rubber Covered Push-Back Wire.
- 1 Dial Lamp and Socket.

The radio-frequency stages are of the tuned-plate type and, with a tuning condenser which has an isolantite base, it is not necessary to insulate the rotor from the chassis. It is important to note that the rotor shaft of the condenser should not "ground" through the tuning dial; use the flexible coupling.

The detector is the standard leaky-grid type, with condenser control of regeneration.

Resistance coupling is used throughout the audio system, which has a low-impedance tube in the first stage and a pentode in the output circuit.

The phone jack is handy for tuning in distance, and its use in the plate circuit of the first audio stage does not cause a change in any of the preceding stages.

All of the tubes are of the six-volt type, and operate directly from a storage battery or from an A.C. transformer.

A 75,000-ohm variable resistor is used in the cathode circuits of the radio frequency tubes as a volume control.


After the batteries have been connected as shown in the diagram, turn the radio-frequency volume control full on; this closes the filament circuit. Wait a short time for the tubes to heat up.

Select the waveband to which you want to listen by moving the band selector switch to the proper point, as shown on the indicator furnished with the coils.

Turn the regeneration control knob and, if the receiver does not give the familiar response, reverse the leads to the feedback coils on the larger tuning unit.

If the detector oscillates, turn the master tuning condenser dial until a voice or telegraph signal is heard. Adjust the trimming condenser for maximum response.

—Short Wave Craft, April, 1932.

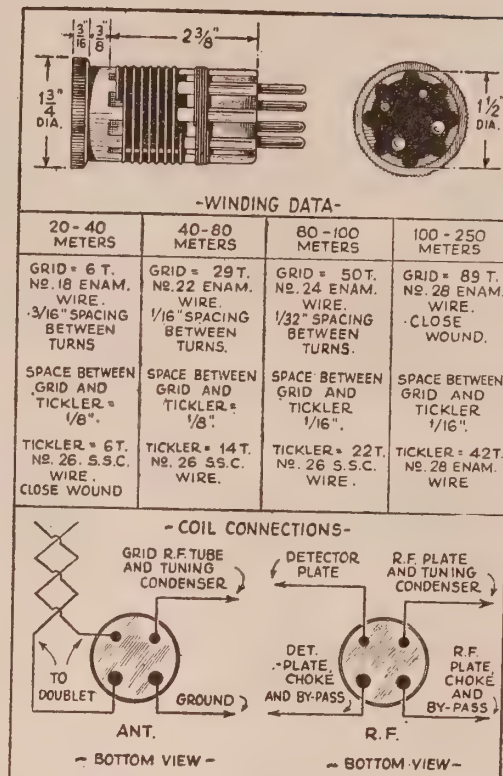

COILS

- 2—Sets (8 coils) Coils.
2—Bud 30 mh. R.F. Choke Coils.

1—.00014 mf. two-gang tuning condenser.
1—.00005 mf. Hammarlund Midget Condenser.
2—8 mfd. 500 v. Electrolytic Condensers.
3—.25 mf. 400 v. Condensers.
4—.25 mf. 200 v. Condensers.
1—.02 mf. 400 v. Condenser.
3—.01 mf. 400 v. Condensers.
1—.0002 mf. Mica Condenser.
1—.0001 mf. Mica Condenser.

1—50,000 ohm Variable Potentiometer with Switch.

1—100,000 ohm 1-watt Carbon Resistor.

1—25,000 ohm 1-watt Carbon Resistor.

1—4 meg. $\frac{1}{2}$ -watt Carbon Resistor.

1—500,000 ohm $\frac{1}{2}$ -watt Carbon Resistor.

1—250,000 ohm $\frac{1}{2}$ -watt Carbon Resistor.

1—150,000 ohm $\frac{1}{2}$ -watt Carbon Resistor.

1—15,000 ohm $\frac{1}{2}$ -watt Carbon Resistor.

1—350 ohm $\frac{1}{2}$ -watt Carbon Resistor.

1—Power Transformer. Rating:
1 650 V. 60 Ma. HV Secondary.
1 2.5 V. 5 A. Secondary.

- 1 5 V. 2 A. Secondary.
1 110/190 V. Primary.

- 1—300 henry Choke—3 Ma. capacity.

- ### 1—"RGH-4" Chassis.

- 1—Coil Shield.
2—58 Tube Shields.

- ### 5—Wafer Sockets.

- ### 1—5-prong Speaker Plug.

- ### 2—4-prong Coil Sockets.

- 1—Dial-Escutcheon Plate and Light Bracket.

- ### 3—Knobs.

- ### 3—Binding Posts—Phone Posts.

- 1—1,800-ohm tapped Speaker, single pentode output.

- 1—Resistor Mounting Strip.

- ### 1—Line Cord and Plug.

- 1—Roll Birnbach Hook-up Wire No. 18.

- ## 1—Solder—Hardware.

Plug-in coils are used in the RGH-4, two of the same color for each band or five sets (ten coils) for the complete range from 16 to 550 meters. The coils are mounted near the tuning condenser on the chassis. The detector coil is placed under a shield to prevent any stray feed-back to the antenna stage which is unshielded. The detector plate is impedance coupled—necessarily so since the high plate impedance of the 58 detector eliminates the possibility of transformer coupling and the high value of the required load resistor in a theoretical resistance stage would not allow the proper


effective voltage on the detector plate. The choke used in the stage is a high impedance one, with ample current carrying capacity.

Because of the high efficiency obtainable from the regenerative detector it is possible to obtain ample loud-speaker volume even on very weak foreign signals with only one stage of audio, so much so that it was found inadvisable to use more than this one stage. The bias for the 2A5 was taken from the speaker tap adding further to the economy and simplicity of the RGH-4.

Almost any kind of antenna can be used with this receiver as can be seen by glancing at the diagram. The antenna coil connections are left free on each end in order that an antenna having a two-wire feed system can be used. For antennas not having two-wire feed systems the point, P, will be connected to F on the secondary coil which is grounded. With two-wire feed systems, the antenna proper should be kept in the clear in order to derive full benefit from the feeders, which can be either parallel or transposed. In some cases an increase in signal strength can be obtained by inserting a .0005 m.f. variable condenser in series with one of the feeder wires. Adjustment of the condenser will then tend to bring the antenna system nearer to resonance with the signal frequency.

For those wishing to listen on the broadcast band above 250 meters the grid coil should have 122 turns of No. 30 enameled wire wound in a length of $1\frac{3}{4}$ inches. The tickler will have 32 turns of No. 34 wire, close-wound. Two of the above coils will be necessary.


A 3-Tube Band Spreader

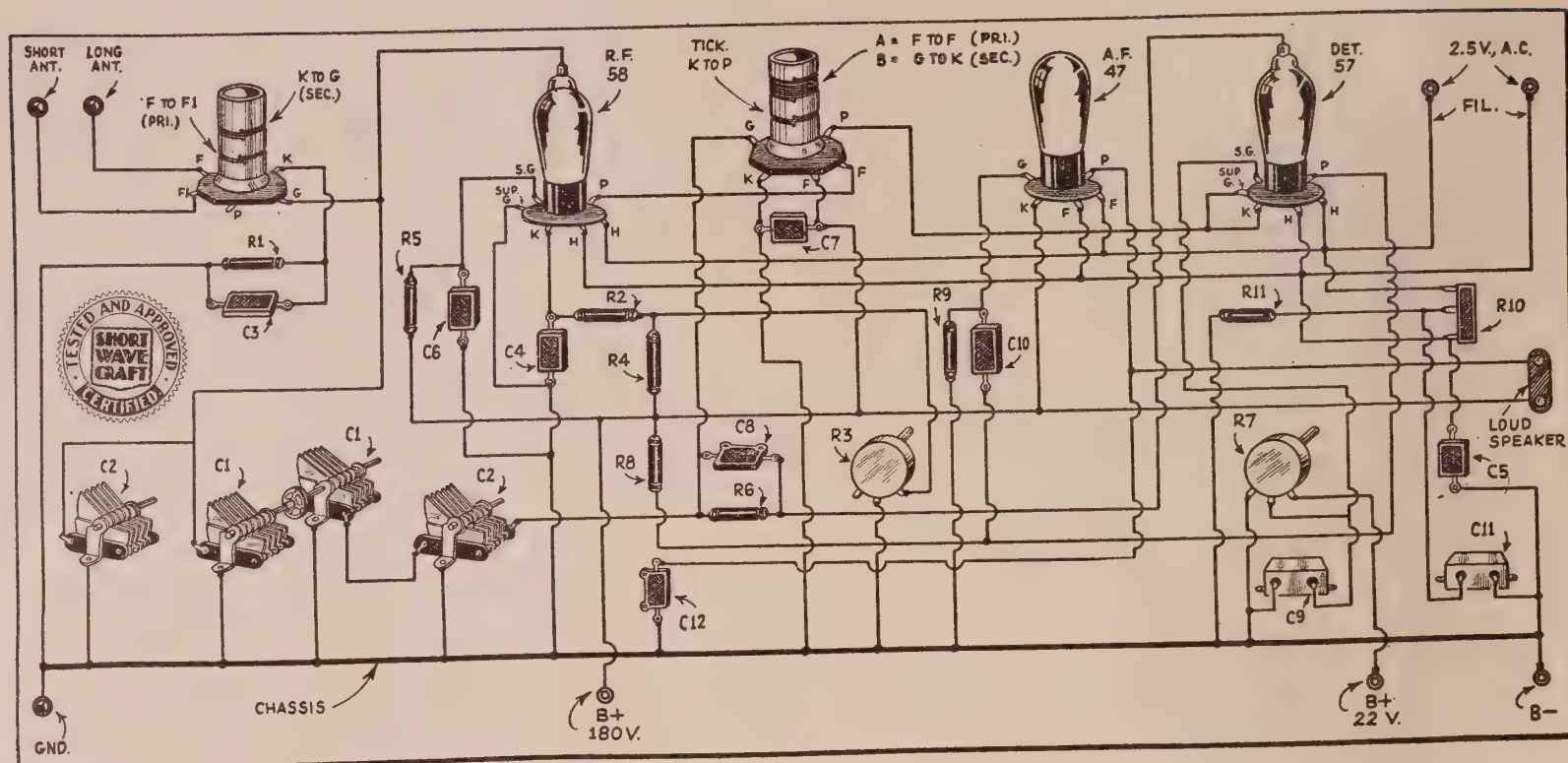

List of Parts

- 1—7x10x1/16" aluminum panel.
- 2—5 1/2 x 2 1/2 x 1/16" sheet aluminum for shields.
- 1—12x10" aluminum for base.
- 1—Type 58 tube Sylvania (R.C.A.).
- 1—Type 57 tube Sylvania (R.C.A.).
- 1—Type 47 tube Sylvania (R.C.A.).
- 6—Hammarlund coil forms (five prong) "small" Isolantite.
- 2—Hammarlund five-prong sockets Isolantite.
- 2—Hammarlund six-prong sockets Isolantite.
- 2—Hammarlund 100 mmf. tuning condensers.
- 2—Hammarlund 35 mmf. tuning condensers.
- 1—Hammarlund flexible coupling.
- 1—National type "B" dial.
- 1—100,000 ohm Electrad potentiometer (Clarostat).
- 1—5,000 ohm Electrad potentiometer (Clarostat).
- 2—Aerovox .5 mf. bypass cond. (Polymet).
- 5—Aerovox .01 mf. fixed cond. (Polymet).
- 1—Aerovox .005 mf. fixed cond. (Polymet).
- 1—Aerovox .0001 mf. fixed cond. (Polymet).
- 1—Aerovox .00025 fixed cond. (Polymet).
- 2—Aerovox 250,000 ohm resistors (Lynch).
- 1—Aerovox 100,000 ohm resistor (Lynch).
- 1—Aerovox 15,000 ohm resistor (Lynch).
- 1—Aerovox 2,000 ohm resistor (Lynch).
- 1—Aerovox 300 ohm resistor (Lynch).
- 2—Aerovox 2 megohm resistors (Lynch).
- 1—Aerovox 20 ohm C.T. resistor (Clarostat).
- 1—Eby five-prong socket.
- 1—Hammarlund "Triple-grid" tube shield.
- 1—Five-wire cable.
- 1—Antenna binding post assembly.
- 1—Speaker cord tip assembly.

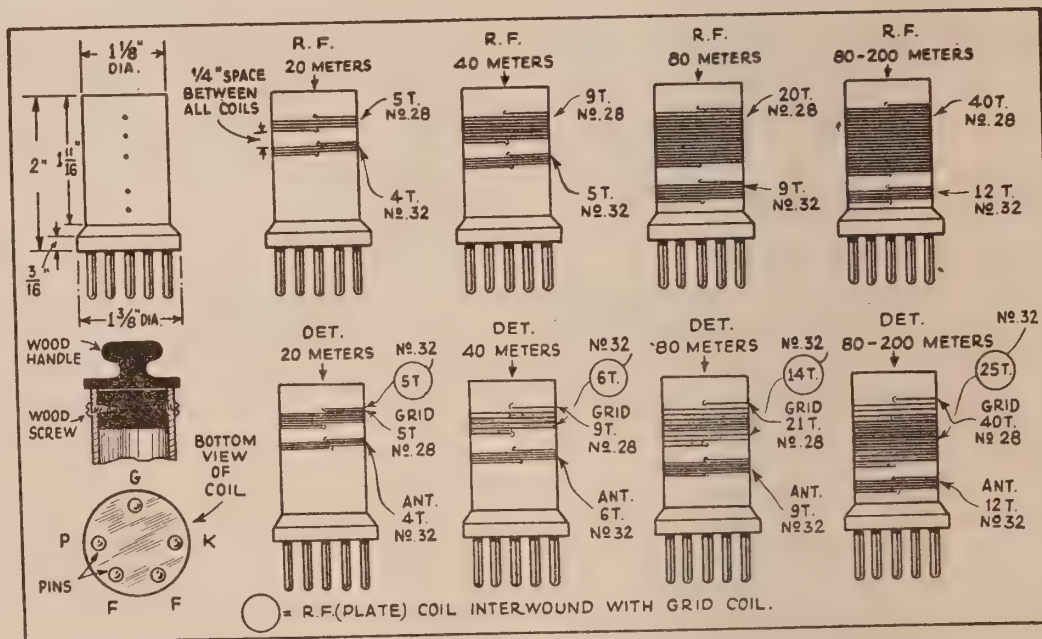As can be seen, this set uses a type 58 as the tuned R.F. amplifier and a type 57 as a detector, with a 47 as audio amplifier,



a 56 can be used instead of the 47 if ear-phones are to be used.

When using a stage of tuned R.F. ahead of an autodyne detector it is absolutely necessary to have some sort of R.F. gain control if overloading of the detector is to be eliminated. Therefore a type 58 is used in order to obtain control of volume by the cathode method. This type of control is very quiet in operation and has very little effect on the tuned circuit. As can be seen in the diagram, the grid circuit of the R.F. stage is decoupled by a 250,000 ohm resistor and a .01 mf. condenser. This helps to prevent the R.F. stage from detuning and allows the full benefit of the shielding. Screen grid voltage is obtained with a 100,000 ohm resistor which adds to decoupling and eliminates one wire in the


cable. Isolantite coil forms and socket and tube sockets are used because of their low loss.

A separate winding on the detector coil form provides the R.F. coupling between the R.F. stage and the detector. This is the most efficient means of coupling and should be used whenever high gain and stability are required. Bypass condensers are used freely but no R.F. chokes are shown because no benefit was derived from them.

The type 57 was chosen as the detector because it oscillated much better at the higher frequencies than any other type. The detector circuit is of the electron-coupled type.

—Short Wave Craft, June, 1933.

The Tetradyne 5 Tube Set

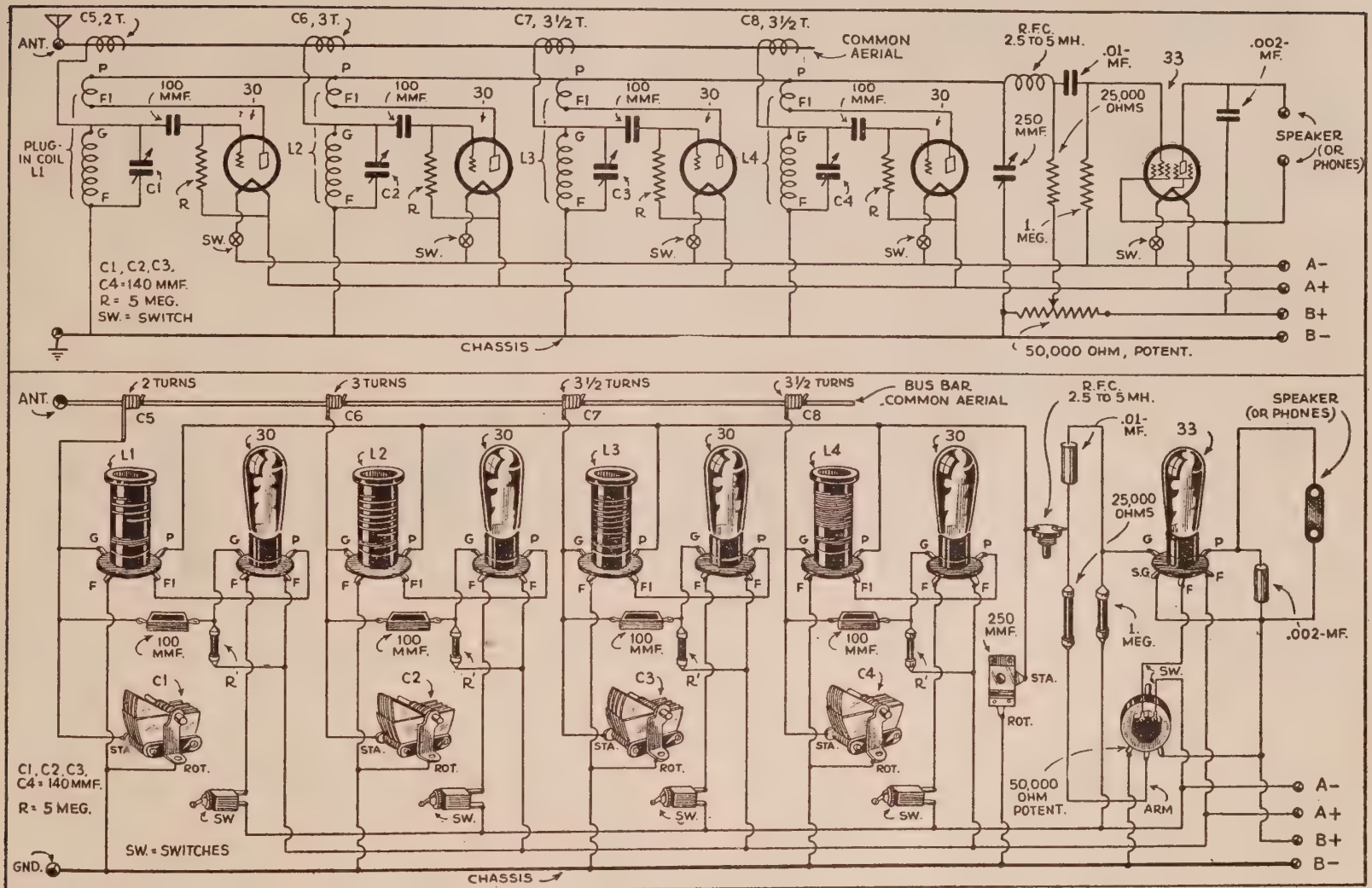

Parts List for "TETRADYNE"

- 4—140 mmf. tuning condensers, National (Hammarlund).
- 1—Set of 4-plug-in coils, Alden (Gen-Win).
- 4—4-prong Isolantite sockets, National (Hammarlund).
- 1—5-prong socket, National (Hammarlund).
- 4—4-prong sockets, National (Hammarlund).
- 4—.0001 mf. mica condensers.
- 4—5 megohm grid leaks, $\frac{1}{2}$ watt, Lynch (I. R. C.).
- 1—25,000 ohm $\frac{1}{2}$ watt resistor, Lynch (I.R.C.).
- 1—1 meg. $\frac{1}{2}$ watt resistor, Lynch (I.R.C.).
- 1—50,000 ohm variable potentiometer, with switch (Acratest).
- 4—filament switches.
- 1—.00025 mf. mica condenser.
- 1—.002 mf. mica condenser.
- 1—.5 mf. bypass condenser.
- 1—2.5 to 5 mh. R.F. choke, National (Hammarlund).
- 4—National 3-inch velvet-vernier dials.
- 1—14" x 7" aluminum panel (Blan).
- 4—UX 230 tubes RCA Radiotron (Arco).

The dream of every short-wave fan has at last been realized in this latest invention of Mr. Gernsback's—the TETRADYNE—which provides four distinct detector stages in one receiver, each stage having its own tuning condenser and coil. By merely flipping any one of four switches controlling the tubes in the different stages, each stage covering one distinct wave band, you are ready to instantly tune for stations in the "desired" stage; all without having to change plug-in coils.

- 1—UY 233 RCA Radiotron (Arco).
- 1—Antenna ground terminal strip.


- 1—Phone terminal strip.

—Short Wave Craft, April, 1934.

Na-ald Plug-in Coil Data


Meters Wavelength	Grid coil turns	Tickler turns	Distance between 2 coils
200-80	52 T. No. 28 En. Wound 32 T. per inch	19 T. No. 30 En. Close wound (CW)	$\frac{1}{8}$ "
80-40	23 T. No. 28 En. Wound 16 T. per inch	11 T. No. 30 En. C. W.	$\frac{1}{8}$ "
40-20	11 T. No. 28 En. 3-32" between turns	9 T. No. 30 En. C. W.	$\frac{1}{8}$ "
20-10	5 T. No. 28 En. 3-16" between turns	7 T. No. 30 En. C. W.	$\frac{1}{8}$ "
Coilform—2 $\frac{1}{8}$ " long by 1 $\frac{1}{4}$ " dia.		4- pin base.	

"Master Composite-4"

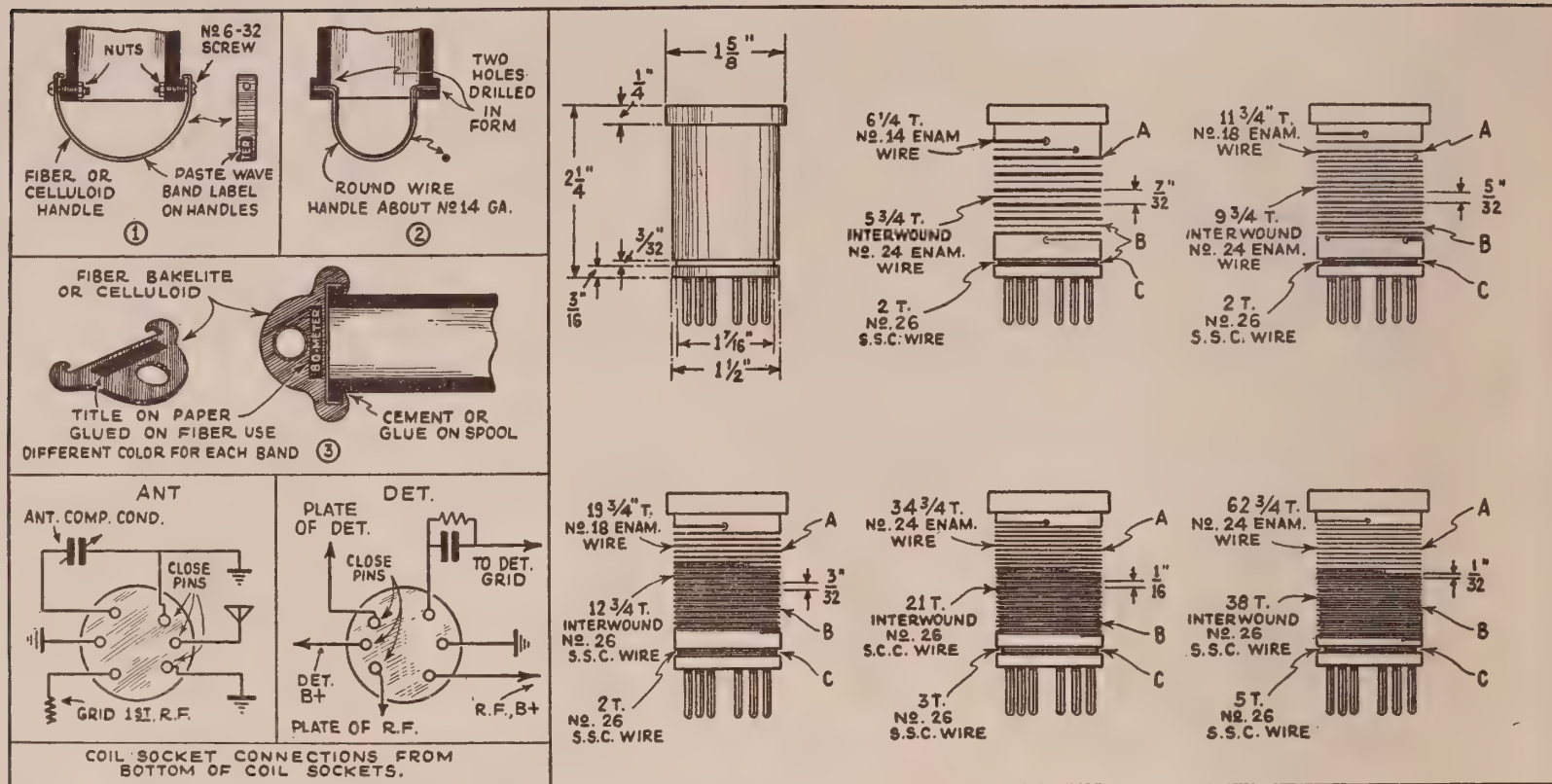

Parts List

One National Co. Type 2-SE 100 tuning condenser (Cap. 100 mmf. each section). (C2, C3.)
 Two National Co. Short Wave Chokes, Type 100, (RFC1, RFC2) (2.5 M. H.)
 One National Co. Radio Frequency Choke, Type 90 (RFC3) (90M. H.)
 One National Co. Screen Grid Coupling Impedance Type S101 (AF1).
 Two National Screen Grid Clips (V1, V2) type 24.
 Two National Coils Sockets, Isolantite 6 prongs for National Coils (L1, L2).
 Two National Isolantite Tube Sockets for 58 type tubes (V1, V2).
 One National Co. Antenna Compensating Condenser, Type ST-50 (C1) (Cap. 59 mmf.).
 One National Coil Cabinet (optional).
 Two National Co. Tube Shields Type T58 (V1, V2).
 One pair of the following National S. W. Coils, Nos. 61, 62, 63, 64, 65 (L1, L2).
 One National "Full Vision" Tuning Dial, Type VKE.
 Three Micamold .01 mf. mica condensers (C4, C5, C12).
 One Micamold .0001 mf. Mica condenser (C15).
 One Micamold .00025 mf. mica condenser (C8).
 One Flechtheim Tubular Condenser .01 mf. (C10).
 One Flechtheim Electrolytic Condenser Type LTI1000 (C11) 10 mf. 30 Vts.
 Two Flechtheim .25 mf. Bypass condensers (C6, C7) Type GF25.
 One Acratest Wire Wound Resistor. 5 Watt, 7000 ohms Cat. No. 5900 (R6).
 One Acratest Wire Wound Resistor, 5 Watt, 400 ohms Cat. No. 5900 (R10).
 One Acratest Carbon Resistor, .5 Watt, 300 ohms Cat. No. 5860 (R2).

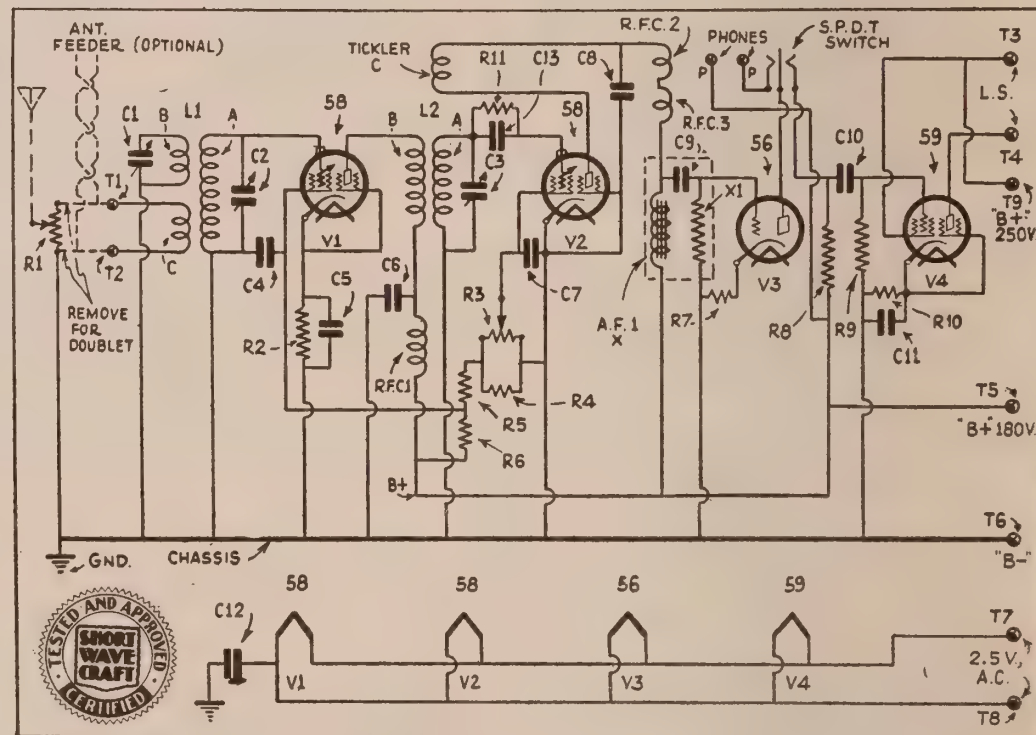

One Acratest Carbon Resistor, .5 Watt, 2000 ohms Cat. No. 3500 (R7).
 One Lynch Mfg. Co. .5 Watt resistor .5 meg. (R9).
 One Lynch Mfg. Co. .5 Watt resistor .1 meg. (R8).
 One Lynch Mfg. Co. .5 Watt resistor 5. meg. (R11).
 One Lynch Mfg. Co. 1. Watt resistor 2000 ohms. (R5).
 One Lynch Mfg. Co. 1 Watt resistor 3000 ohms (R4).
 One Frost 40 series potentiometer Cat. No. 6182 (R1) 3000 ohms.
 One Frost 40 Series Potentiometer Cat. No. 6186 (R3) 50,000 ohms.
 One Wafer Socket Type 59, 7 prong (V4).
 One Wafer Socket 5 prong Type (V3).

(Continued on next page)

A Dual Regeneration Control Set


COIL DATA

Band Meters	Grid Coil Turns	Tickler Coil Turns	Space Between 2 Coils
10-20	4 3/4 T. No. 22 Wound 6 T. per inch.	4 T. No. 31 Close wound	3/32"
20-40	10 3/4 T. No. 22 Wound 12 T. per inch.	6 T. No. 31 Close wound	3/16"
40-80	22 3/4 T. No. 22 Wound 16 T. per inch.	7 T. No. 31 Close wound	3/32"
80-200	51 3/4 T. No. 22 Wound 40 T. per inch.	15 T. No. 31 Close wound	1/8"
200-350	68 3/4 T. No. 28 Close wound	28 T. No. 36 Close wound	1/8"
350-500	131 3/4 T. No. 32 Bank wound in 2 layers.	32 T. No. 36 Close wound	1/8"

Data for Na-Ald coils form 1 1/4 inches dia. by 2 1/8 inches long (4 pin).

Parts List—Dual Control Set

- 1—antenna series condenser (about 10 to 25 mmf.) or Hammarlund equalizer, type E. C. 35.
- 1—tuning condenser Hammarlund MC 140 m. (Cap. .00014 mf.)
- 1—set S-W plug-in coils, Na-ald; (Gen-Win; Kresge; I.C.A. etc.) or other coils suited to match .00014 mf. condenser.
- 1—regen. control cond. Hammarlund MC-100M (Cap. .0001 mf.) (or National).
- 1—4 prong socket Na-ald (or Eby).
- 1—5 prong socket Na-ald (or Eby).
- 1—4 prong wafer socket for coil Na-ald (or Eby).
- 1—50,000 ohm potentiometer, Frost.
- 1—by-pass cond (for potent.) .1 mf., Flechtheim.
- 2—.00025 mf. condensers, Aerovox.
- 1—grid-leak, 5 meg., Lynch.
- 1—1/2 meg. resistor (couples grid of pentode to ground).
- 1—20 ohm rheostat, Frost.
- 1—R.F. choke, National, 2 1/2 m.h. (millihenry).

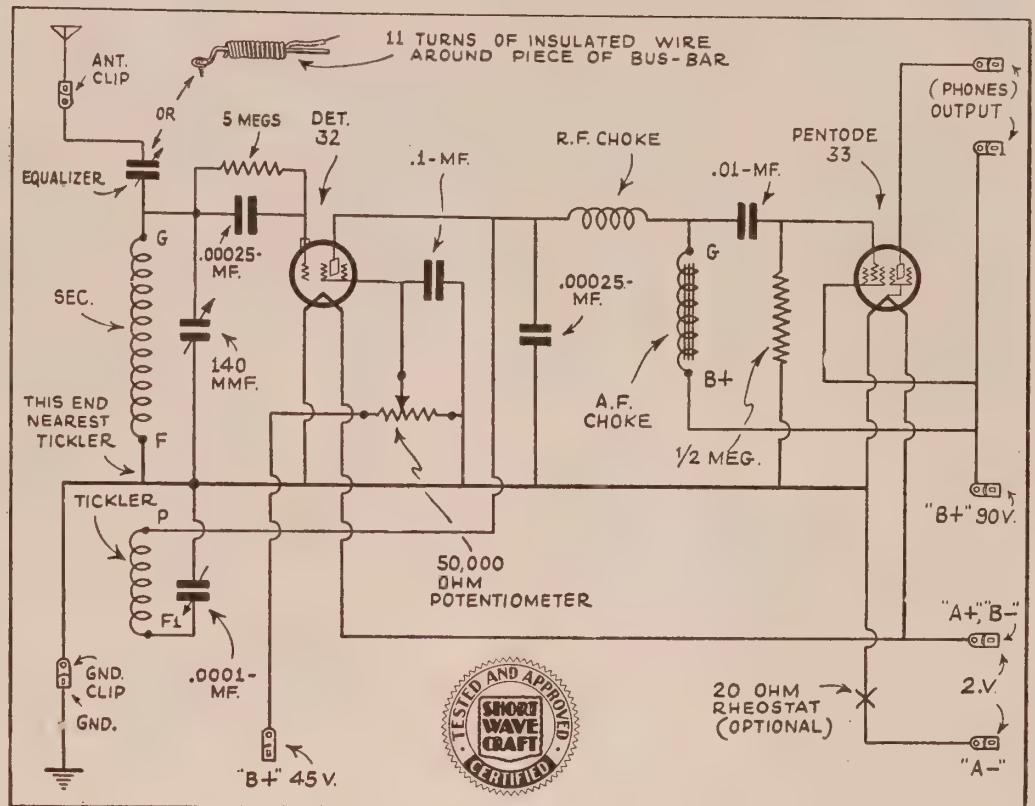

- 1—.01 mf. condenser, Aerovox.
- 1—A.F. Choke; National type S101; or Silver-Marshall A.F. transformer with sec. and prim. con. in series.
- 1—32 type 2 vt. S.G. detector tube, Triad (R.C.A. or Arcturus).
- 1—33 pentode, 2 Vt. output tube, Triad (R.C.A. or Arcturus).

Binding posts (Eby).

- 1—panel, Blan, (or Insuline Corp. of America).
- 1—pair 4000 ohm, high impedance phones, to suit pentode; Trimm "feather-weight."

—Short Wave Craft, June, 1933.

"Master Composite 4"

(Continued from preceding page)

- One Yaxley S.P.D.T. rotary jack switch (S).
- One Wafer socket and male plug for speaker.
- One Eby Ant. Ground terminal strip (T1, T2).
- One four-prong chassis mt'g plug and socket cable connector Type 7A-11 and 11A (T5, T6, T7, T8).
- Two Eby Insulated Binding Posts (for phones) (P).
- One Steel Chassis drilled and folded to specifications—Korrol Mfg. Co. or
- One Aluminum Chassis drilled and folded to specifications, Blan-the-Radio-Man.
- NOTE—The builder has a choice of chassis material.
- One Drilled panel. Aluminum panel is dipped and the steel panel is cadmium plated.

- Two Blan—The-Radio-Man, special aluminum shields for the coils.
- Two Blan—The-Radio-Man "Hand-Hole" Covers for the coil openings.
- Two Blan—The-Radio-Man flexible couplings.
- Two 6 inch lengths of bakelite 1/4 inch in diameter.
- Four small brown knobs.
- Four 5 inch lengths of 6/32 threaded brass rod.
- Two Raytheon 58 type tubes (R.C.A.).
- One Raytheon 59 type tube (R.C.A.).
- One Raytheon 56 type tube (R.C.A.).
- Wire, soldering lugs, machine screws, etc.


PARTS LIST OF THE POWER SUPPLY

- One Jefferson Power transformer, Type 463-934. (P.T.)
- Federated Purchaser Cat. No. 2532.
- Two Jefferson Filter Chokes, Type SA2071.
- Federated Purchaser No. 2503 (CH1, CH2).

- Three Flechtheim Electrolytic Condensers, 8 mf., 500 volts peak. Type JW800 (C1).
- One Flechtheim Dry Electrolytic Condenser 8 mf., 500 peak volts Type KL800 (C2).
- One Korrol Mfg. Co. Steel, cadmium plated chassis drilled and welded.
- Aluminum chassis by Blan, The-Radio-Man.
- One Federated Purchaser power switch No. 4112 (S).
- One Federated Voltage Divider Cat. No. 3915. 25,000 ohms with taps (R).
- One Five Wire Cable (Use No. 16 wire in cable if possible).
- One Rubber Grommet.
- One Four prong wafer socket. Marked 280 (80).
- One Raytheon 80 rectifier tube (R.C.A.).

—Short Wave Craft, June, 1933.

The "Wyeth All-Wave 6"

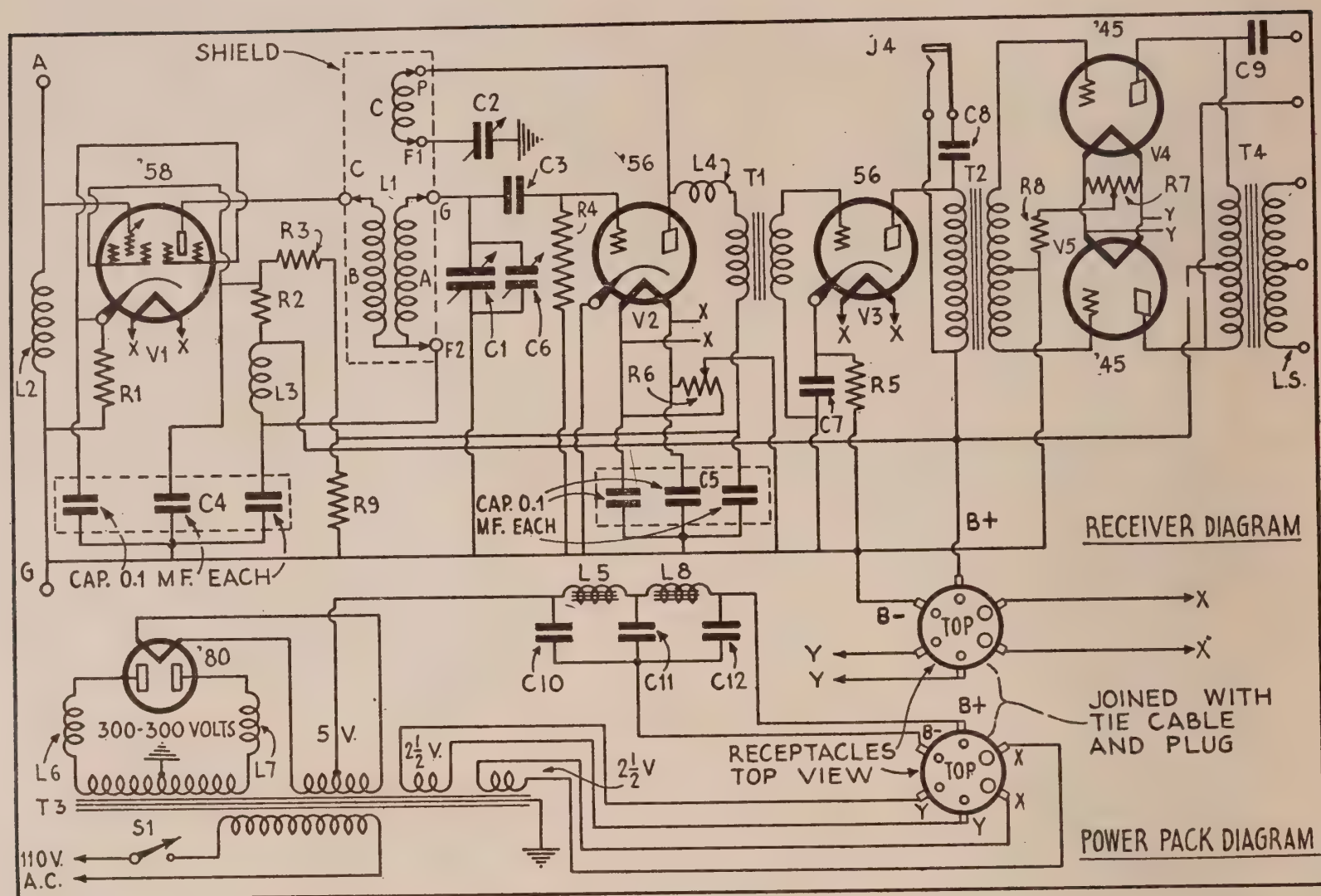

Parts List

One Wyeth receiver panel, drilled, sprayed and baked black.
 One Wyeth special size chassis 16 $\frac{1}{4}$ " by 8" by 2".
 One special aluminum shield for coil.
 One "Hand-Hole" Cover for coil opening.
 One National Dial—Type N Vernier.
 One .00014 mf. tuning condenser (C1).
 One .000075 mf. Midget condenser, (C2).
 One Hammarlund 3-plate midget condenser MC-20-8 (C6). Cap.-20 mmf.
 One .00015 mf. small moulded condenser (C3).
 Two bypass condenser banks (3-.1 mf., units in each) (C4) and (C5).
 Two tubular condensers 25 mf., 400 V. (C8) and (C9).
 One tubular condenser, 0.1 mf., 200 V., (C7).
 One 400 ohm resistor, 1 watt (R1) Lynch, (International).
 Two 8000 ohm resistors, 2 watt (R2) and (R3) Lynch, (International).
 One 4000 ohm resistor, 2 watt (R9) Lynch, (International).
 One 2 Meg. 1 watt (R4) Lynch, (International).
 One 2000 ohm, 1 watt resistor (R5), Lynch, (International).

Two 40 ohm C. T. resistors (R6) and (R7) Lynch, (International).
 One 800 ohm resistor 2 watt (R8) Lynch, (International).
 Three radio frequency chokes (L2), (L3), (L4)—85 M.H. each.
 One each of the following Short Wave Coils 131L, 131M, 131N, 131O, 131P and 131Q

(L1).
 One 1 to 3 interstage transformer (T1).
 One 1 to 2 input push-pull trans. (T2).
 One Output Transformer (optional) (T4).
 Two National Isolantite 5 prong tube sockets (V2) & Coil (L1).
 One National Isolantite 6 prong tube socket (V1).

This 6-tube all wave receiver was designed and built by an engineer who has had many years' experience in radio work. The panel of the set is $\frac{1}{8}$ " thick and allows the set to be mounted on a rack if so desired.

Coil No.	Wavelength Range in Meters	Secondary Turns. Connect to G and F2	Tickler Turns. Connect to P and F1
131L	16.6-31	6 $\frac{1}{2}$ No. 22 E.	5-2/3 No. 34 D.S.C.
131M	30-56.7	13 $\frac{1}{2}$ No. 22 E.	7-2/3 No. 34 D.S.C.
131N	55-104	25 $\frac{1}{2}$ No. 22 E.	12-2/3 No. 34 D.S.C.
131O	103-195	46 $\frac{1}{2}$ No. 24 D.C.C.	25-2/3 No. 34 D.S.C.

Coil No.	Wavelength Range in Meters	Primary Turns. Connect to C and F2	Secondary Turns. Connect to G and F2	Tickler Turns. Connect to P and F1
131P	163-343	60 No. 37 E.	82 $\frac{1}{2}$ No. 29 E.	32-2/3 No. 34 D.S.C.
131Q	273-600	60 No. 37 E.	155 $\frac{1}{2}$ No. 34 D.S.C.	55-2/3 No. 34 D.S.C.

131 P and 131 Q have three windings—primary, secondary, and tickler. The primary coil is wound on a cardboard form $1\frac{1}{8}$ inches in diameter and is secured within the secondary winding. Coil ends are brought out to the prongs as shown in wiring diagram.

Short Wave Craft, Nov., 1933.

—*Short Wave Craft, Dec., 1931.*

The "19" Twinplex

Parts List

L1, L2—Octo-Coil Short Wave Coils, 15-200 meters.

C1—Equalizing condenser 3-35 mmf. EC-35; Hammarlund (National, Cardwell).

C2—Isolantite midget condenser, 140 mmf., MC-140-M; Hammarlund (National; Cardwell).

C3—.0001 mf. moulded mica condenser.

C4, C7—.5 mf. tubular mica condenser, 200 DCWV.

C5—.01 mf. tubular by-pass condenser, 200
DCWV.

C6—.0005 mf. moulded mica condenser.

R1—3 meg. metallized resistor; Lynch.

R2—400 ohm metallized resistor; Lynch.

R3—20 ohm rheostat or Amperite 2H-1.

R4—0.25 meg. metallized resistor

R5—100,000 ohm resistor; Lynch.

R6—50,000 ohm potentiometer; Acratest.

1—Aluminum panel, 7"x5"x1/16"; Blan.

1—Alum
Blan.

1—3" vernier dial; National.

1-4-prong isolantite socket; Hammarlund (National).

1—6-prong wafer socket; Alden.


1—Ant.-ground binding post strip.

1—Twin speaker jack assembly.

1—Type "19" tube RCA (Arco).

Operating Hints

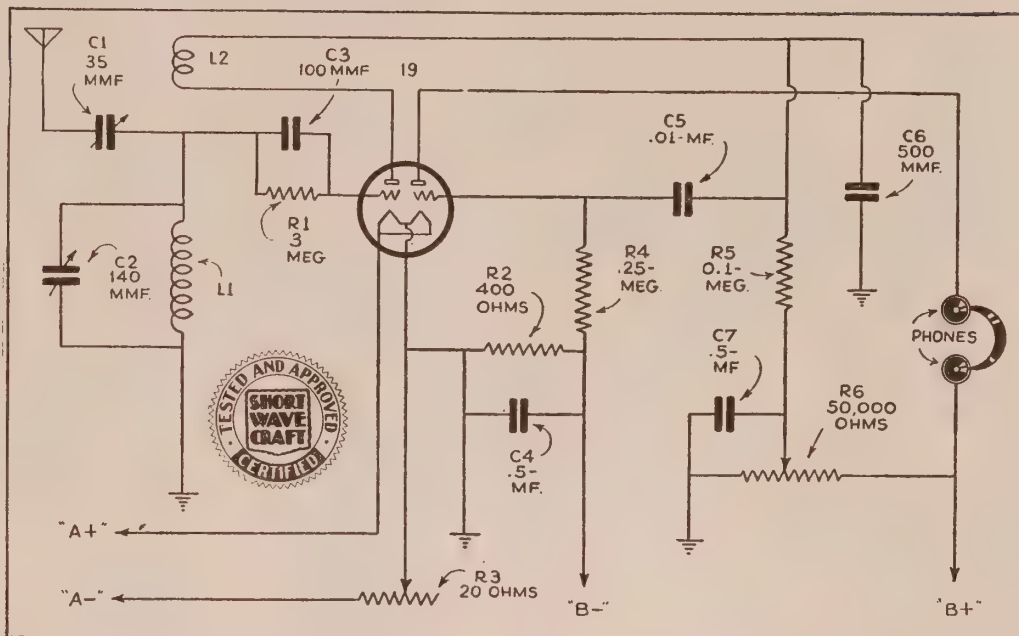
When putting the set into operation the "A" battery should be such that the fila-



ment voltage at the tube socket, is two volts. The potentiometer should be adjusted until the circuit goes into oscillation. When oscillation starts a pronounced thud generally occurs and pronounced clicks will occur when the ungrounded terminal of the

tuning condenser is touched with the finger. It will generally be found advisable to re-adjust the antenna condenser each time a coil is changed.

—*Short Wave Craft, March, 1934.*

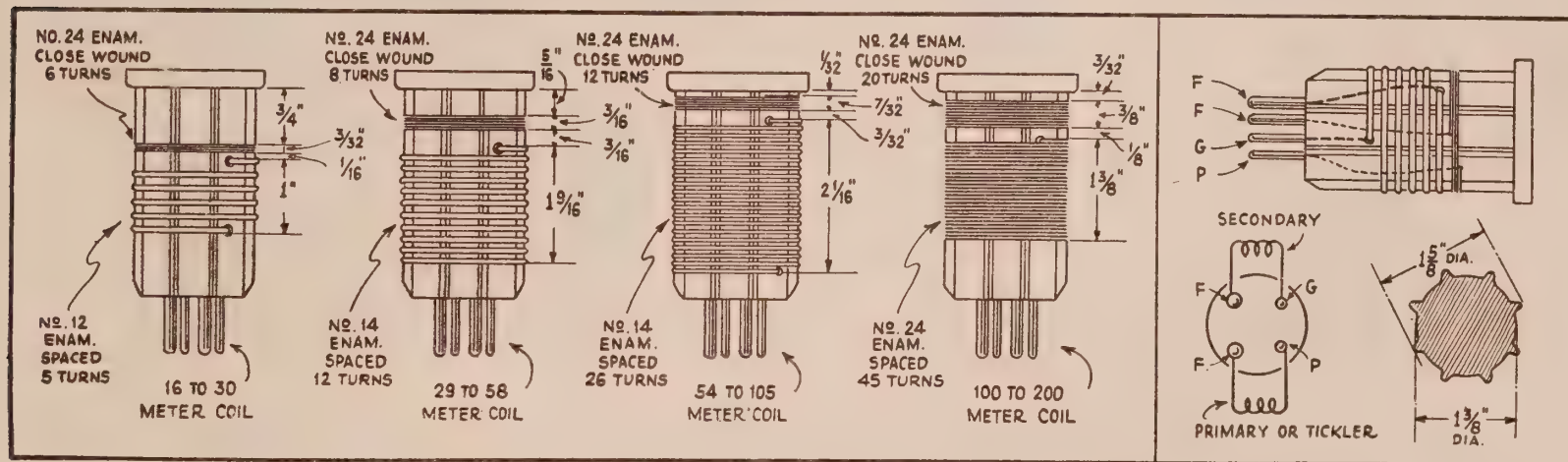


A 4-Tube "Doerle" Set

Constructional Data


This is a 4 tube model of the famous Doerle receiver employing battery tubes. Standard coils may be used with this receiver. A type 33 pentode is used in the output stage to insure good loudspeaker reception. The filament rheostat may be replaced by an Amperite, type 4-1.

This set is capable of giving very fine results when carefully constructed.

**Wiring Diagram for a
4 tube Doerle which
gives excellent results.**

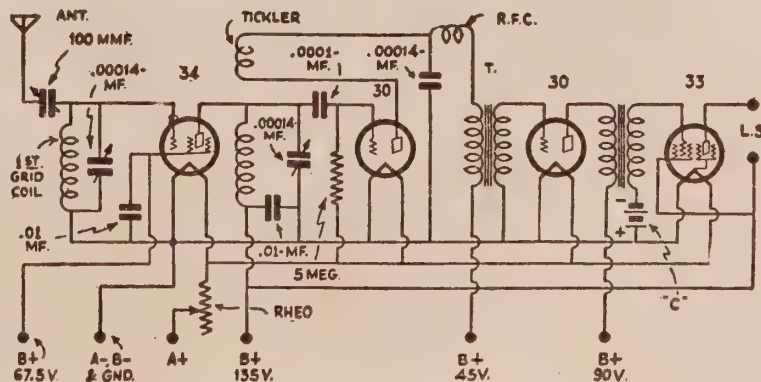

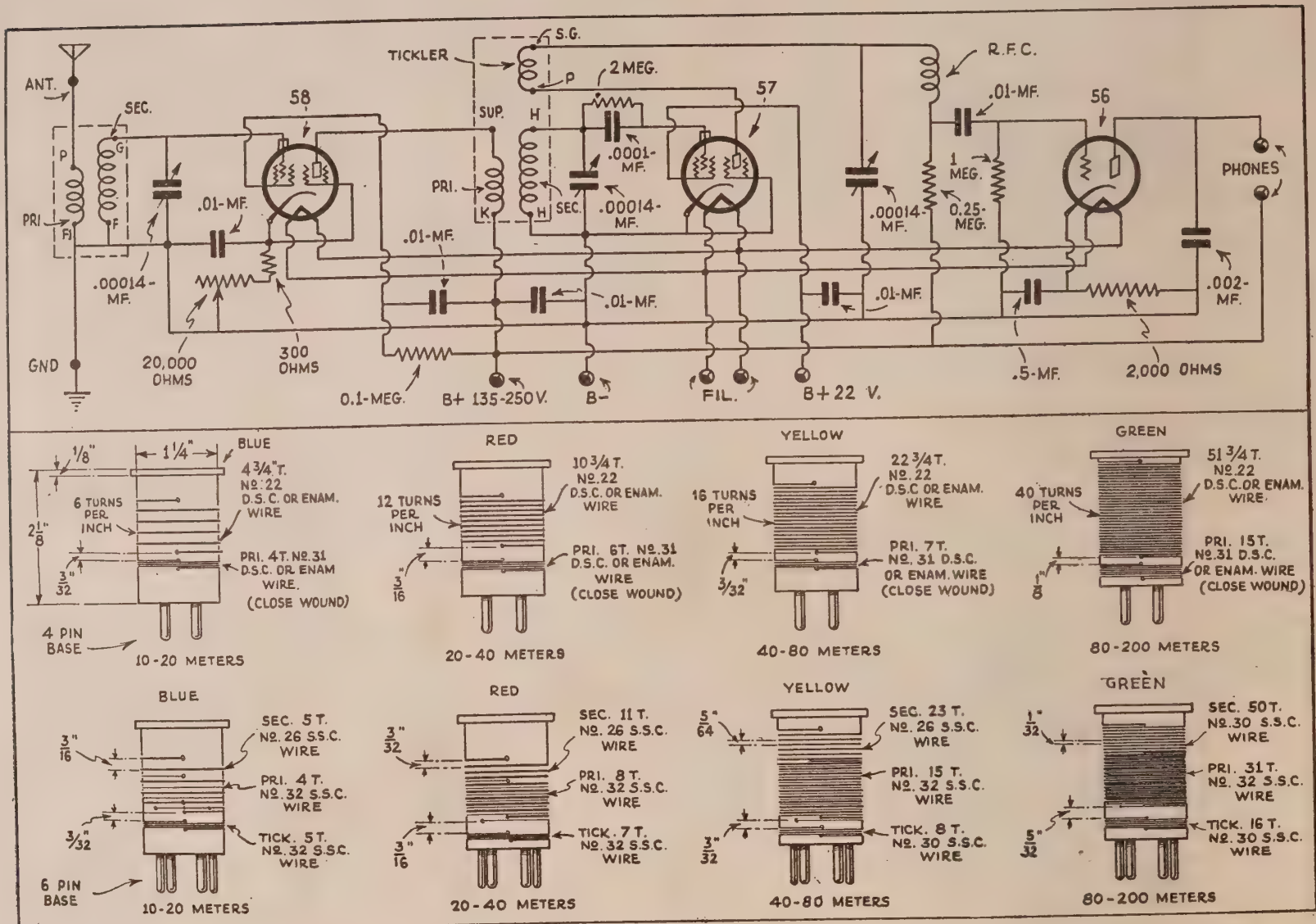Doerle 3-Tube "Signal Gripper" Electrified



The set is truly a wonderful short wave receiver. Foreign short-wave stations can be brought in loud enough to operate a speaker even with only a triode (3-element tube) used in the output stage. If a pentode were used greater volume would be obtained, but then head-phones would be out of the picture, and the author just can't seem to break away from phones, which are really the best for "DX" short-wave reception.

This receiver can be operated from various sorts of power supply arrangement and is adaptable to any location whether A.C. power is available or not. For those having A.C. power it is suggested that this set be run from a regular power supply, delivering from 180 to 250 volts with a 2.5 volt filament winding. A 22 volt tap will be required for the screen of the detector tube, of course. It might be well to state here that the voltage applied to the screen should not exceed 22 volts under any consideration, because the sensitivity of the receiver will be very much affected by running the screen at a higher potential. Also the regeneration control will operate smoothly if the voltage is not

of this value. If one wishes to operate this set from batteries it can be done very nicely with no change in the circuit. It's just a matter of changing the tubes to the automobile type and running them from a six-volt storage battery and using "B" batteries for the plate supply. 135 volts will work very nicely, although higher voltage is recommended if full signal strength is to be had. For operating on a regular power supply from 110 volts A.C., a 58 will be needed for the tuned R.F. stage, a 57 for the detector, and a 56 as the output tube. When operating from a storage battery with "B" batteries for the plate supply, a 6D6 will be used for the R.F. tube, a 6C6 for the detector and a 76 for the audio tube.

List of Parts for the "Doerle" 3-Tube A.C. Receiver

- 1—Drilled Metal Chassis, Radio Trading Co.
- 1—R.F. Choke Coil, Radio Trading Co.
- 1—Set of 4 Special Three-Winding Coils, Radio Trading Co.
- 1—Set of 4 Regular Doerle Coils, Radio Trading Co.

- 5—.01 mf. Fixed Condensers, Flechtheim.
- 1—.002 mf. Fixed Condensers, Flechtheim.
- 1—.5 Bypass Condenser, Flechtheim.
- 1—300 Ohm Resistor.
- 1—100,000 Ohm Resistor, Lynch.
- 1—250,000 Ohm Resistor, Lynch.
- 1—1 Megohm Resistor, Lynch.
- 1—2 Megohm Resistor, Lynch.
- 1—2,000 Ohm Resistor, Lynch.
- 1—2,000 Ohm Resistor, Variable.
- 3—Six Prong Sockets, Eby (National; Hammarlund; Na-ald).
- 1—Five Prong Socket, Eby (National; Hammarlund; Na-ald).
- 1—Four Prong Socket, Eby (National; Hammarlund; Na-ald).
- 2—Triple-Grid Tube Shields, Hammarlund (National).
- 1—.0001 Fixed Condenser, Flechtheim.
- 3—Hammarlund .00014 mf. Tuning Condensers.
- 2—Tuning Dials, National or other make.
- 1—Antenna Ground Terminal Strip, Eby.
- 1—Phone Terminal Strip, Eby.
- 1—Five Wire Cable.


—Short Wave Craft, Aug., 1933.

The “Clip Coil Two” Rolls ‘Em In!


Parts List "Clip-Coil" Set

- 1—Panel and Baseboard.
- 1—Special "Clip-Coil" (see drawing for data). Gen-Win.
- 1—.00025 mf. Variable Condenser. National (Hammarlund).
- 1—.0001 mf. Mica Condenser. Polymet.
- 1—.0005 mf. Mica Condenser. Polymet.
- 1—3 megohm Grid-Leak, ½ watt. Lynch.
- 1—.5 mf. By-Pass Condenser. Polymet.
- 1—500,000 ohm potentiometer.
- 1—3:1 ratio Audio Transformer.
- 2—4-prong Tube Sockets.
- 1—Antenna Ground Terminal Strip.
- 1—Phone Terminal Strip.
- 1—2.5 mh. R.F. Choke. National (Hammarlund).
- 2—230 RCA Radiotrons (Arco).

Short Wave Craft, July, 1934.

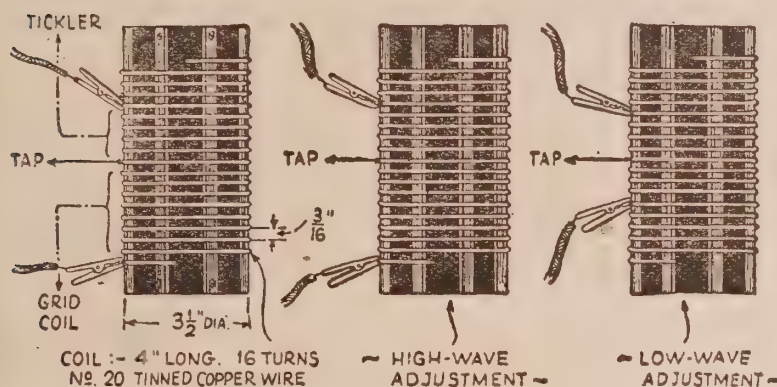

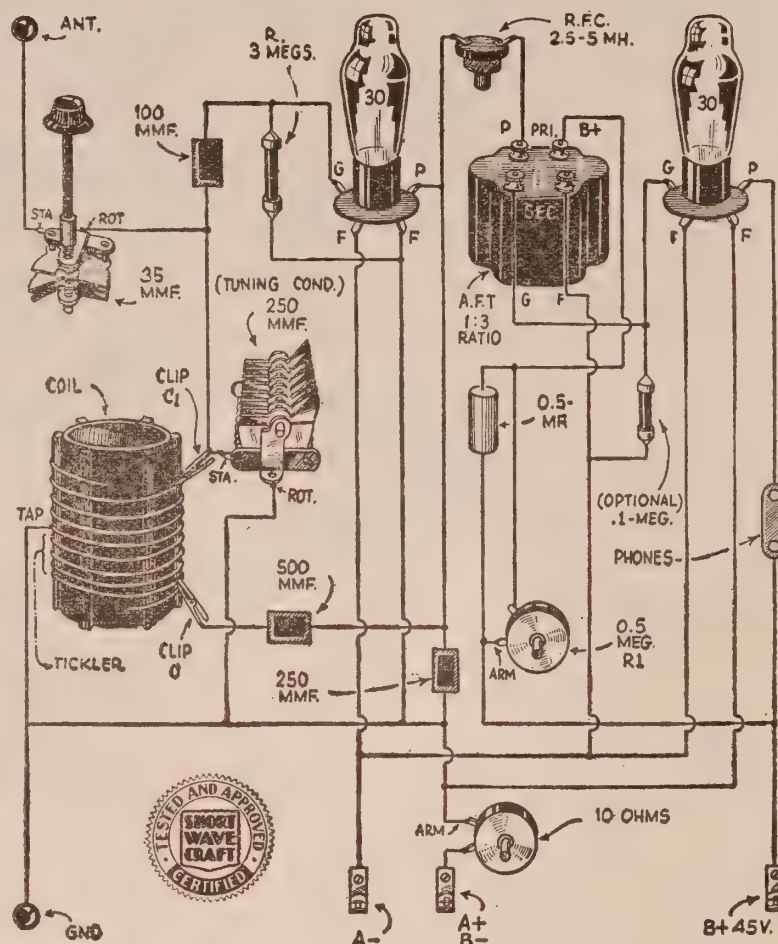
Coil winding details for the "Clip Coil Two"



The DOERLE Goes “Band-Spread”

PARTS LIST—2-TUBE DOERLE BAND- SPREAD


- 1—set of Na-Ald “band-spread” coils.
- 1—drilled metal chassis. Radio Trading Co.
- 2—140 mmf. variable tuning condensers. Hammarlund. (National; I.C.A.).
- 1—antenna trimmer (low min. cap.) 35 mmf max.
- 1—.0001 mf. mica condenser. (Polymet.)
- 1—.01 mf. bypass condenser. I.C.A. (Polymet.)
- 1—.02 mf. bypass condenser. I.C.A. (Polymet.)
- 1—.002 mf. bypass condenser. I.C.A. (Polymet.)
- 1—20 to 25 mf. 25-volt electrolytic condenser. (Polymet.)
- 1—2 meg. grid-leak. Lynch.
- 1—1 meg. grid-leak. Lynch.
- 1—250,000 ohm resistor. Lynch.
- 1—2,000 ohm resistor. Lynch.
- 1—50,000 ohm variable potentiometer. Acratest. (I.C.A.)
- 1—2.5 to 5 mh. R.F. choke. National (Hammarlund; I.C.A.)
- 1—5-prong wafer socket. Na-Ald. (I.C.A.)
- 2—6-prong wafer-socket. Na-Ald. (I.C.A.)
- 1—antenna-ground terminal strip. I.C.A.
- 1—phone terminal strip. I.C.A.
-

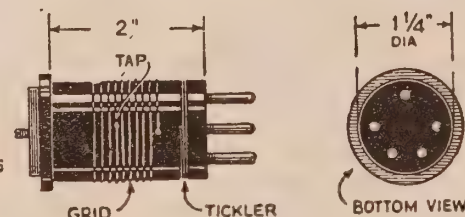

- 20 METER COIL: GRID, 4 1/2 T. NO. 24 WIRE TAPPED AT
1 1/4 T. LENGTH OF WINDING 7/8". TICKLER,
5 T. NO. 30 WIRE CLOSE WOUND.
- 40 METER COIL: GRID, 11 1/2 T. NO. 24 WIRE TAPPED AT
4 1/2 T. LENGTH OF WINDING 1". TICKLER,
7 T. NO. 30 WIRE CLOSE WOUND.
- 80 METER COIL: GRID, 26 1/2 T. NO. 24 WIRE TAPPED AT
13 T. LENGTH OF WINDING 1 1/8". TICKLER,
8 T. NO. 30 WIRE CLOSE WOUND.
- 160 METER COIL: GRID, 52 1/2 T. NO. 28 WIRE TAPPED AT
32 T. LENGTH OF WINDING 1 3/8". TICKLER,
17 T. NO. 30 WIRE CLOSE WOUND.
- 1-5-wire battery cable. I.C.A.
1-57 tube, R.C.A. (Arco).
1-2A5 tube, R.C.A. (Arco).

—*Short Wave Craft, May, 1984.*

This 3-Tube "Super" Has "IT"

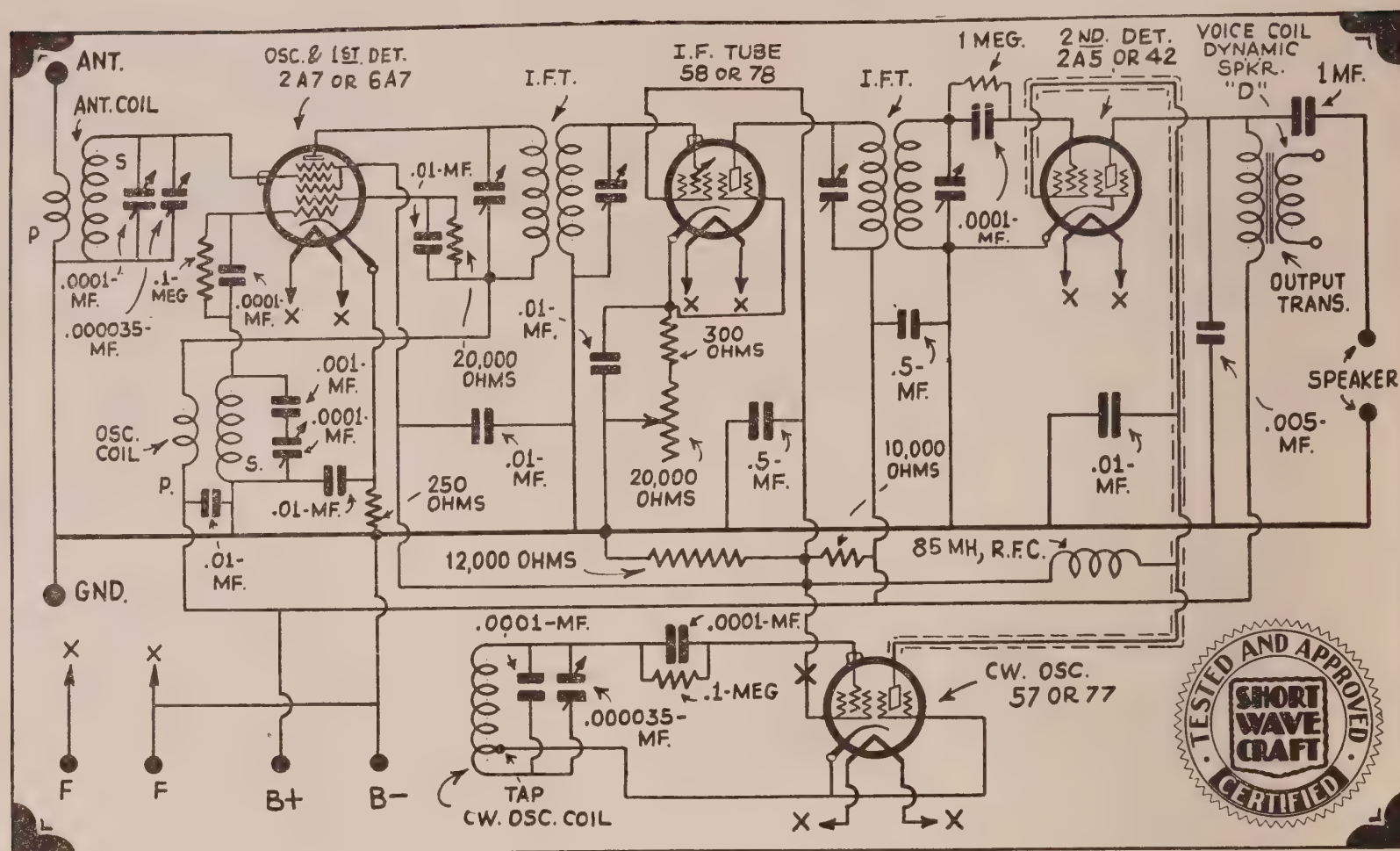

Coil Winding Table

Make two of the following

COIL	Tickler or antenna	GRID
No. 1—	4 turns No. 34 wire	5 turns No. 26 wire
No. 2—	5 turns No. 34 wire	10 turns No. 26 wire
No. 3—	8 turns No. 34 wire	24 turns No. 26 wire
No. 4—	10 turns No. 34 wire	45 turns No. 26 wire

All coils close-wound, Diameter of form $1\frac{1}{2}$ inch.

The above coils cover all of the popular S. W. broadcast and Amateur bands.

Any standard commercial SW coils will work if designed for 100 mmf. condensers. Otherwise change tuning condensers to match coils that are designed to work with 140 mmf. condensers.

Spacing between grid coils and tickler or antenna coil is $\frac{1}{4}$ inch.

Parts List—Shuart 3-Tube Superhet

- 1—8x12x1 Inch Chassis 1/16 in. Blan.
- 1—7x12 Inch Panel 1/16 in. Blan.
- 1—drum dial—National.
- 1—100 mmf. Variable Condenser, Clockwise, National—270°.
- 1—100 mmf. Variable Condenser, Counter Clockwise, National—270°.
- 2—35 mmf. Variable Condensers, Hammarlund.

- 8—5 Prong coil forms, small Hammarlund.
- 2—National Isolantite sockets (5 prong).
- 1—National Isolantite socket (7 prong).
- 2—National "Airtuned" IF. Transformers
- 3—Tube shields, Hammarlund.
- 3—6 prong tube sockets, wafer, Eby.
- 2—.5 MF Bypass condensers.
- 1—.5 MF Bypass condenser.
- 7—.01 MF. Bypass condensers.
- 3—.0001 MF. Mica grid cond.
- 1—22,000 ohm voltage divider, tapped at 12,000.
- 2—100,000 ohm resistors—1 watt, Lynch (International).
- 1—20,000 ohm resistor—1 watt, Lynch, (International).
- 1—300 ohm resistor—1 watt, Lynch, (International).
- 1—250 ohm resistors—1 watt, Lynch (International).
- 1—1 meg. resistor—1 watt, Lynch (International).
- 1—20,000 ohm Volume control, Acratest.
- 1—Antenna-Ground binding post strip, Eby.
- 1—Speaker binding post strip, Eby.
- 1—4 wire cable.
- 1—2A7 or 6A7 tube, Gold Seal.

- 1—2A5 or 42 tube, Gold Seal.
- 1—58 or 78 tube, Gold Seal.
- 1—57 or 77 tube, Gold Seal.


Tube Line-up

The line-up of the tubes is as follows: the 2A7 is used as the frequency converter, a type 58 for the intermediate frequency amplifier, and a type 2A5 as the second detector tube. The type 2A5 used as the second detector gives sufficient audio amplification to operate a speaker, either magnetic or dynamic, at regular speaker volume. That is, any of the major shortwave stations can be heard all over the house and one does not have to stand with one's ear in the speaker either. The fourth tube, the type 57, is the beat oscillator tube and plays no part in the reception of broadcast (phone) reception, other than to aid in tuning or locating the station. The coils used in this receiver are very easy to construct; they are all close-wound and the two sets, that is, the first detector and the oscillator coils are identical in number of turns. The coils used in the set shown are wound on small isolantite forms. Complete coil data is given in the appended "Coil table."

—Short Wave Craft, Sept., 1933.

The Denton S-W Plugless Superheterodyne


CLIFFORD E. DENTON

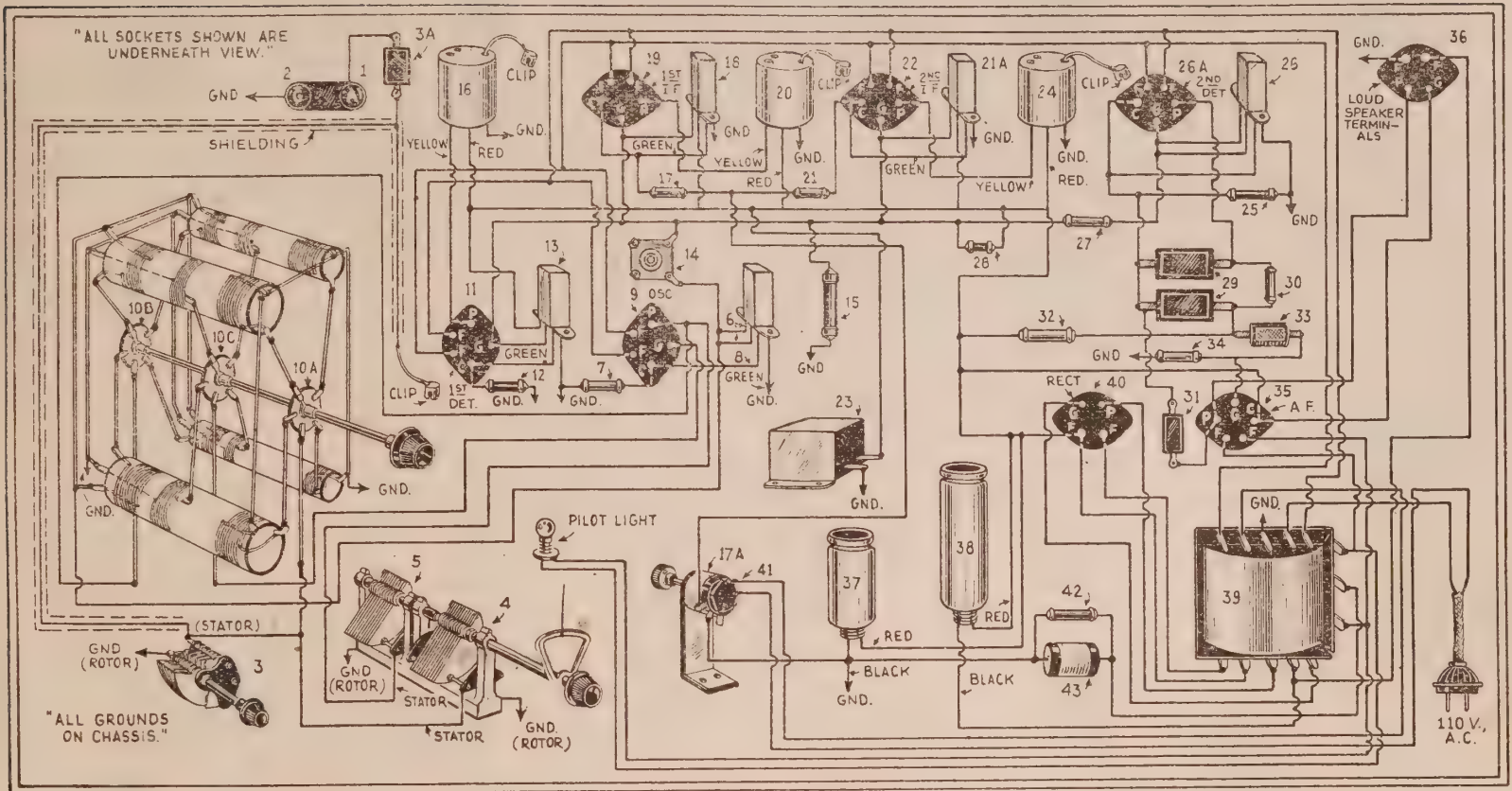


Parts List for Super-het

- 1—Eby Antenna Ground Post (1, 2)
 - 1—Best S.W. C.1 kit (10A, 10B, 10C) coil and switch assembly.
 - 2—National tuning condensers (4, 5).
 - 1—Pilot 80 mmf. trimming condenser (3).
 - 8—Eby wafer sockets marked for tubes (9, 11, 19, 22, 26A, 35, 36, 40).
 - 5—Blan .1 mf. by-pass condensers, 2 in each can (6, 8, 13, 18, 21A, 26).
 - 1—Electrad volume control and fil. switch R1-202-P (17A, 41).
 - 1—International or Lynch resistor, 2500 ohms, 1 watt (7).
 - 1—International or Lynch resistor, 10000 ohms, 1 watt (15).
 - 1—International or Lynch resistor, .1 meg., 1 watt (32).
 - 1—International or Lynch resistor, .5 meg., 1 watt (34).
 - 2—International or Lynch resistors, 500 ohms, 1 watt (17, 21).
 - 2—International or Lynch resistors, 25000 ohms, 1 watt (12, 25).
 - 3—International or Lynch resistors, 10000 ohms, 1 watt (30, 15, 27).
 - 1—International or Lynch resistor, 416 ohms, 1 watt, (42).
 - 1—International or Lynch resistor, 50000 ohms, 1 watt (28).
 - 3—Acratest 465 K.C. I.F. transformers (16, 20, 34).
 - 1—Blan R.F. choke (14).
 - 1—Flechtheim Filter Condenser 2 mf. 450 volts (23).
 - 1—Sprague midget condenser .04 mf. (83).
 - 2—Aerovox .000125 mica condensers (29).
 - 1—Aerovox .001 mica condenser (31).
 - 4—Hammarlund tube shields.
 - 1—Acratest power transformer 2532 (39).
 - 2—Acratest Electrolytic condensers (1-8 mf. No. 5308 and 1-4 mf. No. 5304) (37, 38).
 - 1—Blan chassis and volume control m.t.g. bracket, completely drilled and folded.
 - 1—Crowe "full vision" dial and light holder.
 - 1—G.E. power cord and plug.
 - 1—Acratest 25 volts, 25 mf. No. 6646 (43).
 - 1—Raytheon 280 tube.
 - 1—Raytheon 247 tube.
 - 2—Raytheon 224 tubes.
 - 2—Raytheon 224 tubes.
 - 2—Raytheon 235 tubes.
 - 1—Raytheon 227 tube.
 - 1—loud-speaker with output transformer for '47 pentode, with 1800 ohm field.
 - 1—Blan 4 wire plug and beads for speaker cable.
- In the event that the builder wishes to use an ordinary loud-speaker, he may procure a pentode output transformer having a secondary of low impedance to match the average speaker.

—June, 1932, Short Wave Craft.

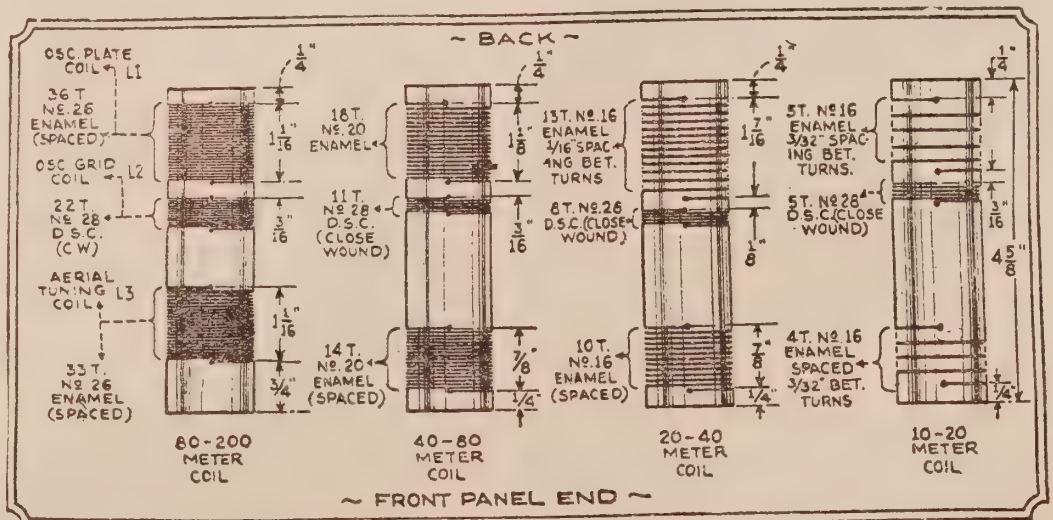

The "Globe-Girdler 7"

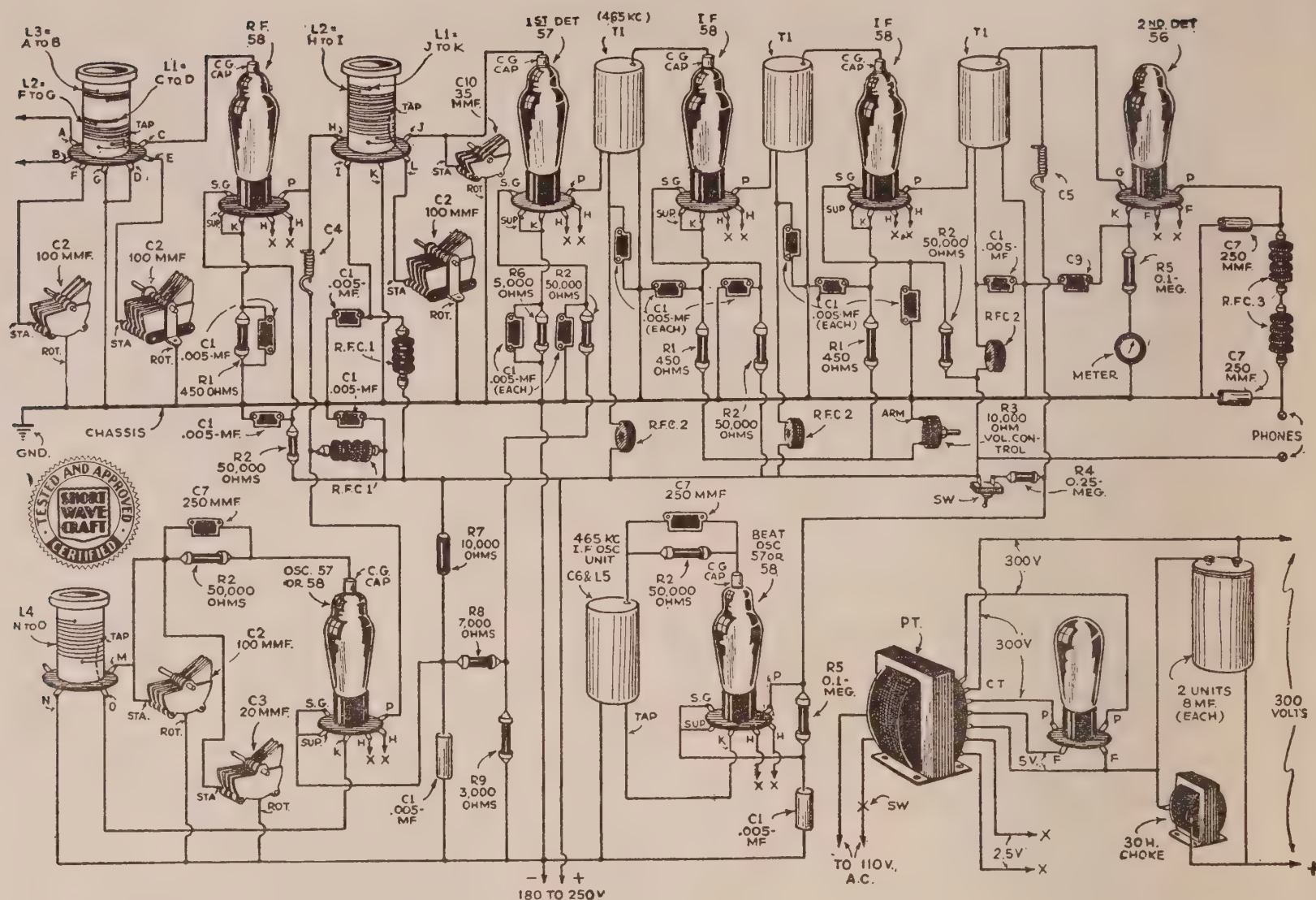

Parts List

- 15—(C1) .005 mf. fixed condensers.
 3—(C2) .0001 mf. midget variable condensers, National, (Hammarlund).
 2—(C3) 20 mmf. variable midget condensers, National, (Hammarlund).
 C4, (C5) Special condensers—see text.
 1—(C6) padding condensers of I.F. transformer.
 4—(C7) .00025 mf. mica condensers.
 2—(C8) 8 mf. electrolytic condensers.
 1—(C9) 1 mf. paper by-pass condenser.
 1—(C10) 35 mmf. Hammarlund No. 35 condenser.
 3—(R1) 450 ohm, 1 watt resistors (R1), Lynch, (International).
 6—(R2) 50,000 ohm, 1 watt resistors, Lynch, (International).
 1—(R3) 10,000 ohm volume control, Acra-test, (R. T. Co.).
 1—(R4) 250,000 ohm ½ watt, Lynch, (International).
 2—(R5) 100,000 ohm, ½ watt resistors, Lynch, (International).
 1—(R6) 5000 ohm, ½ watt, Lynch, (International).
 1—(R7) 10,000 ohm, 1 watt resistor.
 1—(R8) 7000 ohm, 1 watt resistor, Lynch, (International).
 1—(R9) 3000 ohm, Lynch, (International).
 1—(RFC1) National R.F. Choke, 2.5 M.H.
 3—(RFC2) Hammarlund SPC. 10 M.H.

- 2—(RFC3) 800 turn "universal" wound, 85 MH.
 3—(T1) 465 kc. I.F. transformers, National, (Hammarlund), Gen-Win.
 2—National drum dials.
 2—Coil forms, National.
 6—6-prong sockets, National.
 1—5-prong socket, National.
 6—Tube shields, National.
 2—Coil sockets 6 prong, National.
 1—Coil socket, 5 prong.
 1—Power transformer 300-0-300, 5V, 2.5 V., National, (R. T. Co.).
 1—4-prong socket for 280, National.
 1—30 henry filter choke (60 ma.), National, (R. T. Co.).
 4—Type 58 tubes, R. C. A. (Arco).
 2—Type 57 tubes, R. C. A., (Arco).
 1—Type 56 tube, R. C. A., (Arco).
 1—Type 80 tube, R. C. A., (Arco).

L1—is tapped for band spread; as the tap is taken off nearer the ground end of the grid coil, the band-spreading increases. About ⅓ distance from the ground end gives best results. L4, the local oscillator coil, is tapped to obtain oscillation; this tap should be taken off ⅓ the distance from the ground end of the coil. L5 is made from one of the coils removed from an old 465 KC. I.F. transformer. Remove about 30 turns; solder on a tap at this point and wind back the wire previously removed. This coil should be connected into the cir-

cuit so that the tap at 30 turns is brought next to the grounded end of the coil.

The RF chokes and IF transformers should be good ones. The chokes arrived at were found the best possible and the IF transformers used have large coils and the smallest padding condensers conveniently possible. It is admitted that mica is inferior to air for dielectric but if one manages to use a minimum of mica in the padding condensers, i.e., two plates separated by one sheet of mica, there will be approximately one-fourth the possible variation where four plates separated by two sheets of mica are used.


The beat oscillator plate lead, shielded except for about one and one-quarter inches on one end, is coupled to the grid of the 56 detector by wrapping the unshielded portion around the grid lead of the 56 2nd detector. This method of coupling is very effective and the strongest C.W. signal can be heterodyned. (This is C4, C5 on the diagram.)

COIL DATA

	80 M.	40 M.	20 M.
L1	30T.	13T.	6T. (tapped)
L2	20T.	8T.	4T.
L3	8T.	5T.	4T.
L4	20T.	12T.	5T. (tapped)
L5	(see text)		

—Short Wave Craft, Feb., 1934.

The "Rex" Portable Super-het

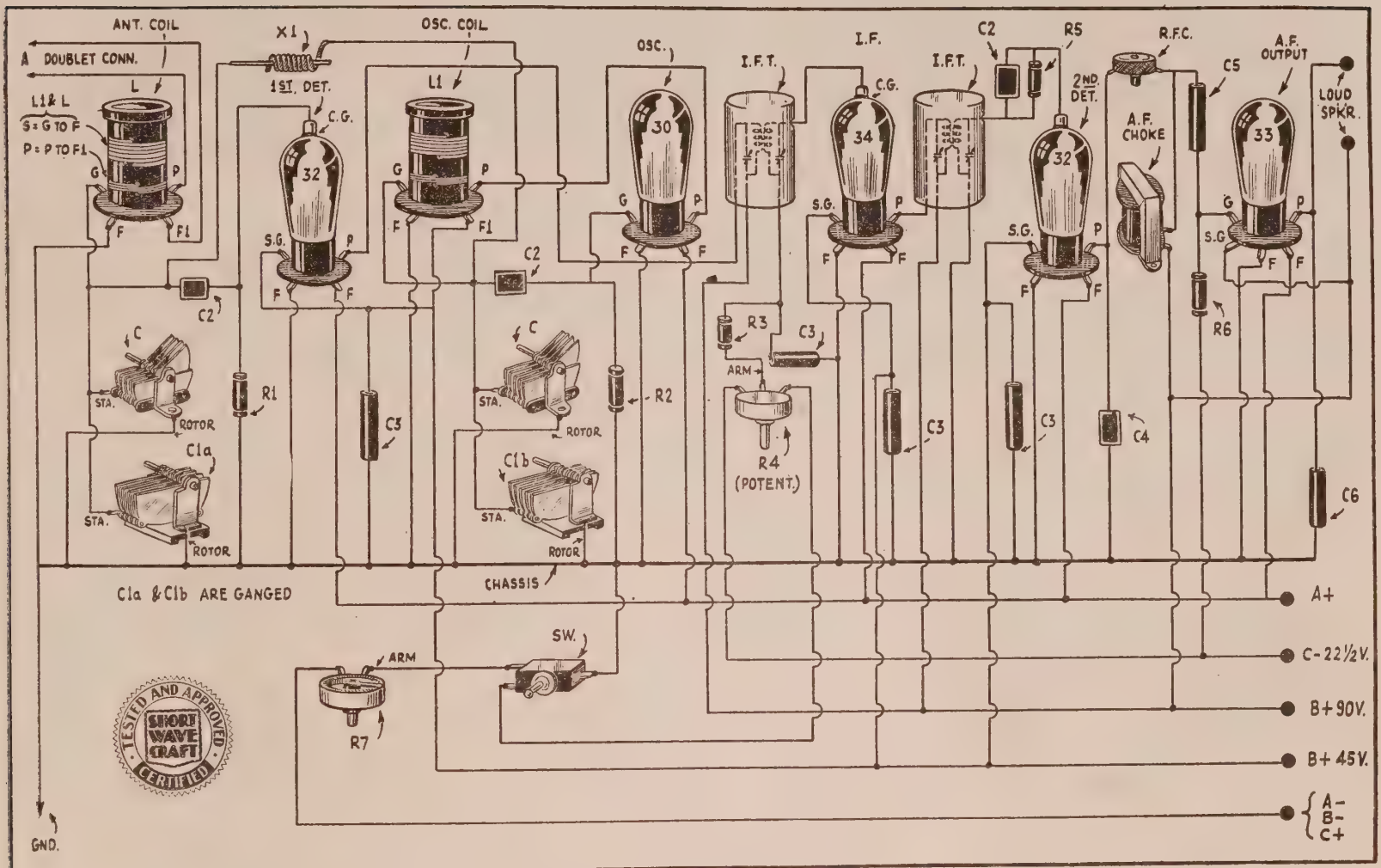

Plug-In Coil Data

Meters Wave-length	Grid coil turns	Tickler turns	Distance between 2 coils
200-80	52 T. No. 28 En. Wound 32 T. per inch	19 T. No. 30 En. Close wound (CW)	1/8"
80-40	23 T. No. 28 En. Wound 16 T. per inch	11 T. No. 30 En. C. W.	1/8"
40-20	11 T. No. 28 En. 3-32" between turns	9 T. No. 30 En. C. W.	1/8"
20-10	5 T. No. 28 En. 3-16" between turns	7 T. No. 30 En. C. W.	1/8"

Coil form—2 3/8" long by 1 1/4" dia. 4-pin base.

"REX" Portable Superhet

2 sets of Alden plug-in SW 2-Winding coils (L, L1).

1—Hammarlund 35 mmf. dual cond. (C1).

2—Hammarlund 100 mmf. cond. (C).

2—Hammarlund 465 kc. I.F. trans. (IFT).


3—Acratest .0001 mf. mica condensers (C2).

4—Tubular cond. .01 mf. (C3).

1—Acratest .00025 mica cond. (C4).

1—Tubular cond. .015 mf. (C5).

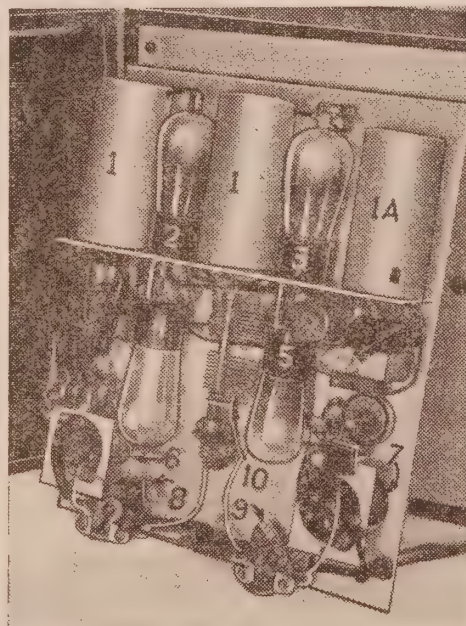This portable super-het employs two volt battery tubes. Band-spread is included among other features and economy is assured by the use of five tubes.




Rear View of "Rex" Chassis.

- 1—Acratest .002 mf. mica cond. (C6).
- 2—32 type wafer sockets, Eby (Na-ald).
- 1—30 type wafer sockets, Eby (Na-ald).
- 1—33 type wafer sockets, Eby (Na-ald).
- 1—34 type wafer sockets, Eby (Na-ald).
- 2—plain 4 prong wafer sockets, Eby (Na-ald).
- 1—Acratest 3 meg. 1/2 watt resistor (R1).
- 2—Acratest 1 meg. 1/2 watt resistor (R5, R6).
- 2—Acratest 5 meg. 1/2 watt resistor (R2, R3).
- 1—"dual" circuit-closing toggle switch (S).
- 1—Acratest 6 ohm rheostat (R7).
- 1—Acratest potentiometer, 50,000 ohm (R4).
- 1—Acratest 800 henry choke (A. F. C.).
- 1—5" diameter magnetic loud speaker; 7000 ohms impedance.
- 1—carrying case.
- 2—Special panels: Aluminum (drilled as per drawings)
- 1—special hardware kit.
- 1—National 3" vernier dial.
- 4—1" small black knobs.
- Wire, soldering lugs, etc.


—Short Wave Craft, Oct., 1933

A South American 7-Tube Super-Het.

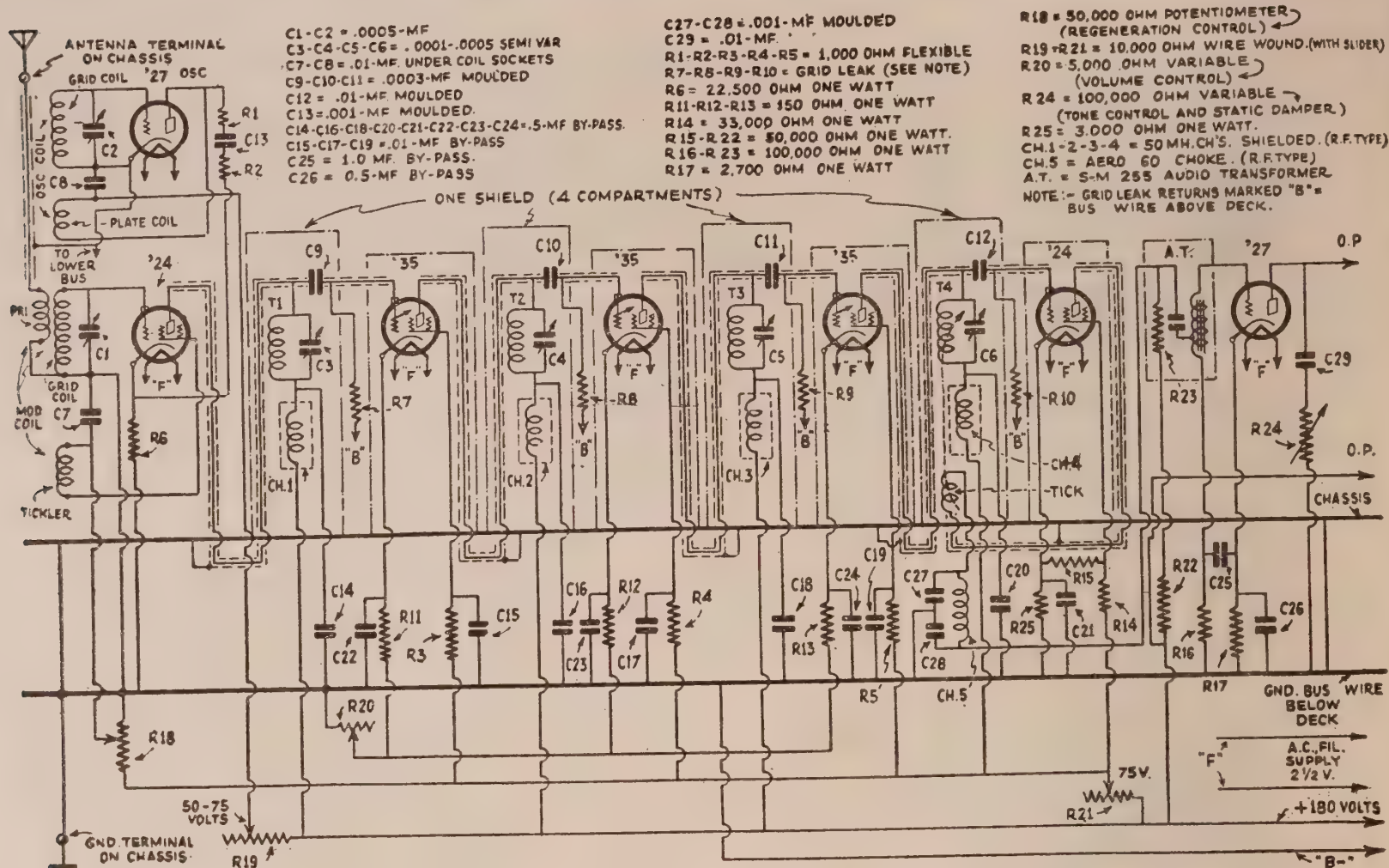

List of Parts for the Baldwin All-Wave Superhet

- 1—Chassis of copper, brass or aluminum, measuring 20.5" long, 11.75" wide, and 2" deep. Blan, the Radio Man.
- 1—aluminum, brass, or copper shield with four compartments, or four separate shield cans. Single shield measures 14" long, 3.5" wide, 5" high, inside dimensions. If separate shield cans are used (either round or square may be employed) they should measure 3.5" in diameter by 5" high. Blan.

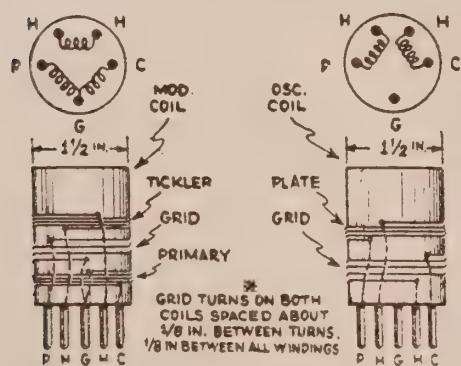


MOD. COIL				OSC. COIL			
COIL	TICKLER	GRID	PRI.	COIL	—	GRID	PLATE
1	4 1/2	5 1/2	6	1	—	2 3/4	4
2	5 1/2	5 1/2	12	2	—	7 3/4	6
3	6 1/2	8 1/2	16	3	—	26	24
WIRE	NO. 32 ENAM.	NO. 28 S.S.E.	NO. 32 ENAM.	WIRE	—	NO. 28 S.S.E.	NO. 32 ENAM.

- 4—I.F. tuned impedances 465 kc. standard I.F. transformers may be used by removing one of the coils in each unit, and placing a small coil for the tickler near the I.F. coil in unit No. T4; number of turns given in text.
- 2—sets of plug-in coils for modulator or first detector and oscillator, wound as described in the text and also illustrated in special coil drawing.
- 1—"plate" and "heater" current supply, utilizing separate 2 1/2 volt transformer, if desired, with 180 volt plate supply taken from a well-filtered "B" power-pack.
- 2—.0005 mf. tuning condensers, Hammarlund (National).
- 4—.0001 to .0005 mf. semi-variable condensers "XL" type, G5.
- 7—.01 mf. moulded condensers.
- 3—.001 mf. moulded condensers.
- 3—.0003 mf. moulded condensers.
- 9—.5 mf. by-pass condensers.
- 1—1 mf. by-pass condenser.
- 5—1,000 ohm flexible resistors.
- 4—grid leaks; R7—20,000 ohms; R8—125,000 ohms; R9—125,000 ohms; R10—1 megohm (one million ohms). Lynch.
- 1—22,500 ohms one watt resistor, R6. Lynch.
- 3—150 ohm one watt resistors, R11, 12, and 13. Lynch.
- 1—33,000 ohm one watt resistor, R14. Lynch.
- 2—50,000 ohm one watt resistors, R15, 22. Lynch.
- 2—100,000 ohm one watt resistors, R16, 23. Lynch.
- 1—2,700 ohm one watt resistor, R17. Lynch.
- 1—50,000 ohm potentiometer, R18, regener-

- ation control. Clarostat.
- 2—10,000 ohm Electrad wire-wound resistors (with sliders), R19, R21.
- 1—5,000 ohm variable resistor, R20, volume control, Frost (Clarostat).
- 1—100,000 ohm variable resistor (R24, tone control and static damper), Frost (Clarostat).
- 1—3,000 ohm one watt resistor, R25. Lynch.
- 4—50 millihenry R.F. chokes, shielded type, Hammarlund (Gen-Win).
- 1—60 millihenry R.F. choke, Aero or other type, such as Hammarlund or National (Gen-Win).


(Continued on next page)

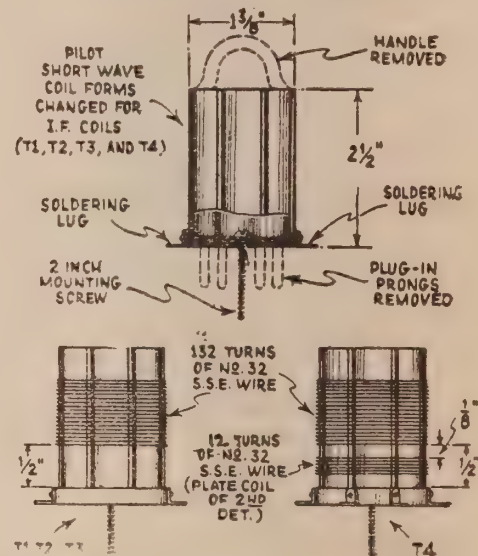

Winding data on I. F. Transformers.

— COIL DATA —

DET. COIL			WIRE USED 	OSC COIL		
RANGE METERS	ANT	SEC		PLATE	GRID	PICK-UP
10 - 20	4 TURNS CLOSE WOUND	4 TURNS SPACED 3/16"	ALL GRID COIL = NR. 24 D.S.C ANT., PLATE AND PICK-UP COILS = NR 30 D.S.C	4 TURNS CLOSE WOUND	4 TURNS SPACED 3/16"	2 TURNS CLOSE WOUND
20 - 40	7 TURNS CLOSE WOUND	11 TURNS SPACED 1/8"		7 TURNS CLOSE WOUND	11 TURNS SPACED 1/8"	2 TURNS CLOSE WOUND
40 - 80	7 TURNS CLOSE WOUND	23 TURNS SPACED 1/16"		7 TURNS CLOSE WOUND	23 TURNS SPACED 1/16"	3 TURNS CLOSE WOUND
80 - 200	16 TURNS CLOSE WOUND	50 TURNS SPACED 1/32"		16 TURNS CLOSE WOUND	50 TURNS SPACED 1/32"	4 TURNS CLOSE WOUND

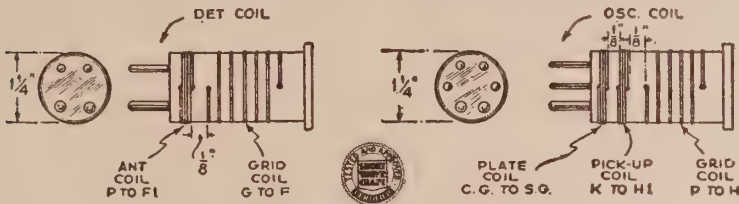

- 1—Chassis and Panel
- 1—Set Na-ald 2 winding, 4 pin S-W plug-in coils.
- 1—Set special 3 winding, 6 pin S-W plug-in coils.
- 5—Tube Shields, National (Hammarlund).
- 3—465 Kc. I.F. Transformers, National; (Gen.-Win; Hammarlund.)
- 1—2 gang .00015 mf. variable condenser, National.
- 1—.000025 mf. midget variable condenser, National.
- 1—.001 mf. padding condenser. Hammarlund.
- 1—.00035 mf. mica condenser.
- 1—.00025 mf. mica condenser.
- 1—.01 mf. 400 v. coupling condenser.
- 10—.1 mf. bypass condensers. Flechthaim.

- 1—7 prong socket Eby (Na-ald).
- 1—10,000 ohm potentiometers—Acratest.
- 2—350 ohm 1 watt resistors, Lynch (International).
- 1—400 ohm 5 watt resistor, Lynch (International).
- 1—500 ohm 1 watt resistor, Lynch (International).
- 2—25,000 ohm 1 watt resistors, Lynch (International).
- 2—30,000 ohm 1 watt resistors, Lynch (International).
- 2—250,000 ohm $\frac{1}{2}$ watt resistors, Lynch (International).
- 1—Antenna-Ground terminal strip.
- 1—A.C. line switch.
- 1—650 volt C. T. power transformer, Radio Trading Co.
- 1—Dynamic speaker and plug, with output transformer for '59 tube, R. T. Co.

- 1—25 mf. 50 volt
Electrolytic con-
denser. R. T. Co.
- 2—8 mf. Electroly-
tic condensers.
R. T. Co.
- 1—10 millihenry R.
F. choke, (Ham-
marlund)*.
- 1—80 millihenry R.
F. choke, National (Hammar-
lund)*
- 1—High ratio tun-
ing dial.
- 1—5 prong socket
Eby (Na-ald).
- 3—4 prong socket
Eby (Na-ald).
- 5—6 prong socket
Eby (Na-ald).

- ## Tubes


- 1—'56 type tube, Gold Seal, Arco, Van Dyke.
2—'57 type tubes, Gold Seal, Arco, Van Dyke.
2—'58 type tubes, Gold Seal, Arco, Van Dyke.
1—'59 type tube, Gold Seal, Arco, Van Dyke.
1—'80 type tube, Gold Seal, Arco, Van Dyke.
*Choose the nearest standard size.—
Editor.

—*Short Wave Craft*, Dec., 1933.

(Continued from last page)

- 1—Silver-Marshall No. 255 audio transformer, A.T.
 - 1—Front panel, bakelite or aluminum 20.5 inches long and about eight inches high (or to suit your cabinet) Blan.
 - 7—tubes; 2—27 type; 2—24 type; 3—35 type.
 - 9—tube sockets, 5-prong—Na-ald.
 - 6—Binding posts, Eby.
- The grid leaks R7, R8, R9 and R10 are very important. I am now using R7—20,000 ohms; R8—125,000; R9—125,000; and R10—1 megohm. The builder should try different values and each change will give different results. Usually the I.F. tubes will oscillate if the resistances are too high. Don't forget this point as it is very important.

—*Short Wave Craft*, April, 1933.

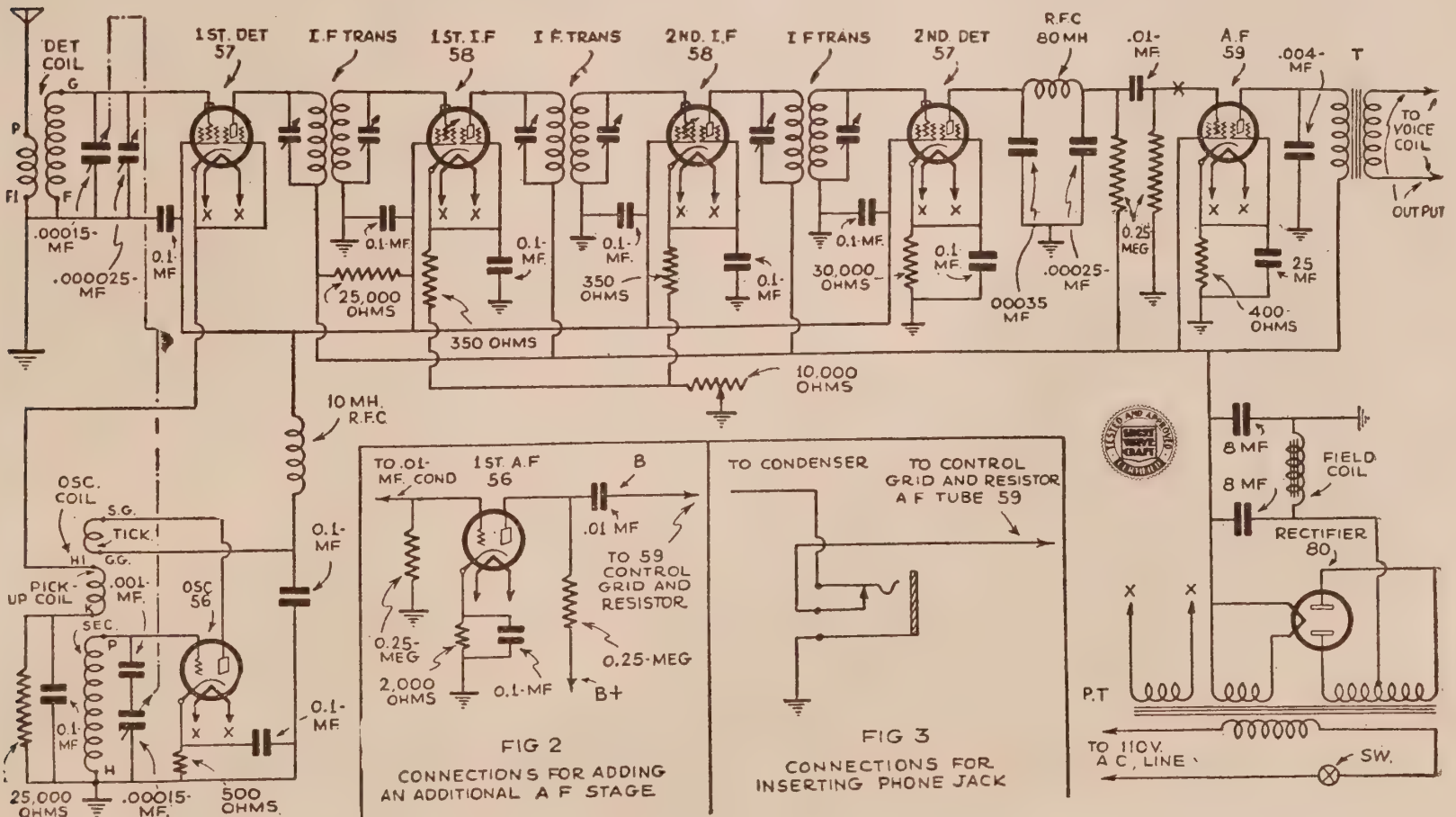

"Ultra Seven" Portable All-Wave Super-Het.

Complete List of Parts Required for the Portable "Ultra-Seven" Superhet

- 3—Hammarlund midget variable condensers, .0002-mf., type MC-200M (3, 10, 15).
- 1—Hammarlund midget variable condenser, .00008-mf., type MC-75M (4).
- 1—Hammarlund padding condenser, 700 to 1,000 mmf., type MICS-10000 (78).
- 8—Hammarlund isolantite short-wave coil forms, 6-prong, type CF-6. (Four sets of two coils each, one antenna coil (2), one detector coil (9). See coil winding directions below.)
- 2—Hammarlund 6-prong isolantite sockets (2, 9).
- 1—Hammarlund 5-prong isolantite socket (14).
- 1—Hammarlund flexible coupling (between condensers (10) and (15)).
- 1—Metallic coupling (between condensers (3) and (10)).
- 3—Automatic Winding Co. intermediate frequency transformers, complete with I.F. coils, tuning condensers and shields; 115 kc. (23, 24), (33, 34), (45, 46).
- 7—Automatic Winding Co. R.F. chokes (25, 31A, 35, 43, 47, 52, 64), 2.5 mh.
- 1—Silver-Marshall 131P oscillator coil (14 A, B, C) or coil wound according to directions on Hammarlund isolantite short-wave coil form, type CF-5.
- 2—Electrad 50,000-ohm potentiometers, type RI-205 (21, 69).
- 3—Electrad Truvolt 400-ohm flexible resistors (7), (30), (41).
- 1—Electrad Truvolt 1,000-ohm flexible resistor (38). Note: Used to control oscillation. Try smaller or large values as needed.
- 1—Electrad Truvolt 1,500-ohm flexible resistor (62).
- 1—Electrad Truvolt 2,000-ohm flexible resistor (17A).
- 1—Electrad Truvolt wire-wound resistor, 300 ohms, type C-3, with clip moved to 250-ohm position (73). Note: A 250-ohm rheostat may be substituted, provided this will carry 300 mls. without undue heating.
- 4—I.R.C. (Durham) 2-megohm metallized resistors, type M.F.4½ (27, 37, 50, 67).
- 1—I.R.C. (Durham) 5-megohm metallized resistor, type M.F.4½ (12).
- 2—I.R.C. (Durham) 20,000 ohm metallized resistors, type M.F.4 (22, 70).
- 1—I.R.C. (Durham) 25,000-ohm metallized resistor, type M.F.4 (58).
- 1—I.R.C. (Durham) 50,000-ohm metallized resistor, type M.F.4 (17).
- 2—Aerovox .1-mf. (each section) double section metal case condensers, type 260-21 (6, 8), (18, 25A).
- 2—Aerovox .1-mf. (each section) triple section metal case condensers, type 260-31 (29, 31, 32), (40, 42, 44).
- 1—Aerovox .00015-mf. mica condenser, type 1460 (11).
- 1—Aerovox .00025-mf. mica condenser, type 1460 (16).
- 1—Aerovox .0005-mf. mica condenser, type 1460 (77).
- 5—Aerovox .002-mf. mica condensers, type 1460 (26, 36, 48, 53 54).
- 2—Aerovox .01-mf. mica condensers type 1450 (20, 63).
- 2—Aerovox .25-mf. metal case condensers, type 260 (74, 75).
- 1—Aerovox .5-mf. metal case condenser, type 260 (57).
- 1—Aerovox 1-mf. metal case condenser, type 260 (68).
- 1—Aerovox 4-mf. dry electrolytic condenser, type E5-4 (small can (61)).
- 1—Aerovox 8-mf. dry electrolytic condenser, type E5-8 (78).
- 1—Trutest 30-henry audio choke (77).
- 1—Eby twin "speaker" jack (65, 66).
- 7—5-prong wafer-type sockets (5, 13, 19, 28, 39, 49, 60).
- 1—Drum dial with escutcheon plate and 3-ampere, pilot light (76).
- 1—Antenna binding post or antenna flexible lead (1).
- 5—Binding posts for control box.
- 1—110-volt type single-throw, double-pole flush-plate toggle switch (72, 72A).
- 1—Single-pole, single throw Cutler-Hammer toggle switch (71).
- 4—Arcturus 136-A screen grid tubes (5, 13, 28, 39).
- 2—Arcturus 137-A tubes (19), (49).
- 1—Arcturus 138-A tube (60).
- 1—3-volt flashlight battery (51).
- 1—22½ volt "C" battery (56).
- *1—Trutest audio transformer, ratio 3½ to 1, AF-8, type 2A325 (55).
- *1—Trutest audio choke, 30-henry.
- 1—Weston D.C. milliammeter (0 to 1 range), model 301, for visual tuning.
- 1—Littelfuse fusible cap, No. 1037, with two ½-ampere, 500-volt instrument Littelfuses, type 1046 (79).
- 1—Small Wright-De Coster No. 255 reproducer (66A), 6⅜ inches diameter (6-volt field for storage battery operation or 110-volt field if operated from line).
- 1—Control box.
- 1—Jones plug (9-prong) with corresponding socket.
- 1—Bakelite panel 12¾ x 11¾ x 3/16 inches (See Fig. 7).
- 3—Aluminum shields, same size as shields containing I.F. transformers, 2⅝ inches high. Shield "X" containers (25, 26, 27), Shield "Y" containers (35, 36, 37), Shield "Z" containers (47, 48, 50).
- Note—Numbers in parentheses refer to corresponding numbers used to mark parts on diagrams.
- *Trutest parts manufactured by Wholesale Radio Service Co. of New York City.
- DATA ON COILS USED IN THE "ULTRA-SEVEN" SUPERHETERODYNE COILS (2) AND (9)**
- Coil Forms: Hammarlund Isolantite, 1½ inches diameter, 2½ inches long exclusive of knobs and prongs. Six-prong forms used.
- 9 to 15 Meters:
Secondary, 2-5/6 turns of No. 16 enamel.
Primary, 1-5/6 turns of No. 34 enamel.
Tickler, 3 turns of No. 32 double silk.
- 14.5 to 25 Meters:
Secondary, 6¼ turns of No. 16 enamel.
Primary, 3-5/6 turns of No. 34 enamel.
Tickler, 3 turns of No. 32 double silk.
- 23 to 41 Meters (Coil Set No. 1):
Secondary, 11-5/6 turns of No. 18 enamel.
Primary, 7-5/6 turns of No. 34 enamel.
Tickler, 3 turns of No. 32 double silk.
- 40 to 70 Meters (Coil Set No. 2):
Secondary, 19-5/6 turns of No. 18 enamel.
Primary, 12-5/6 turns of No. 34 double silk.
Tickler, 4 turns of No. 32 double silk.
- 65 to 115 Meters:
Secondary, 34-5/6 turns of No. 24 enamel.
Primary, 21-5/6 turns of No. 34 double cotton.
Tickler, 4 turns of No. 32 double silk.
- 115 to 200 Meters (Coil Set No. 3):
Secondary, 62-5/6 turns of No. 28 enamel.
Primary, 38-5/6 turns of No. 32 double silk.
Tickler, 5 turns of No. 32 double silk.
- 200 to 360 Meters (Coil Set No. 4)
- Antenna Coil (2)**
Secondary, 130-5/6 turns No. 32 double silk.
Primary, 60-5/6 turns No. 32 double silk.
Tickler, 7 turns No. 32 double silk.
- Detector Coil (9)**
Secondary, 98-5/6 turns No. 32 double silk.
Primary, 47-5/6 turns No. 32 double silk.
Tickler, 7 turns No. 32 double silk.
- 350 to 550 Meters (Coil Set No. 5)
- Antenna Coil (2)**
Secondary, 171-5/6 turns No. 32 enamel.
Primary, 82-5/6 turns No. 32 enamel.
Tickler, 9 turns No. 32 double silk.
- Detector Coil (9)**
Secondary, 166-5/6 turns No. 32 enamel.
Primary, 82-5/6 turns No. 32 enamel.
Tickler, 9 turns No. 32 double silk.
- Note.—It may be necessary to add several turns to tickler winding of detector coil (9) to obtain desired regeneration.
- OSCILLATOR COIL (14 A, B, C)**
Coil Form: Hammarlund Isolantite, 1½ inches diameter, 2½ inches long. Five-prong form used.
- Grid Coil (14A):**
82½ turns No. 28 enamel.
- Plate Coil (14B):**
32-2/3 turns No. 28 double silk.
- Inner Coupling Coil (14C):**
50 turns No. 28 double silk. (14C) is wound on cardboard form which just fits inside isolantite form.
- The intermediate frequency coils are "universal" wound with 800 turns of No. 36 S.S.C. wire each; tuned by Hammarlund adjustable condensers of 140-220 mmf. range. Each coil has an inductance of 6,900 microhenries or 6.9 millihenries. The I.F. coils are wound "universal" machine or "bank" style on a ½-inch diameter dowel. The I.F. is 115 kc.
- Short Wave Craft, Oct., 1932.

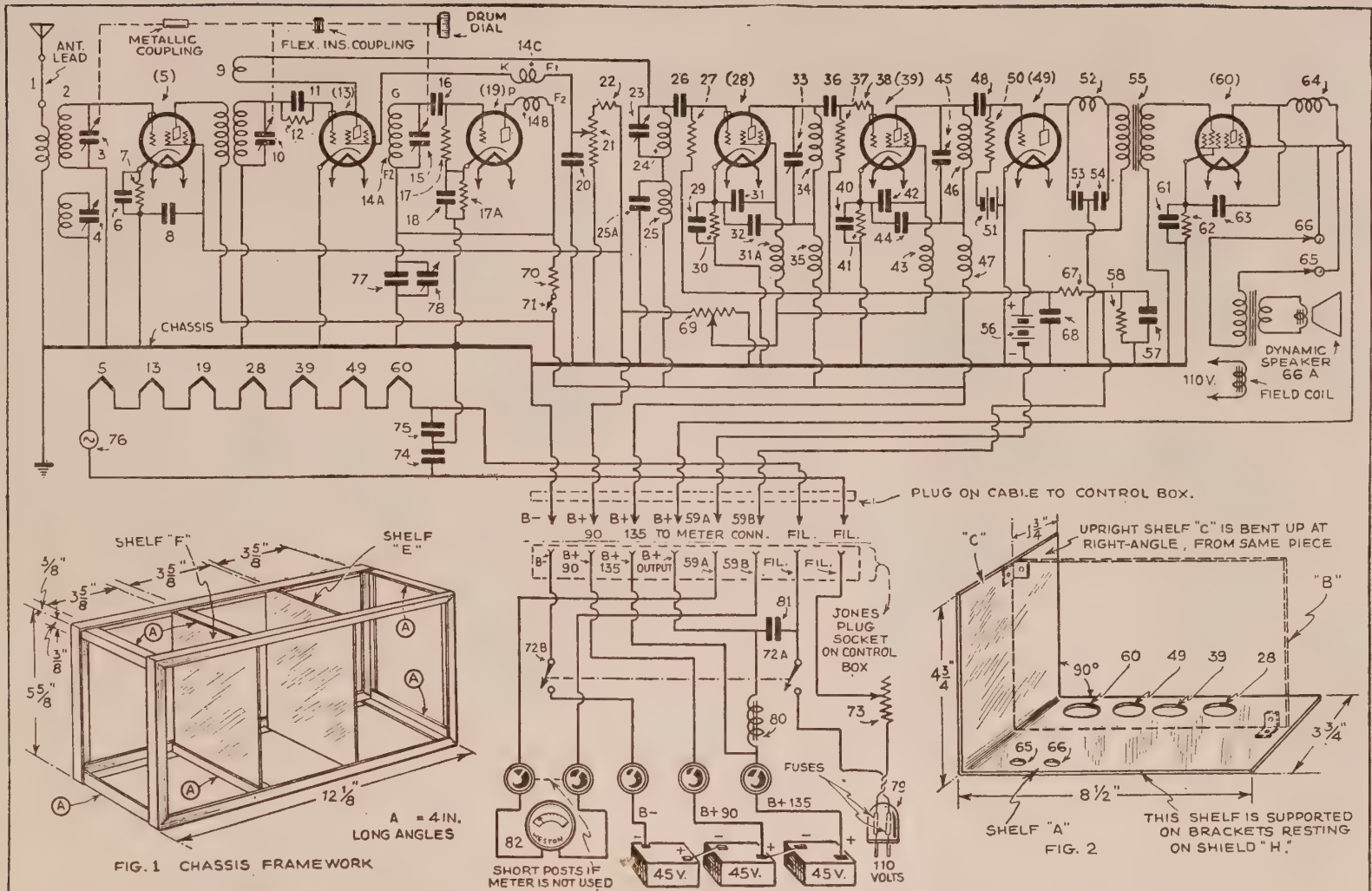


FIG. 1 CHASSIS FRAMEWORK

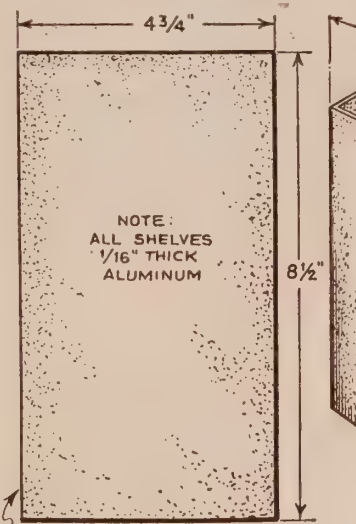


FIG. 1A UPRIGHT SHELF "B" FASTENED TO FRAMEWORK. ALSO FASTENED TO "A" AND "C" BY RT. ANGLE BRACKETS.



FIG. 3 ALUMINUM U-SHIELD SURROUNDING TUBE (39)

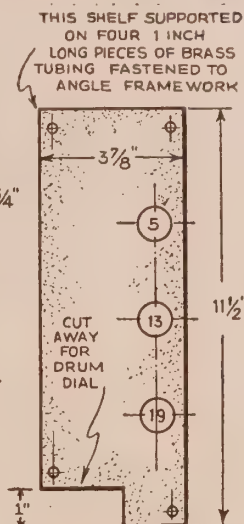


FIG. 4 UNDERSIDE VIEW OF SHELF "D"

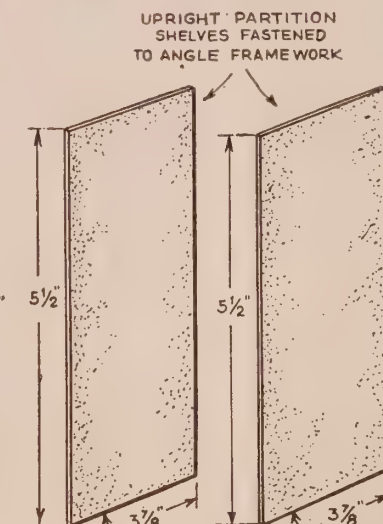


FIG. 5 SHELF "E"

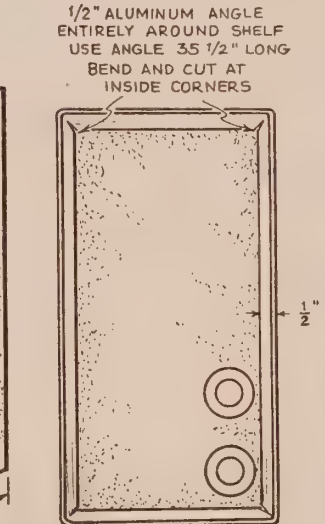


FIG. 6A UNDERSIDE VIEW OF SHELF "G"

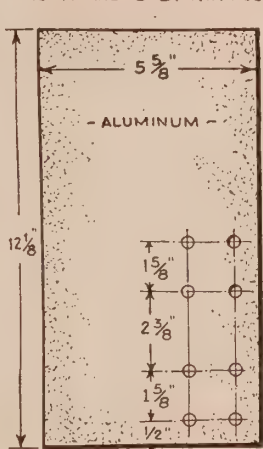


FIG. 6B REAR UPRIGHT SHELF "G"

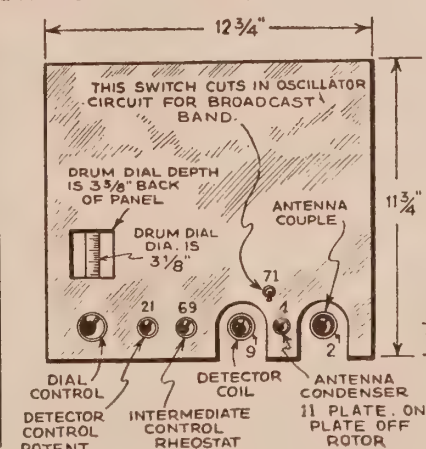


FIG. 7A FRONT VIEW (PANEL)

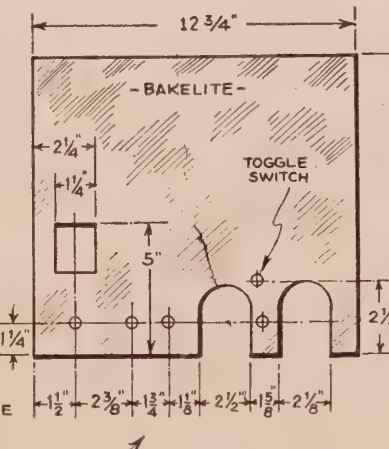


FIG. 7B FRONT VIEW OF PANEL SHOWING DRILLINGS & PUNCHES

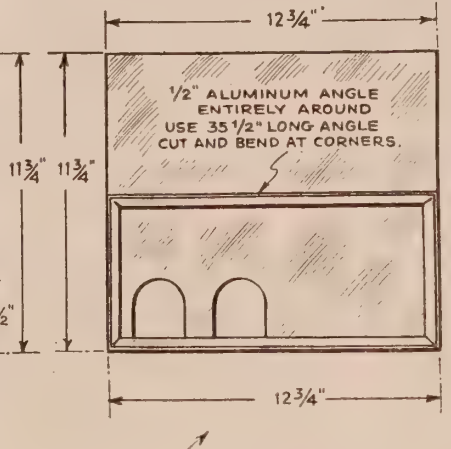


FIG. 7C BACK VIEW OF PANEL SHOWING FRAME

"Improved" 5 Meter Super-Regenerator


Parts List for 5 Meter Receiver

- 1—grid coil (see text).
- 1—18 mmf. tuning condenser. National.
- 1—interruption frequency coil. Gen-Win.
- 1—250 R.H. Rf choke. Gen-Win.
- 1—.0001 mf. mica condenser.
- 3—.001 mf. mica condenser.
- 1—.002 mica condenser.
- 1—.1 mf. Bypass condenser.
- 1—.01 mf. Bypass condenser.
- 1—20 mf. 25 volt electrolytic condenser.
- 2—2 meg. $\frac{1}{2}$ watt resistor. Lynch.
- 1—2,000 ohm 1 watt resistor. Lynch.
- 1—250,000 ohm 1 watt resistor. Lynch.
- 1—25,000 ohm 1 watt resistor. Lynch.
- 1—500 ohm 1 watt resistor. Lynch.
- 1—50,000 ohm potentiometer. Acratest.
- 1—20 ohm C.T. resistor. R. T. Co.
- 1—6 prong isolantite socket, National (Hammarlund).
- 1—6 prong laminated socket. Na-ald.
- 1—5 prong laminated socket. Na-ald.
- 1—Type "B" 270 degree dial. National.
- 1—57 tube R.C.A. Radiotron Co. (Arco).
- 1—56 tube R.C.A. Radiotron Co. (Arco).
- 1—2A5 tube R.C.A. Radiotron Co. (Arco).

Cathode Tap

The cathode tap is taken off the grid coil three turns from the ground end. Oscillation can be obtained with the tap at the second turn but the screen voltage will have to be turned up too high and results in less sensitivity to weak signals and a very high hiss level.

One must also be careful not to have too

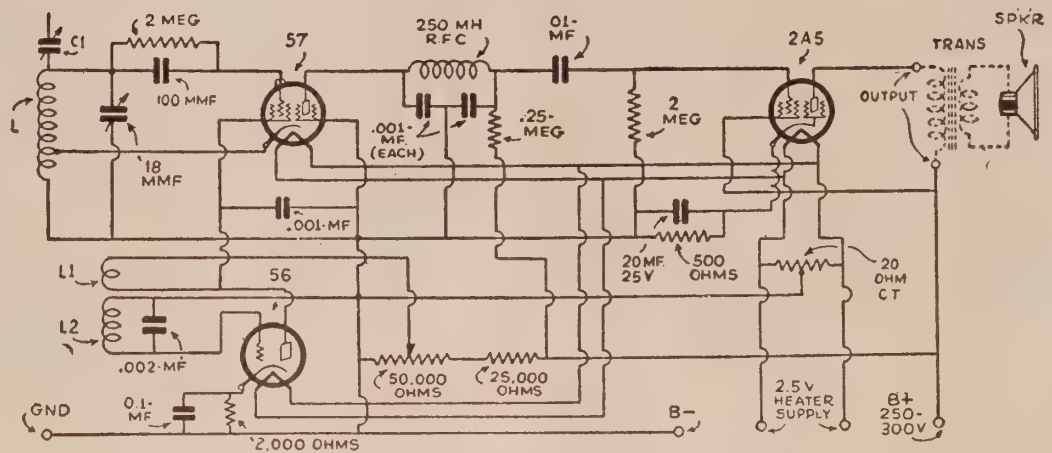

much capacity across the grid coil of the receiver; eight turns of No. 12 solid enameled antenna wire are used, having an inside diameter of one-half inch. This is tuned with an 18 mmf. National ultra frequency condenser, having plates cut to give a 270 degree tuning range. With this coil and condenser, the 5 meter band is spread over 60 degrees on the dial.

The Question of Interruption Frequency

In a circuit where we have increased sensitivity, it is possible to use a much higher interruption frequency and so obtain much better quality. Using a higher frequency does not reduce the audio volume level to any great extent, so far as can be determined by the ear; the improved quality alone would be worth a slight decrease in volume. To obtain a higher interruption

frequency it is necessary to remove about one-third of the turns from the transformer primary and secondary, assuming that the original has 800 turns in the primary and 1200 to 1400 for the secondary.

The writer has found that the sizes of the tuning condensers shunted across the interruption frequency coils has a decided effect on the receiver's ability to perform during duplex QSO's.

Antenna Coupling Critical

One of the most critical points of the 57 detector is the antenna coupling. Extremely loose coupling was found necessary and surprising as it may seem loose coupling does not reduce the sensitivity of the receiver. The best antenna system used was a vertical wire three half-waves in length, or 24 feet.

—Short Wave Craft, Feb., 1934.

5 Meter Super-Regenerator

Construction Data

The two detector coils are each wound with 5 turns of No. 10 gauge copper wire (B&S) and are made by winding the wire on one-half inch bakelite rod, letting it slide off and pulling it out so that there is a space about one diameter between turns.


The adjustable condenser in series with the aerial should be a neutralizing condenser and should generally be worked at a very small capacity. (10 to 20 mmf.)

The "super" tube is simply a straightforward oscillator. All it needs is coils! These were wound originally on a solid $1\frac{1}{2}$ inch ebonite (bakelite) former with two deep slots turned in it. No. 32 or 34 (B&S) gauge wire was used and 1,000 turns were wound for the grid coil and 750 turns for reaction (plate coil). Here again the outside ends go to the grid and plate and the "middles" to L.T. negative (A minus) and

H.T. positive (B plus) respectively. The grid coil is shunted by a .002 mf. fixed condenser.

The operation is as follows: First of all, don't use more than 60 volts of H.T. (B battery). It isn't necessary. Remove the "super" tube altogether and make sure that the detector is oscillating. Then put in the "super" and listen for the characteristic mushy hissing noise which indicates that it is working. You only hear this, by the way, when the detector is oscillating and you should set the reaction condenser so that it is not oscillating too hard (although the setting is not at all critical).

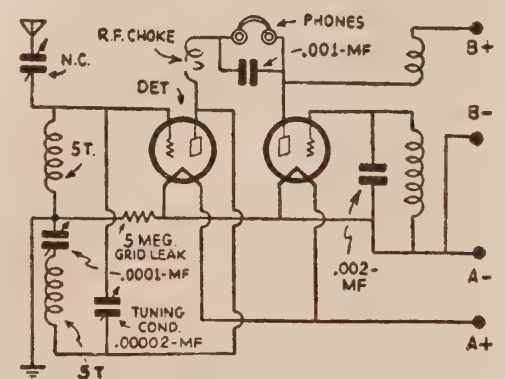
Don't worry about what will appear to be a loud background noise—as soon as you tune in a signal of any strength the noise disappears! A carrier wave without any modulation on it will appear as a hole in the mush. Tune around the band very



slowly, listening for any diminution in the mush. A really weak station will only cut it down slightly, but you should be able to hear speech and music through the noise that remains.

—Amateur Wireless, London.

5 Meter Bear-Cat Receiver

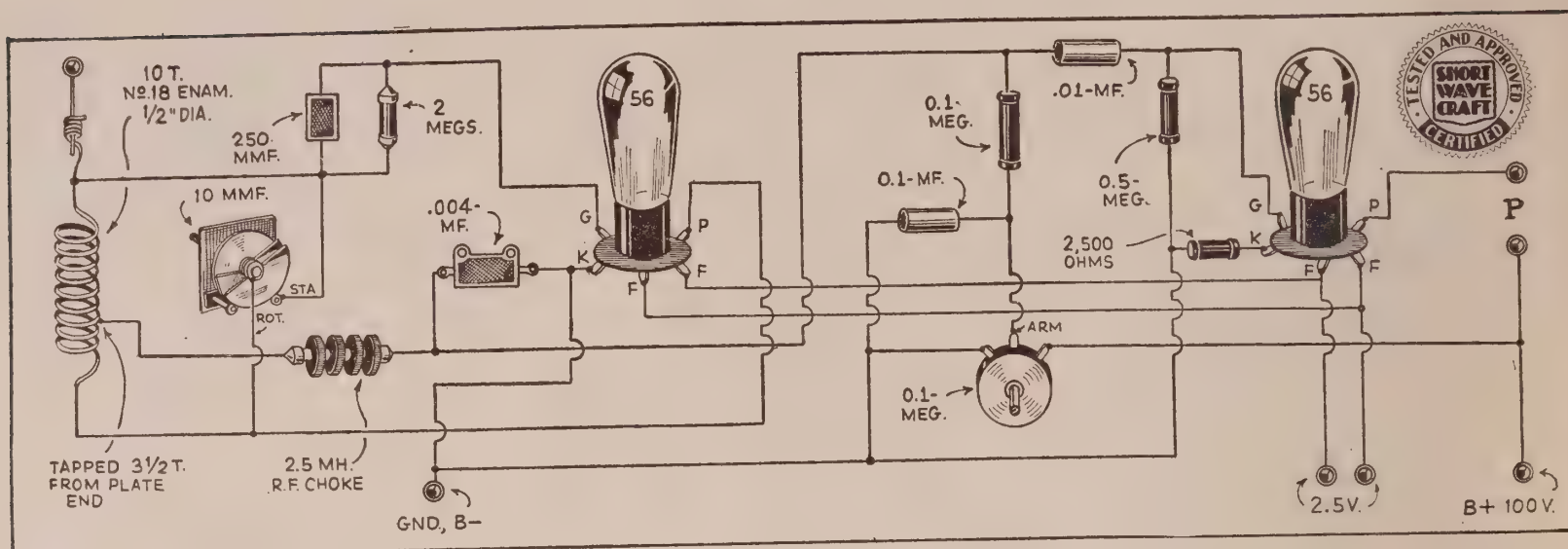

Parts List for 5-Meter Super-Regenerator

- 1—(approximately) 10 mmf. midget variable condenser.
- 1—.00025 mf. mica condenser.
- 1—.004 mf. mica condenser.
- 1—.1 mf. by-pass condenser.
- 1—.01 fixed condenser.
- 1—2 megohm grid leak.
- 1—.1 meg. fixed resistor.
- 1—.5 meg. fixed resistor.
- 1—25 ohm fixed resistor.
- 1—100,000 ohm potentiometer.

- 2—5-prong sockets.
- 1—Special inductance (homemade)—see diagram.
- 1—2 1/2 millihenry R.F. choke.
- 2—Type 56 RCA Radiotron tubes.
- 1—6"x10"x7" chassis. Blan; Insuline.

—Short Wave Craft, Aug., 1934.


The Oscillodyne

Parts List for Building the Oscillodyne

- 1—Aluminum panel, 4 1/2"x6"x1/16". Blan (Insuline Corp. of America.)
- 1—Bakelite subpanel, 4 1/2"x5 1/2"x3/32". Insuline Corp. of America.
- 1—50,000 ohm variable resistor, R2, Frost, (Clarostat).
- 1—Set of 4 pin plug-in coils wound on Hammarlund Isolantite forms 1 1/2" dia., per specifications given in article.
- 1—Series antenna condenser, C1, about 25 mmf. max., Hammarlund Compensator type condenser.
- 1—Variable tuning condenser, C2, .0001 mf., Hammarlund.
- 1—Grid condenser, C3, 100 mmf., or 50 mmf. Illini (Polymet).
- 1—Fixed resistor, R1, 3 megohms, Lynch.
- 1—Fixed condenser, C4, .0005 mf., mica type, Pilot or Flechtheim. (Polymet.)
- 7—Binding posts, Eby.
- 1—3" midget National Velvet Vernier Dial, type BM.

The plug-in coils employed are wound on tube bases. The specifications for the windings are given in the table accompanying this article. The turns of both windings are wound without spacing. It is essential that the two windings be wound in the same direction. This means that if the two inside terminals of the windings are connected together, the coil will appear like a continuous winding tapped near the center.

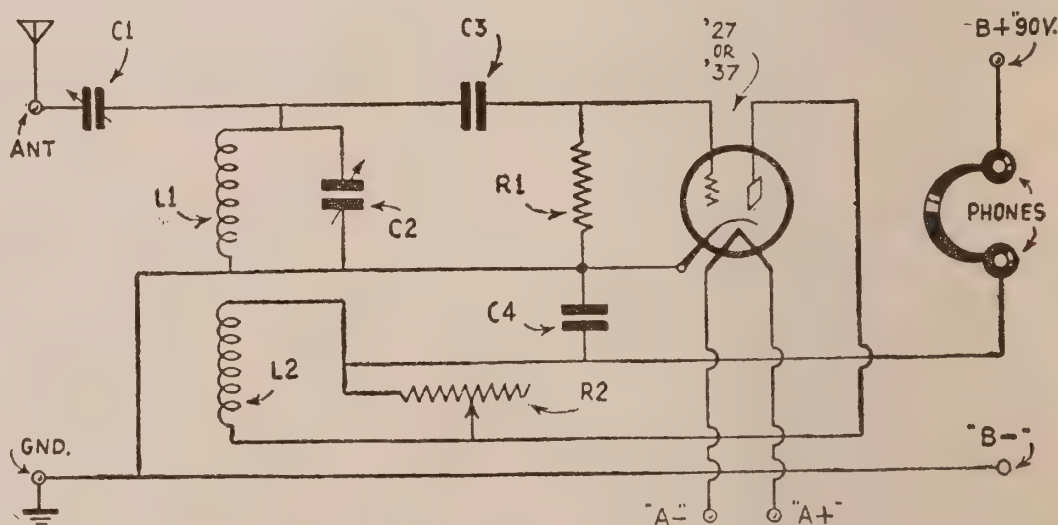In regard to coil specifications, the following table is furnished for tube base



coils wound with No. 36 D.S.C. wire and tuned with a 100 mmf. (.0001 mf.) condenser. The first two coils may need a half turn adjustment one way or the other.

Approximate Wavelength (meters)	Sec.	Tickler
14-25	4	6
23-41	7	9
40-85	14	12
83-125	23	23
120-200	36	36


About 1/8" separation between windings. It will obviously be necessary to extend the

tube base forms if coils for the 'broadcast band' are used. However, grid and plate windings of about 67 turns will tune from 200-360 meters and 105 turn windings will tune from 350-550 meters with the above condenser.

The windings should be so connected that the two outside leads go to the grid condenser and the plate of the tube, respectively, while the two inner leads go to the cathode and phones respectively. If connections are not made in this manner the tube will not oscillate!

—Short Wave Craft, April, 1933.

The "53" 1-Tube Twinplex

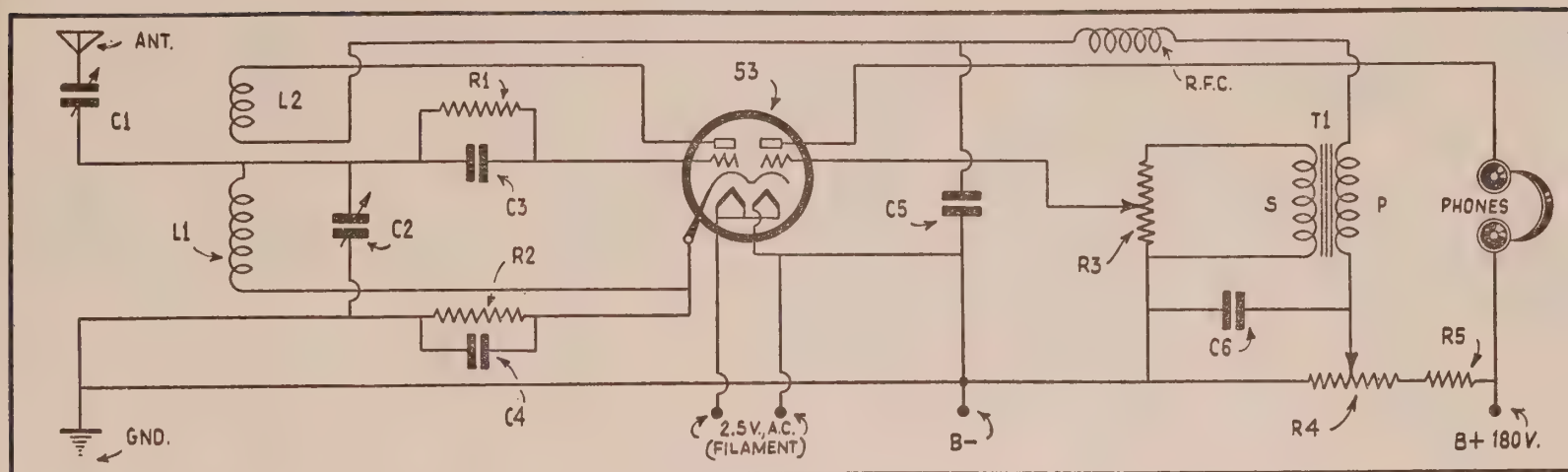

Parts Required

C1—35 mmf. midget variable condenser.
C2—Hammarlund "Midline" midget variable condenser—140 mmf., Type MC-140-M.
C3—Molded mica condenser—.0001 mf.
C4, C6—.5-.5 mf. dual by-pass condenser.
C5—.0005 mf. Molded mica condenser.
L1, L2—Set of short-wave Octo-Coils 16-200 meter.

RFC—Hammarlund isolantite R.F. choke, 8 millihenrys, Type CH-8.
R1—3 meg. grid-leak; Lynch (International).
R3—400 ohm wire-wound Resistor.
R2—200,000 ohm potentiometer (Acratest).
R4—25,000 ohm potentiometer (Acratest).
R5—50,000 ohm resistor, Lynch (International).
T1—Audio frequency transformer.
1—Alden 4 prong socket, type 481X.

1—Alden 7 prong socket, Type 487.
7—Fahnestock clips.
1—Type 53 Tube.
1—Roll hook-up wire.
1—National Type "B" Velvet-Vernier dial (0-100-0).
1—Aluminum panel 6"x9"x1/16".
1—Baseboard 9"x7"x3/4".
1—Type 53 tube; Gold Seal, Arco, Van Dyke.

—Short Wave Craft, Oct., 1933.

Building a 2-Tube Oscillodyne

List of Parts Required for Two Tube Oscillodyne

C1—Hammarlund equalizing condenser, EC-35. (3-35 mmf.).
C2—Hammarlund midget condenser, midline plates, 80 mmf. capacity, type MC-75-M. (Cardwell Midway, 100 mmf. type C, plates, 404-C.)
C3—Aerovox Type 1460, .00015 mf. mica condenser.
C4—Aerovox Type 1460, .002 mf. mica condenser.
C5—Aerovox Type 1460, .004 mf. mica condenser.
C6—Aerovox Type 261 filter condenser—single section 1. mf. 300 volt D.C. working voltage.
C7—Aerovox Type 261 Filter Condenser—double section .5-.5 mf., 200 volt D.C. working voltage.
L1—Bakelite Tubing 1" diameter x 2" long (Wholesale Radio Service Co., Inc.). See text for winding details.
L2—Hammarlund Isolantite R.F. choke—type CH-8, 8 millihenrys.
L3—Stromberg-Carlson A.F. transformer, No. 3-A (secondary winding only used).
R1—Aerovox Type 1095 Resistor, 2 megohms.
R2—Aerovox Type 1095 Resistor, 100,000 ohms.
R3—Electrad Type RI-205, 50,000 ohm volume control (potentiometer).

R4—Aerovox Type 1095 Resistor, .5 megohms.

R5—Electrad Type GB Flexible Resistor 500 ohms, 2 watt rating.

R6—Yaxley center-tapped resistor, 20 ohms.

1—Yaxley No. 1625 two gang 5 point tap switch.

1—Eby Twin binding post assembly.

1—Eby Twin jack assembly.

5—Eby binding post.

2—Hammarlund Isolantite 5 prong sockets, Type S-5.


1—Vernier Dial (National) 5", with variable ratio.

2—1"x8 1/2" brackets.

1—Aluminum panel 6"x9".

1—Aluminum panel 4 1/2"x8 1/2".

Miscellaneous nuts, bolts, wire, etc.

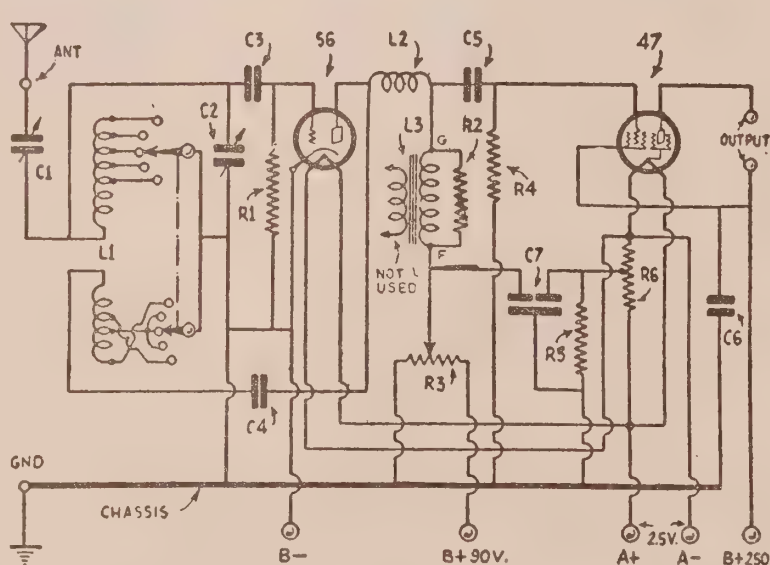

Coil Construction


The tapped inductance coil is wound on a bakelite form 1" in diameter and 2" long. No. 35 D. S. C. wire is employed and there is no spacing between turns. The windings are separated by one-eighth of an inch. The winding procedure is as follows:

Start the grid winding from the inside and wind outward, tapping the coil at 5, 8, 12, and 20 turns while winding. This winding should have a total of 33 turns.

When the first winding is finished, the tickler winding is started from the inside and wound in the same direction as the preceding. This means that the two windings would appear like a continuous winding if joined in the center. This winding is tapped at 8 and 11 turns and has a total of 15 turns.

—Short Wave Craft, May, 1933.

A 5-Tube A.C. Oscillodyne Set

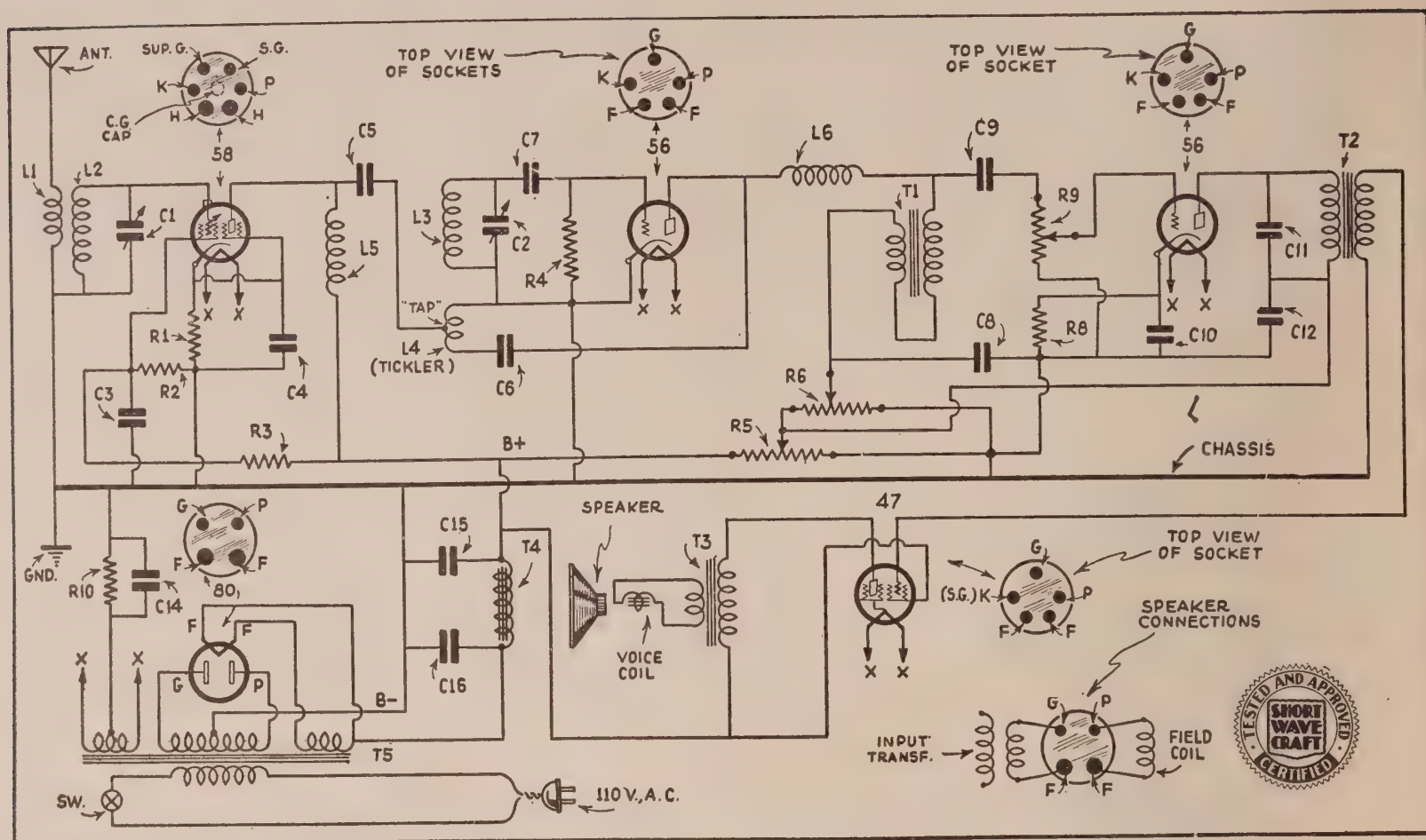

Coil No.	Turns	Wdg. L1	Wdgs. L2 and L3	Turns	Wdg. L4
1	4 1/4	4 3/4	1 3/4	6	6
2	6 1/4	10 3/4	1	12	8
3	7 1/4	22 3/4	1 7/8	40	12
4	15 1/4	51 3/4	1 5/8	40	20

It will be noted that the rewound winding L4 is tapped at the center. In order to do this and at the same time employ a four-prong coil form it is necessary to solder the grounded lead of this winding into the prong occupied by the grounded terminal of L3. The tapped lead then occupies the prong vacated by this procedure, while the outside terminal retains its former position. As previously, the windings L3 and L4 should be wound in the same direction or the tube will not oscillate.

Parts List

- C1, C2—Cardwell Midway Double Section "C" Type Variable Condenser—140 mmf. per section. Type 405-c.
 C3, C4, C5, C6, C11—Aerovox Type 1460 Mica condenser .004 mf.
 C7—Aerovox Type 1460 Mica Condenser—.00015 mf.
 C8, C10, C12—Aerovox Type 281 Tubular Cartridge Condensers, .5 mf., 200 D.C. W.V.
 C9—Aerovox Type 281 Tubular Cartridge Condenser, .01 mf., 200 D.C. W.V.
 C14—Aerovox Type PR25 Dry Electrolytic Tubular Condenser, 25 mf., 25 V. D.C.
 C15, C16—Aerovox Type E5 Dry Electrolytic Filter Condenser, 8-8. mf., 450 D.C. W.V.

- R1—Electrad Truvolt Wire Wound Pigtail Resistor, Type PG, 400 ohm.
 R2, R3—Aerovox Type 1094 Resistors, 50,000 ohm, 1 watt.
 R4—Aerovox Type 1095 Resistor, 1 megohm, 1/2 watt.
 R5—Electrad Truvolt Adjustable Resistor, Type B 150, 15,000 ohm, 25 watts, with one extra slide.
 R6—Electrad Potentiometer, Type R1-279, 25,000 ohms.
 R8—Electrad Truvolt Wire Wound Pigtail Resistor, Type P6, 2000 ohm.
 R9—Electrad Potentiometer, Type R1-281P, 200,000 ohm, with A.C. Switch.
 R10—Electrad Truvolt Wire Wound Pigtail Resistor, Type PG, 500 ohm.
 L1, L2, L3, L4—2 sets Alden Short Wave Coils, Type 704SWS. L4 rewound, see text for details.
 L5, L6—Hammarlund Isolantite R.F. chokes Type CH-8. (Inductance 8 M. H.)
 T1, T2—Thordarson Audio Frequency Transformers, Type T-5736.
 T3, T4—Jensen Dynamic Loud Speaker Type 3007A, 1800 ohm field.
 T5—Thordarson Pentran Power Transformer, Type T-4900.
 2—Hammarlund 4 prong isolantite sockets, S-4.
 1—Alden* 4 prong laminated socket, 280 marking; 2—5 prong, 56 mark; 1—5 prong, 47 mark; 1—6 prong, 58 mark; 1—4 prong, plain; 1—4 prong connect-orald socket, type 94. *(Na-ald).
 1—Eby Twin Binding Post Assembly.
 1—Special "Blan" chassis.

Five tubes—R.C.A., one-58, two-56, one 47, one-80 (Arcturus; Sylvania or R. C. A.).

By inserting a screen grid tube between the two tuned circuits it is possible by taking suitable precautions in regard to shielding to practically eliminate all feedback from the detector circuit into the input circuit. This enables a degree of selectivity to meet the demands of the average short-wave listener.

Complete shielding of the R.F. and detector stages is essential for two reasons.

The loud speaker used in connection with this set is a Jensen type 3007A having a built-in transformer designed to couple to a single type 47 output. The field of this speaker has a resistance of 1800 ohms and is used as the choke in the power-supply filter. Connections to the loudspeaker are with an Alden four-prong wafer socket mounted on the back of the subpanel. The proper method of making connections to this socket is shown in the diagram.

After the set has been completely wired it is necessary to make alterations to the Alden coils used in the detector circuit before the set can be put in operation. The ticker winding is removed and rewound according to the specifications given in the appended table. The details of the other windings are also given for the benefit of those wishing to wind their own coils from blank forms.

—Short Wave Craft, June, 1933

The "Regenerative-Oscillodyne"



PARTS REQUIRED FOR REGEN.-

OSCILLODYNE SET

- C1, C5—Hammarlund Adjustable Padding Condenser, 10-70 mmf., type MICS-70.
- C2—Hammarlund Midline Midget Condenser, 140 mmf., type MC-140-M.
- C3—.0001 mf. Molded Mica Condenser, pigtail leads.
- C4—25 mf. Dry Electrolytic Condenser, with Mounting Strap. Type DR-275.
- C6—.005 mf. Molded Mica Condenser, type MC-1218 or NM-1283.
- C7, C8—.5 mf. Tubular By-Pass Paper Condensers, type BB-2050 (Concourse).
- L1, L2—5 Hammarlund 4-prong isolantite coil forms, type CF-4.
40 feet No. 22 enameled magnet wire.
35 feet No. 26 double-silk covered wire.
100 feet No. 34 double-silk covered wire
(See below for Winding Details.)
- L3—Hammarlund 8 mh. R.F. choke, type CH-8.
- T4—National Impedance Coupling Unit, type S-101.
- R1—Lynch 2 megohm Metallized resistor, ½ watt, type LF-4½.
- R3—50,000 ohm Volume Control (Potentiometer).
- R2—20-ohm Rheostat, or Amperite, type 1-1.
- R4—Wire-Wound Pigtail Resistor, 700-ohms.
- 2—Eby 4-prong isolantite sockets.
- 1—Eby 4-prong wafer socket.
- 1—Eby molded Twin Binding Post Assembly.
- 1—Eby Molded Twin Speaker Jack Assembly.
- 1—National Type B Dial (0-100-0).
- 1—Midget Jack Switch, S.P.S.T.
- 1—Midget Jack Switch D.P.S.T.
- 1—Alden (Na-ald) 4-prong socket, type 424.
- 1—Alden (Na-ald) Connectorald Plug, type 94.
- 1—Blan Aluminum Subpanel, 1/16", 8¾" x 8½".
- 1—Blan Aluminum Panel, 6" x 9".
- 3 feet of 4-Conductor Battery Cable.
- 2—Triad type 230 tubes.
- 1—Roll Hookup wire (solid).

CIRCUIT DATA

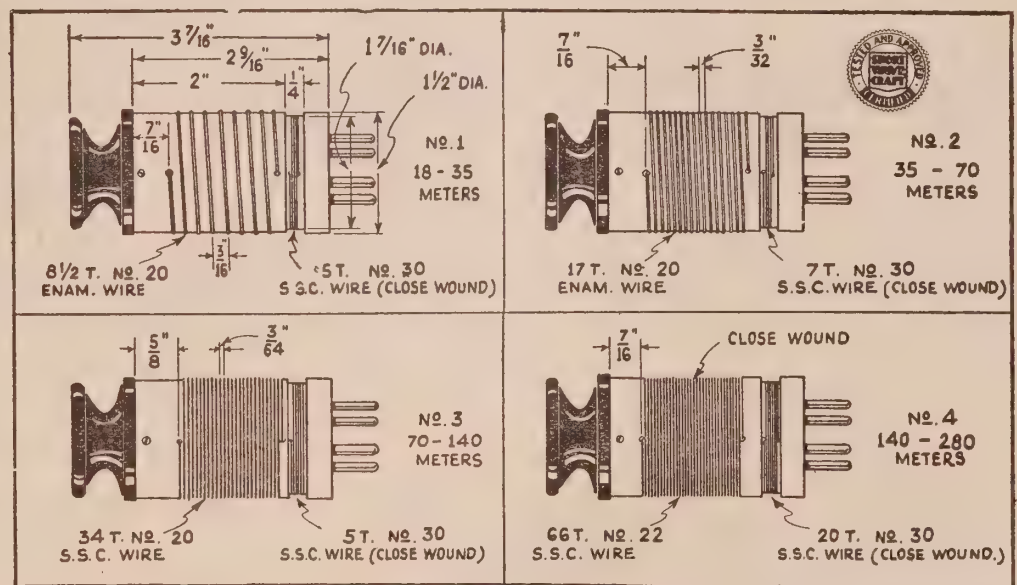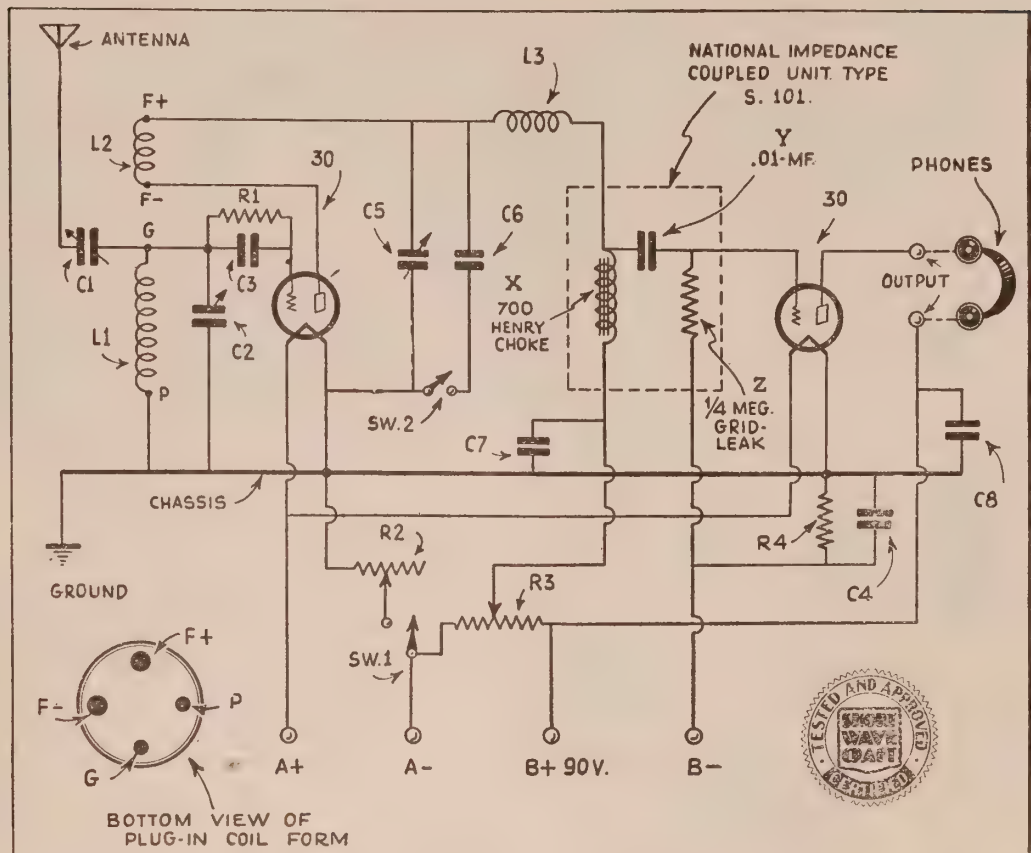The audio frequency amplifier is impedance-coupled, which makes it possible to match the rather high plate impedance of the 30 tube when employed in the oscillodyne connection. Of course, this condition could also have been met by resorting to resistance type coupling but



impedance-coupling will result in substantially greater volume and has other advantages as well. For this purpose, a National S-101 impedance-coupling unit is employed, which consists of a 700 henry

choke, together with a .01-mfd. coupling condenser and a 250,000-ohm grid-leak, all mounted in a single container.

—Short Wave Craft, July, 1933.

Coil Data

Coil No.	Wavelength range (Meters)	No. Turns	L1 B.&S. Wire Ga.	L2 No. Turns	B.&S. Wire Ga.
1	18-35	* 8.5	22 En.	5	34 D.S.C.
2	35-70	* 17.0	22 En.	7	34 D.S.C.
3	70-140	* 34.0	22 En.	12	34 D.S.C.
4	140-280	66.0	26 D.S.C.	20	34 D.S.C.
5	280-560	130.0	34 D.S.C.	20	34 D.S.C.

*Turns spaced to make length of winding equal to 1½ inch.

The Short-Wave Superregenode

List of Parts


Two Hammarlund "MLW-125" 125 mmf. Short Wave condensers, C1, C2, and two Kurz-Kasch vernier dials;
 One Hammarlund 14-to-110 meter "Model LWT-4" short-wave kit, L1;
 One Hammarlund 14-to-110 meter "Model LWC1" short-wave kit, L2;
 One Hammarlund "Type RFC 250" 250-mh. R.F. choke, RFC1;
 One Hammarlund "Type EC 80" 80 mmf. equalizing condenser, C4;
 One Flechtheim filter block (five 1-mf. units), C6, C7 (2 mf.), C8 (1 mf.);
 One Ferranti "Type AF-5," 3.75-to-1 ratio audio transformer, T;
 Two Sangamo .001-mf. fixed condensers, C3, C5;
 Two Electrad 50,000-ohm "Super-Tonators," R1, R2;
 One Acme 30-kc. I.F. transformer, L3 (see text);
 One Yaxley 7-wire cable, 3 to 9;
 Two Eby lettered binding posts, 1 and 2;
 One output connection block, 10-11;
 Two Pilot 4-prong UX sockets, V1, V2;
 One Pilot 5-prong UY socket, V3;
 One aluminum cabinet 7 x 9 x 18 x 3/32" thick;
 Two aluminum sheets (partitions), 7 7/8 x 9 5/8 x 3/32" thick;
 Miscellaneous hardware (screws, nuts, lock-washers, wire, etc.).

The kit of coils designated as LWC1 consists of single windings with the same number of turns as the secondary in the Type LWT4 kit. Data on the latter are as follows:

Meter Range	Sec. Turns
14- 24	3
22- 40	7
36- 65	15
60-110	24

(Continued from previous page)
 A winding, S4, must be placed on the core of S3. This consists of 120 turns of No. 28 silk covered wire. Loosen the two top machine screws holding the core in place and slide the L shaped section out of the frame. Random-wind 60 turns of wire and then leave a 6 inch long loop. This loop will serve as the center tap connection of the oscillator pick-up winding. Then continue with the additional 60 turns, which will give the required number of turns.

—Short Wave Craft, Jan., 1933.

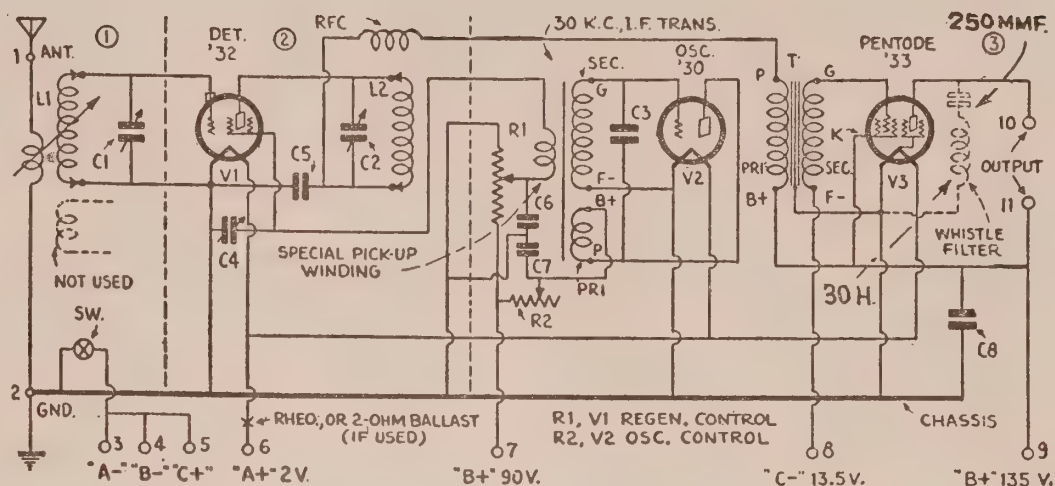

The first two coils are wound with No. 16 D.S.C. wire, 11 turns to the inch; the last two coils, No. 18 D.S.C., 17 turns to the inch; all on forms two inches in diameter. The adjustable antenna primary has 6 turns of No. 28 D.S.C. wire on a two-inch tube.

Some explanation is necessary, of the extremely novel, effective and compact oscillator inductance design which has been selected as the best.

An old Acme 30-kc. superheterodyne I.F. transformer (appropriately enough) had its outer protective metal covering removed; and over the outside of the exposed winding (the original primary-secondary combination) was wound a third or tertiary pick-up coil L of 150 turns of No. 28 enamelled wire, random wound. Condenser C3, .001-mf., tunes the oscillator circuit.

This happy artifice worked right off the bat, and oscillated to beat the band; functioning exactly right for the particular receiver shown in the diagram.

Operation of the Set

Insert in their respective receptacles the requisite two coils for a given tuning range

and turn the receiver's control switch to the "on" position. If the receiver is working, a thin high-pitched whistle will be heard in the background.

If this whistle is not evident, it is an indication that the oscillator is not functioning; and the first step is to reverse the leads to either the primary or secondary winding of the 30-kc. transformer (or the honeycomb coils, if used). This should correct the condition.


Vary the resistor R2; the volume of the whistle should change. Rotate the tuning control until a signal is heard; and, for 'phone reception, vary the voltage on the screen-grid of V1 until the circuit is just under the point of "plop-over". For C. W. signals, let it "plop." Simple?

Every short-wave receiver must be nursed along until the operator becomes conversant with its eccentricities.


When searching for 'phone signals tune by the chirps and then lower the screen voltage by means of the potentiometer R1.

—Short Wave Craft, Oct., 1931.

A Balanced Detector Super-Regenerator

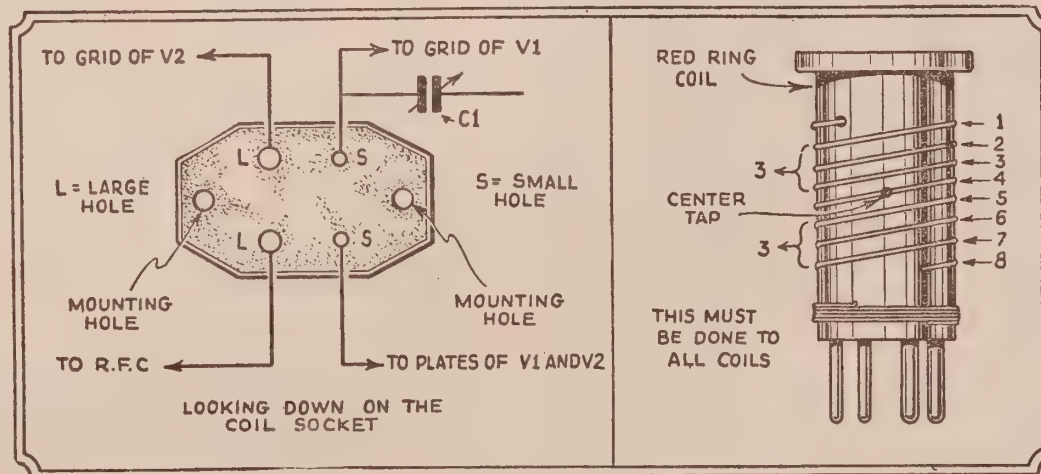

Armstrong "Super" 1-Tuber

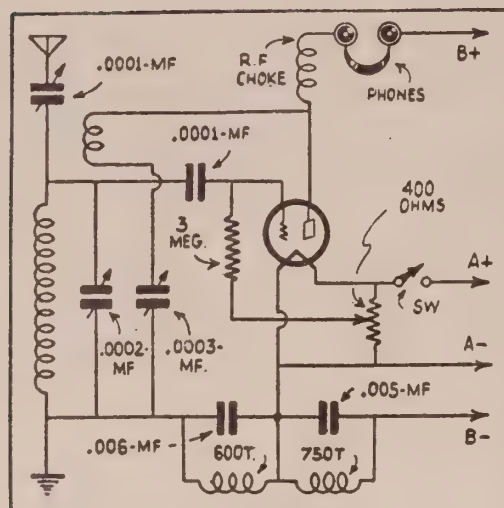

Construction Data

The quenching coils are wound on spools

made from scrap plywood. Three large plywood discs approximately 3 inches in diameter should be cut from this plywood to form the "flanges" of the spools, while two similar discs 1 in. in diameter are needed for the center core on which the wire is wound. When you have cut the wood, clamp the five pieces together with a brass screw.

Wind 600 turns of No. 36 D.S.C. wire in one slot and 750 turns of the same gauge wire in the second slot in the same direction. The accompanying circuit diagram shows how the two coils are connected together in the grid side of the circuit.

To tune these two coils to the required oscillation frequency there are fixed condensers shunted across each. These have a critical effect on the quenching frequency.

If you want to get a good quenching oscillation and do not mind the note being just within the limit of audibility, then use .006 mf. condensers across each coil. If you have .005 condensers shunted, then the quenching will not be quite as effective, but the note will be above the range of the average ear.

As the fine results you can get from a short-wave Armstrong super depend largely on critical regeneration control you will find that this short-waver requires careful handling, but the results will repay you. Make several trials of various H.T. ("B") voltages and move the arm of the potentiometer with a pencil or insulated screwdriver until you get smooth oscillation and find that the set is "supering" properly.

—Amateur Wireless, London.


The "Easy-Build" S-W

By Clifford E. Denton

Super Regenerator

Parts List

- Two Eby 4 prong sockets (10, 15).
- One set Na-ald (or Octocoils) for S. W. Bands, mount in socket 10.
- One Hammarlund Equalizing condenser, 100 mmf. (9).
- Eight Fahnestock clips, (1, 2, 3, 4, 5, 6, 7, 8).
- One Hammarlund MC-140-M condenser, 140 mmf. (11).
- One Hammarlund MC-35-S condenser, 35 mmf. (12).
- One Illini .000125 mf., mica condenser (13); (Polymet).
- One International Resistance 1 watt, 3 megohms, (14); (Lynch).
- One Aerovox .006 mf. mica condenser, 16; (Polymet).
- One Flechtheim By-pass condenser, 1 mf., 250 volts D.C. (21); (Polymet).
- One Flechtheim Tubular condenser .0015 mf., 1000 volts (20); (Polymet).
- One Silver Marshall Type 240 audio frequency transformer (19).
- One National tuning dial, midget type B.
- One Acratest S.P.D.T. toggle switch Cat. No. 4104 (17).
- One Acratest toggle switch Cat. No. 4010 (23).
- One Frost volume control, type 6158 Acratest, 100,000 ohms (22); (Clarostat).

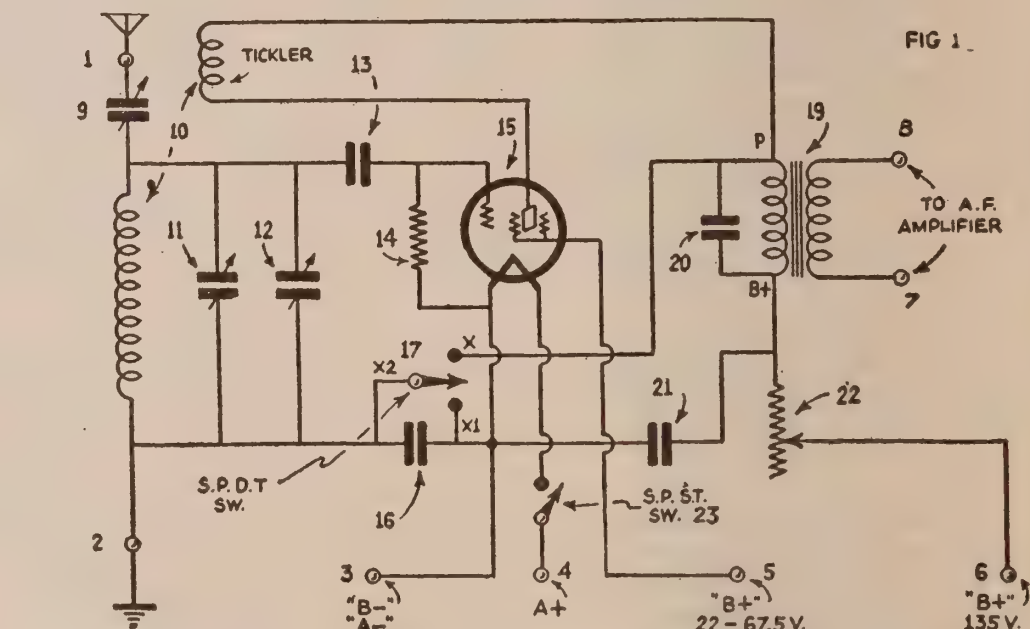

- One wooden baseboard 7x10 inches.
- One aluminum panel 7x10 inches, Blanche-Radio-Man.
- One Raytheon type 32 screen-grid tube, (R.C.A.).

This "dual role" short-wave receiver, which can be changed by the flip of a switch from "regenerative" to "super-regenerative", is particularly efficient for the reception of CW or code signals when operating on the super-regenerator principle,



particularly on the lower wavelengths, or those below twenty meters. Phone stations may be tuned in by means of super-regeneration and the change-over switch operated to change the circuit to the ordinary "regenerative" type. In other words, at the lower wavelengths and on code or CW signals, the super-regenerative circuit shows the most marked gain in efficiency. The cost of this set is very nominal and any wave band can be tuned in by using suitable plug-in coils.

—Short Wave Craft, May, 1933.

A 4-Tube "5 and 10" Meter Receiver With Optional Super-Regenerator

Parts List of Receiver

- 1—Pentode output transformer. Acratest.
- 1—Chassis.
- 6—4 prong coil forms; ultra-high frequency type; National.
- 2—4 prong isolantite sockets; National (Hammarlund).
- 2—6 prong isolantite sockets; National (Hammarlund).
- 1—6 prong wafer socket (laminated); Eby (Na-ald).
- 1—5 prong wafer socket (laminated); Eby (Na-ald).
- 2—35 mmf. variable tuning condensers; Hammarlund.
- 1—20 mmf. variable tuning condensers; Hammarlund.
- 1—Vernier dial; National, type B.
- 1—2.5 millihenry choke; National.
- 1—250 millihenry choke (universal wound).
- 1—50,000 ohm potentiometer; Acratest.
- 1—"Interruption Frequency" transformer, 700 turns pri. 1500 sec; Gross Radio.
- 3—.001 mf mica fixed condensers. Flechtheim.
- 2—.005 mf. mica fixed condensers.
- 2—.00005 mf. mica fixed condensers (connected in series).
- 1—.0001 mf. mica fixed condenser.
- 1—.5 mf. bypass condenser.
- 4—.01 mf. bypass condensers (tubular).
- 1—25 mf. 25 volt electrolytic condenser; Acratest.
- 1—300 ohm 1 watt resistor, Lynch (International). Also following resistors.
- 1—500 ohm 1 watt resistor.
- 1—2,000 ohm 1 watt resistor.
- 1—25,000 ohm 1 watt resistor.
- 1—100,000 ohm 1 watt resistor.
- 1—250,000 ohm 1 watt resistor.
- 1—.5 megohm 1 watt resistor.
- 1—2 megohm 1 watt resistor.

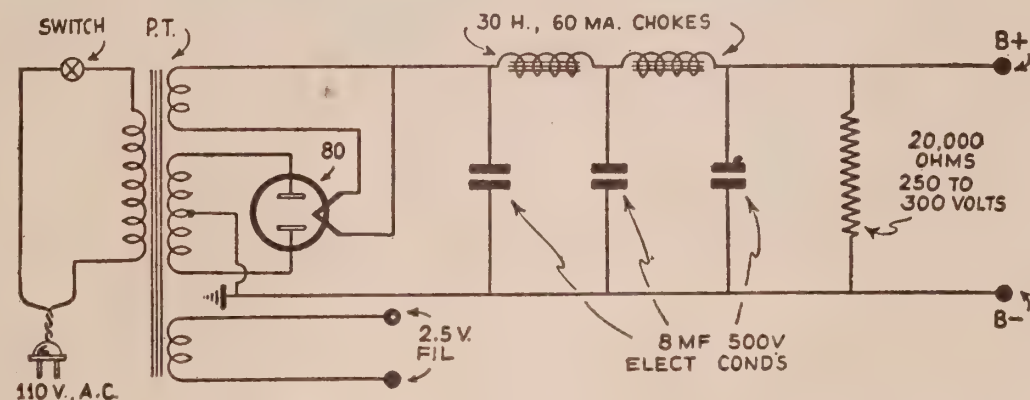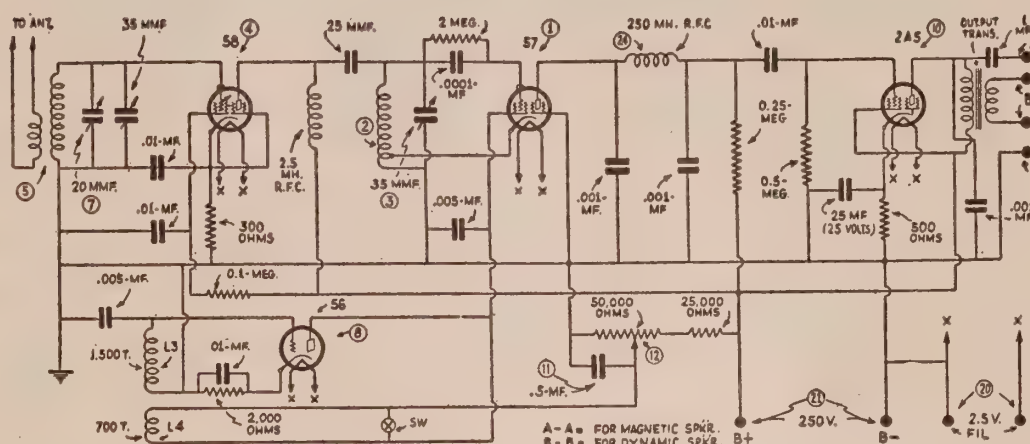

Parts for "Power Supply"


- 1—Power transformer 325-0-325 plate, 2.5 fil, 5 v. R.T. Co.
- 2—30 henry, 60 milliampere chokes; Acratest.
- 3—8 mf. 500 V. electrolytic filter condensers; Acratest.
- 1—20,000 ohm bleeder resistor (20 watts rating).
- 1—4-prong wafer socket, Eby (Na-ald).

An extra tube was added to the receiver to obtain super-regeneration, although this was not entirely necessary as very fine phone reception is obtained without it. The primary function of this addition is to enhance the reception of the very weak or broad modulated signals, such as those from new police broadcasting systems now operating on about eight and one half meters. These signals are so broad during modulation that it is impossible to receive them on a straight regeneration detector. However, when using super-regeneration the signal sounds first rate.

A type 56 is used as the generator of the interruption frequency oscillations, which produce the super-regenerative effect. The plate of the 56 is directly coupled to the screen-grid of the detector tube, the screen voltage to the detector tube and the plate voltage to the low-frequency oscillator being fed through L4 and controlled by the 50,000 ohm potentiometer.

The voltage to both tubes is adjusted at the same time, providing very smooth operation.

—Short Wave Craft, Nov., 1933.

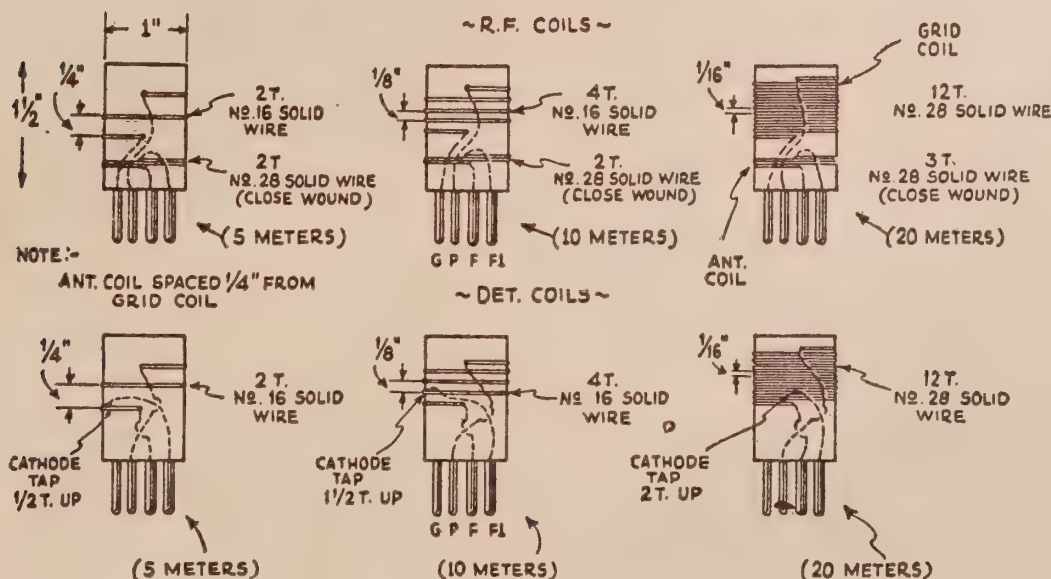

3 in 1 Monotube Super-Regenerator

Parts List for Both One Tube Super-Regenerators

One—Hammarlund Midget Condenser. Type MC250M. 250 mmf. (14).

One—Hammarlund Midget Condenser. Type MCD-140; 140 mmf. (5, 6).

One—Flechtheim By-pass Condenser. Type GB-100. 1 mf., 200 volts. (12).

Two—Flechtheim Tubular Condensers. Type AZ-10. .002 mf, 1000 volts. (9, 10).

Two—Sets Alden Mfg. Co. Short Wave Coils. 15 to 200 meters.

Eight—Fahnstock Clips, (1, 2, 15, 16, 17, 18, 19, 20).

Two—Eby Chassis type sockets (3, 4) Four prong for the plug-in coils.


One—Eby Socket, type depends on the choice of tube used for reception. (11).

Two—Blan Special choke windings. (7, 8).

One—International Resistor 10,000 ohms, 1 watt (13).

One—Hammarlund Equalizer Condenser. Type EC-80, 25 to 80 mmf. (21).
(Optional method of antenna coupling.)

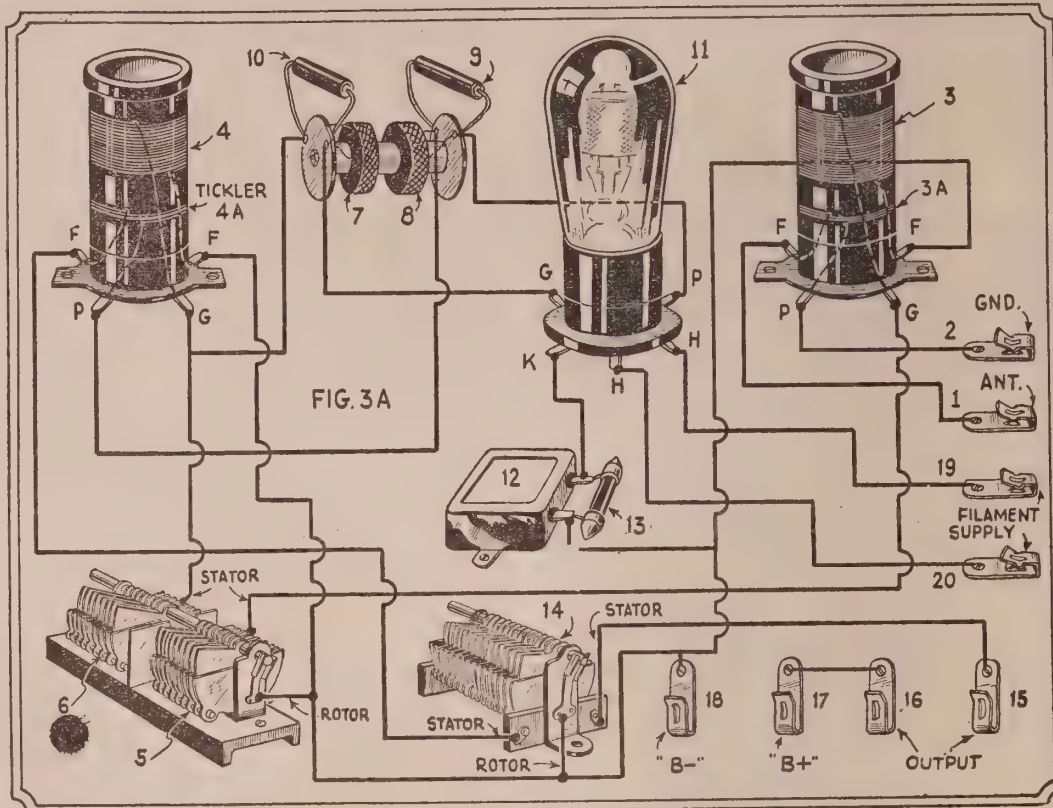One—Blan 6 inch by 10 inch aluminum panel.






One—Wooden base-board 8x10x $\frac{3}{4}$ inches.
All small brackets and incidental hardware can be purchased from Blan the Radio Man.

One Tube Super-Regenerator

Type of Tube	Plate Voltage	Grid Bias	Value of Resistor 13 in Ohms
01A	135V	-13.5V*	-----
210	350V	-35.0V*	-----
112A	180V	-20.0V*	-----
22**	135V	-13.5V*	-----
24**	250V	- 9V	5,000
27	250V	-30V	15,000
30	180V	-20V*	-----
32**	180V	- 6.75V*	-----
36**	180V	- 6V	5,000
37	180V	-20V	15,000
56	250V	-20V	15,000
57**	250V	-10V	5,000


*Bias furnished by "C" battery.

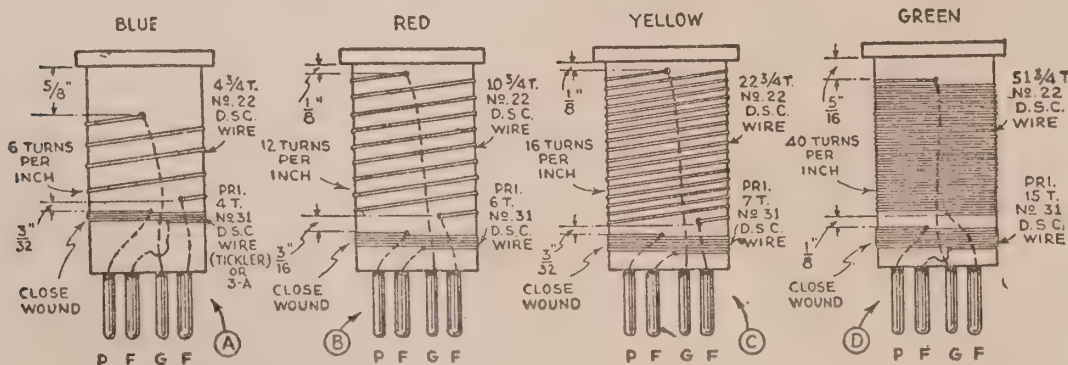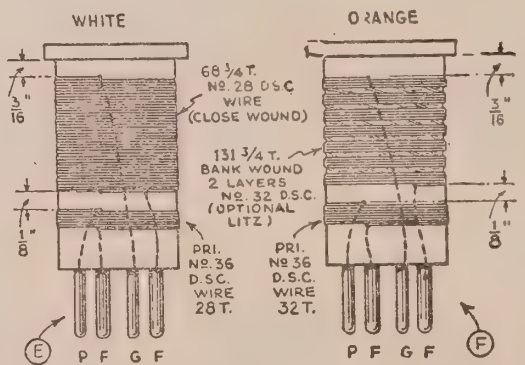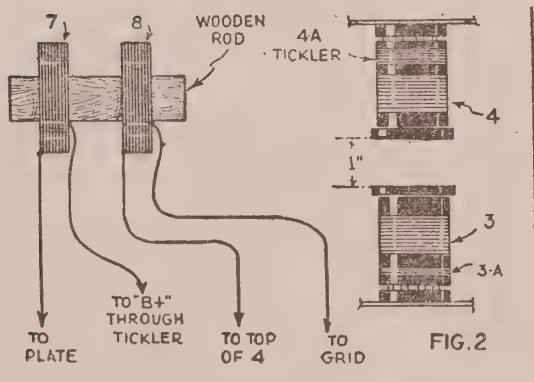**Requires very large coupling impedance.




NOTE: ALL COIL FORMS 1/4" DIAMETER BY 2 1/8" LONG (OVERALL) 1/8" SHOULDER.

—Short Wave Craft, Dec., 1932.

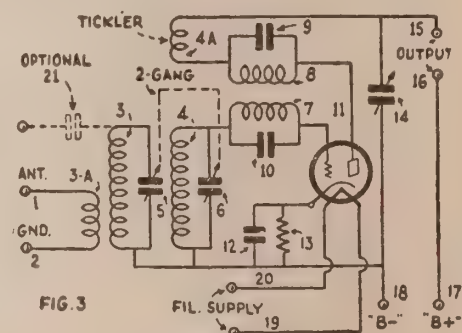

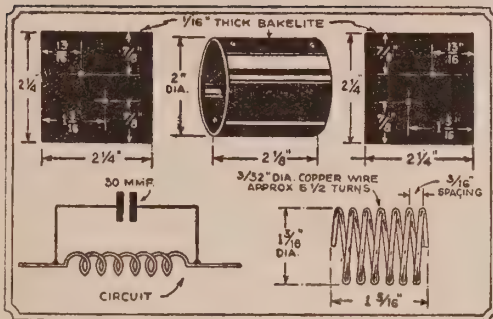A. C. Model.

The "Bear-Cat-3" 5-Meter Super-Regenerative Receiver



Above—Details of antenna resonance coil and condenser.

COIL DATA

The specifications for coils 4 and 5 are given below:

	No. of turns	Wire size	Spacing
Coil 4	7	14	1/16 inch
Coil 5	7	14	1/16 inch


Coil 17.—Coil 17 consists of 650 turns No. 36 double silk covered wire, wound on a small bobbin 1/2 inch in diameter and closely coupled to the coil 18.

Coil 18.—The grid coil is number 18 and consists of 1,000 turns of the same size wire used on 17. This is wound in the same direction on the same bobbin and due to its small size can be bolted into place under the chassis.

Radio Frequency Choke No. 9.—This is a small choke and care should be used in building it. As the frequency range to which the receiver responds is very high, it is necessary that the distributed capacity of the winding be kept at a minimum. A satisfactory choke can be made by "jumble-winding" 30 turns of No. 36 double silk covered wire on a bobbin 1/2 inch in diameter.

Parts List

- 1—Antenna Binding Post (1).
- 2—Hammarlund equalizing cond. 35 mmf. (2, 3).
- 1—Hammarlund midget condenser (6).
- 1—International Resistance Co., 1-watt, 2-meg. resistor (7).
- 1—Panel mount socket, 5-prong (8).
- 1—Radio frequency choke (9). See above for specifications.
- 1—Aerovox mica condenser, .001-mf. (10).
- 1—Medium ratio audio transformer (11).
- 1—Flechtheim by-pass condenser, .1-mf (12).
- 1—Electrad 50,000-ohm potentiometer (13) with filament switch (28).
- 1—Flechtheim by-pass condenser, .1-mf. (14).

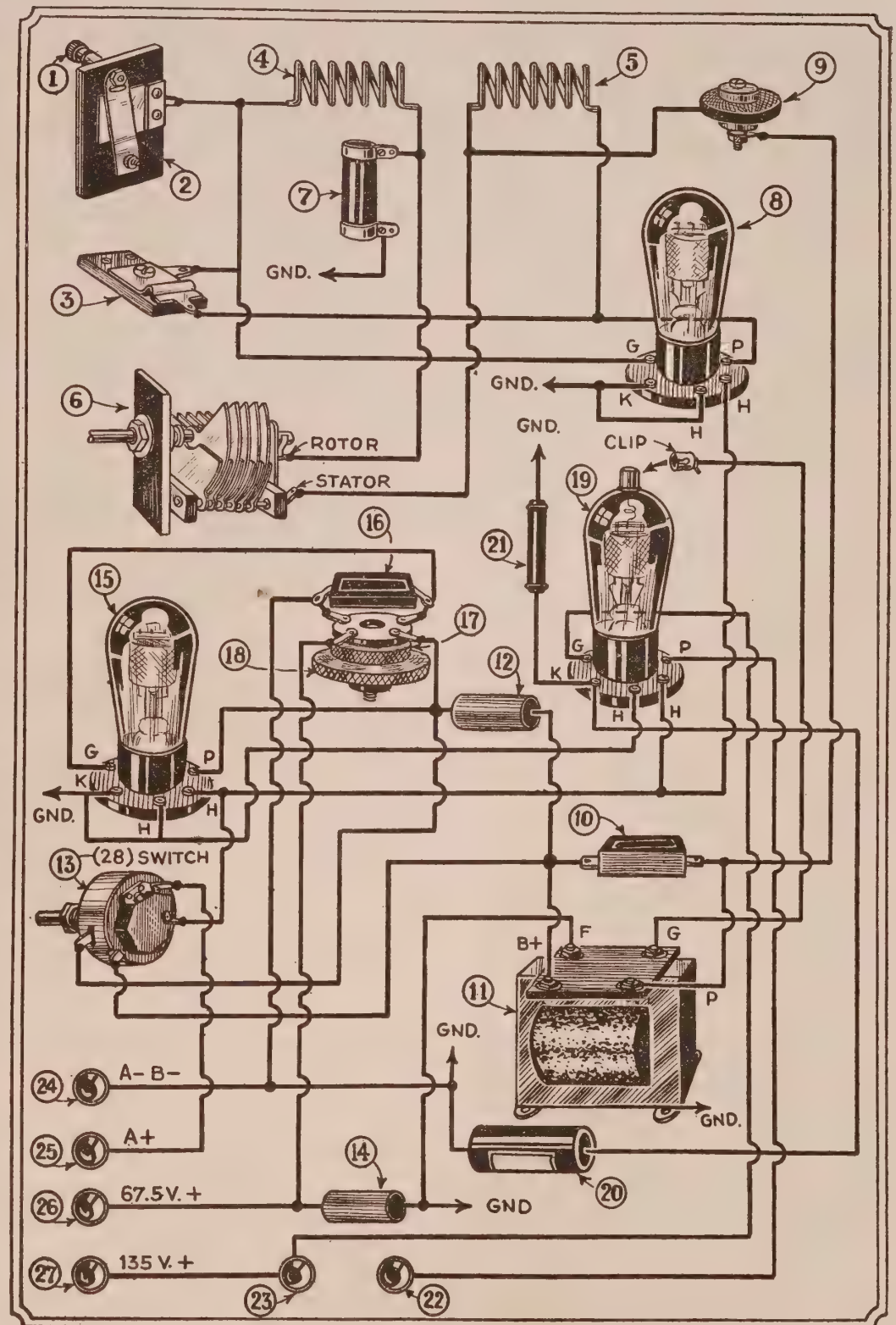

- 2—Wafer sockets, 5-prong (15, 19).
- 1—Mica condenser, .001-mf. (16).
- 1—By-pass condenser, .1-mf. or larger (20).
- 1—1,500-ohm resistor, 2 watts (21).
- 2—Output terminals (22, 23).
- 4—Binding posts (24, 25, 26, 27).
- 1—metal chassis and front panel.
- 1—Tuning dial.

- 1—Screen-grid clip. Wire, etc.

Note—Coils 4, 5, 17 and 18 winding data included in text above.

- 2—Eveready-Raytheon 37 tubes.
- 1—Eveready-Raytheon 38 tube.

Auto Tube Receiver

Parts List

One—Hammarlund Type ML 5 shortwave condenser (C1).
 One—Hammarlund Type ML 11 shortwave condenser (C2).
 One—Hammarlund Equalizer condenser, 32 mmf. (C3).
 Two—Sprague or Aerovox tubular bypass condensers, 0.1 mf. capacity (C4, C5).
 Two—Sprague or Aerovox tubular bypass condensers, 0.5 mf. capacity (C6, C9).
 One—Aerovox moulded mica condenser mid-gate type, .00015-mf. (C7).
 One—Aerovox moulded mica condenser, .02-mf. capacity (C8).
 Two—Lynch metallized resistors with pig-tails, 1 watt, 100,000 ohms (R1, R4).
 One—Lynch metallized resistor with pig-tails, 1 megohm, 1 watt (R5).
 One—Lynch metallized resistor with pig-tails, 6 megohm, 1 watt (R3).
 One—Lynch metallized resistor with pig-tails, 1500 ohms, 2 watt (R6).
 One—Electrad 500-ohm pigtail grid-suppressor resistor (R2).
 One—Electrad 0-50000 ohm bakelite shell Supertonatrol (R7).
 One—Bryant Electric switch, power type, single pole single throw two position (obtainable from Blane the Radio Man, N. Y. C.).
 One—Eby wafer socket, type 236 (V1).
 One—Eby wafer socket, type 237 (V2).
 One—Eby wafer socket, type 238 (V3).
 One—Pilot moulded bakelite socket, type 216 (V4).

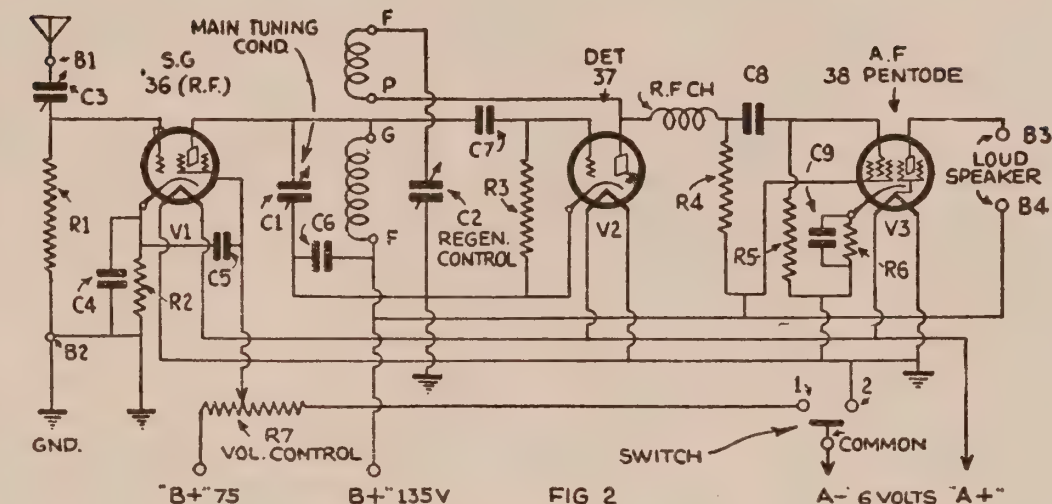


FIG 2

A-6V "A+"

One—Pilot 80-millihenry R.F. choke.
 Four—Pilot binding posts (B1, B2, B3, B4).
 Two—Sheets aluminum $4\frac{1}{4}$ inches long by $3\frac{3}{4}$ inches wide by $\frac{3}{64}$ inches.
 Two—Sheets aluminum $8\frac{1}{4}$ inches long by $5\frac{1}{4}$ inches wide by $\frac{3}{64}$ inches.
 Two—Sheets aluminum $5\frac{1}{4}$ inches long by 4 inches wide by $\frac{3}{64}$ inches thick.
 Four—Aluminum Corp. of America aluminum corner posts $5\frac{1}{4}$ inches long tapped for 6/32 screws.


Three—Hammarlund screen-grid tube shields (V1, V2, V3).
 One—Coil shield can 3 inches diameter by 4 inches high.
 One—Bakelite or hard-rubber panel $1\frac{1}{4}$ inches by 2 inches by $\frac{3}{16}$ inches.
 Two—National type C vernier dials (C1, C2).
 One 236—One 237—One 238 automobile tubes. (Arcturus used in tests.)

—Short Wave Craft, Dec., 1931.

The A.C. Superregenode

List of Parts Used

Two Hammarlund "MI-W-125" 125-mm short-wave condensers, C1-C2, and two Kurz-Kasch vernier dials.
 One Hammarlund 14-to-110 meter "Model LWT-4" short-wave coil kit, L1.
 One Hammarlund 14-110 meter model LWI-4 coil kit, L2.
 One Hammarlund "Type RFC 250" 250-mh. R.F. Choke, RFC1.
 One Hammarlund "Type EC 80" 80 mmf. equalizing condenser, C4.
 One Flechtheim filter block (five 1-mf. units), C6-C7-C8-C9-C12.
 One Ferranti "Type AF-5," 3.75-to-1 ratio audio transformer, T.
 One Sangamo .002-mf. double fixed condenser unit, C5-C13.
 One Aerovox .001-mf. fixed condenser, C3.
 One Sangamo .006-mf. fixed condenser, C10.
 One Aerovox 25-mf., 25-volt dry electrolytic condenser, C11;
 Two Electrad 50,000-ohm "Super-Tonotrols," R1-R2.
 Two Electrad 20-ohm V-type resistors, R6-R9.
 One Electrad 500 ohm wire-wound grid resistor, R3.
 Two Durham $\frac{1}{2}$ meg. 7-watt resistors, R4-R5.
 One Electrad 400-ohm wire-wound grid resistor, R7.
 One Electrad "R 71" 13,000-ohm voltage dividers, R8.
 One Carter battery switch.
 One Acme 30 kc. I. F. transformer or equivalent, L3.

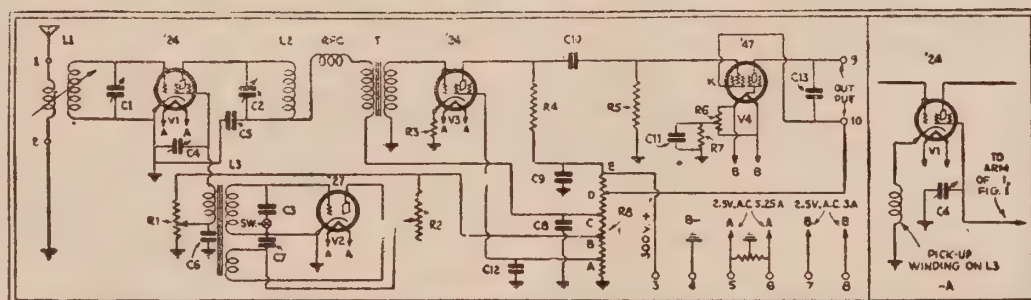

Four Pilot UY (5-prong) sockets, V1-V2-V3-V4.
 One Yaxley 7-wire cable, 3-4-5-6-7-8.
 Two Eby lettered binding posts, 1 and 2.
 One output connection block, 9-10.
 One aluminum cabinet 7x9x18x3/32" thick.
 Miscellaneous hardware (two National screen-grid clips; screws, nuts, lock-washers, wire, etc.).


Any standard '45-type power pack may be used, as long as it delivers about 65 ma. at 300 volts or more; in the latter instance, it may be necessary to connect in series with the "B+" lead of the eliminator a heavy-duty variable resistor, such as the compression-type Clarostat, with a range of zero to one megohm to reduce the voltage to the correct value to match the characteristics of the voltage divider in the receiver chassis.

The type '47 pentode operates best at a plate potential of 250 volts and a control-grid bias of 16.5 volts. In the A.C. Superregenode, this plate or "B" potential is obtained directly from the current-supply system; while from the total output of this system must be subtracted the required "C" bias (obtained by means of bias resistor R7 and, for V3, R3.)

The voltage divider in the receiver proper must be adjusted carefully to obtain maximum efficiency. The voltage readings at the taps should be about as follows: A, 18; B, 90; C, 180; D, 250; and E, 350 volts. A slight readjustment of A may be needed to obtain maximum A.F. amplification; this is the most critical operating value in the receiver.

—Short Wave Craft, Dec., 1931.

An English Super-Regenerator Four

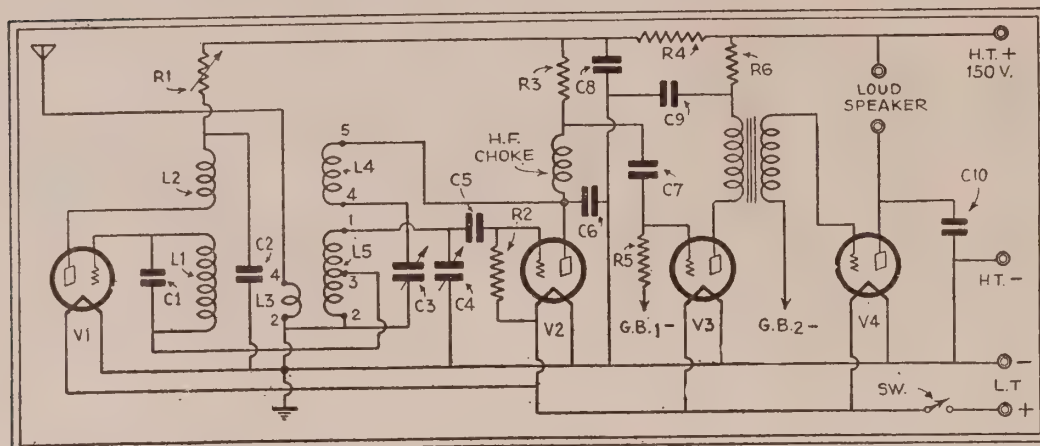


variable; R2, 5 megohms; R3, 30,000 ohms; R4, 20,000 ohms; R5, 2 megohms; R6, 10,000 ohms; V1, V2 and V3, average general purpose type tubes; V4, small power tube.

Oscillations generated by V1 are controlled by a variable resistance in series with the H. T., since this is a more economical method than utilizing a potentiometer arrangement, especially as the receiver was battery-operated. This resistance (R1) is variable between 0-2 megohms. It should be adjusted so that the tube just oscillates. Strong oscillations are not desirable, and if they are too weak adjustment of C3 to the point where the detector breaks into oscillation periodically suppresses the quenching oscillations and produces an effect akin to motor-boating. A fractional turn of R1 corrects this and gives a satisfactory working condition. The regeneration condenser is adjusted to give the best compromise between signal strength and back-ground noise.

With R1 adjusted so that the quenching tube is inoperative, the set can be used as a straightforward Det.-A.F. arrangement, in which condition C.W. signals are receivable in the normal manner. When a telephone station is heard, V1 can be brought in to action and the super-regenerative properties utilized to boost the signal for loud speaker reproduction.

Under Super-regenerative conditions more regeneration capacity is required at C3, which, of course, is in keeping with the theory, since the circuit L5, C4 will not reach the critical state for self-oscillation until its effective resistance is reduced to a lower level.

—Short Wave Craft, Oct., 1932

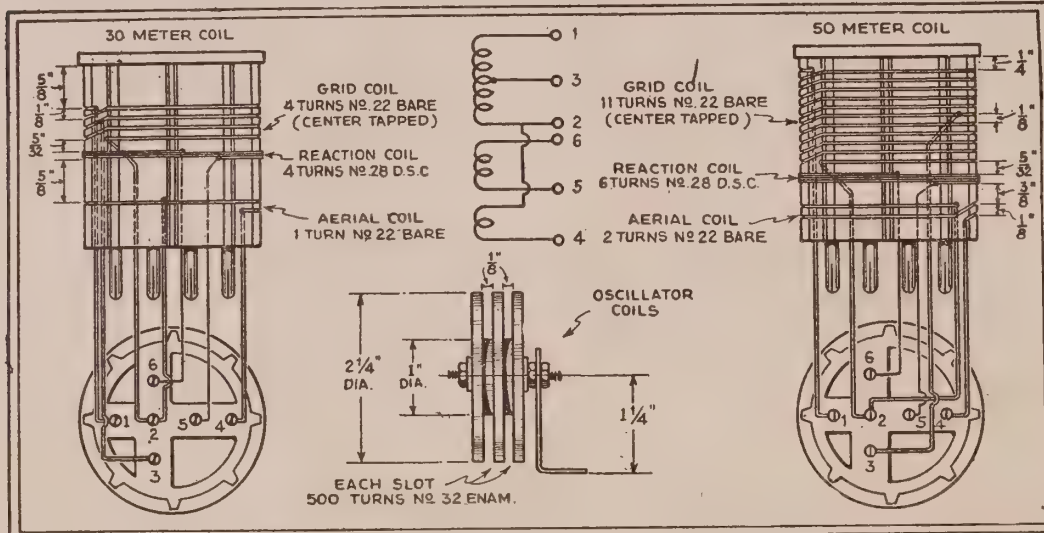

Coil Data for this novel super-regenerative set from overseas.


Values are as follows: C1, 0.05 mf.; C2, 0.00015 mf.; C5 and C6, 0.0001 mf.; C7, C8 and C9, 2 mf.; C3, 0.0003 mf.; C4, 0.01 mf.; C10, 0.001 mf.; R1, 0-2 megohm

The "International" Dx Q Set

A NOVEL RECEIVER

Here is a nice little set for the beginner who has tired of the battery type of receivers and would like to try his hand at constructing a self-powered or all-electric receiver. This set has a regenerative detector. Regeneration is controlled by varying the screen voltage and results in very smooth operation. This tube is resistance capacity coupled to a 38 pentode and a 37 or 76 is used as a half-wave rectifier. All the heaters are connected in series and a 325 ohm line voltage dropping power cord is used to reduce the 110 volts to that required by the 3 tubes.

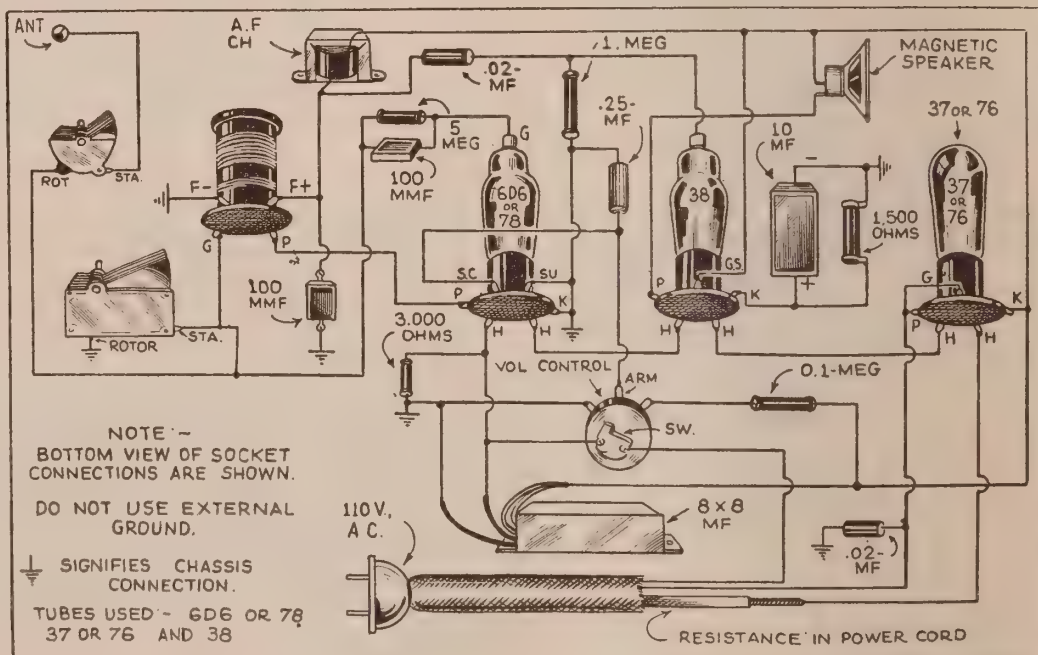Of course, with all receivers of this type the results depend a great deal upon the efficiency of the antenna system. The antenna should be at least 75 feet long; this has proven to be about the best value for the single wire type of antenna.



A Symmetrical Input Super Regenerator

V1, V2, V3—237 type tubes. R. C. A. (Arco).

V4—238 type tubes. R. C. A. (Arco).
R1, R2—50,000 ohms, resistor. All Lynch.
R3—500,000 ohms, resistor.
R4—1,000 ohms, resistor.
R5—2,500 ohms, resistor.
R6—50,000 ohms, resistor.
C1—100 mmf. Hammarlund Midget variable. (National).

C2—.002 mf. condenser.

C3—.5 mf. condenser. All Flechtheim.

C4—.5 mf. condenser.

C5—50 mf. condenser (electrolytic).

L1, L2, L3, L4 and L7 are wound on $\frac{3}{4}$ inch victron or other tubing with numbers of turns to suit the frequency desired. Care must be taken to make the input circuit symmetrical. With the number of turns on each coil as shown below the frequency range of the receiver was from 54 to 61 megacycles.

L1—3 turns.

L2—3 turns.

L3—7 turns.

L4—7 turns.

L7—4 turns.

By changing the turns of various coils, frequencies from 40 to 185 megacycles have been covered with this receiver.

L5 and L6—Made by separating the winding of a No. 125, 250 mh, Samson choke into two separate coils with a ratio of 1 to 3. The coil L5 has roughly three times the numbers of turns as coil L6. The variation frequency is approximately 100 kcs.

The approximate number of turns for L5 is 1,200 and for L6, 500; in most cases it is necessary to tune each of these coils

with a .001 or .002 mf. fixed condenser. More specifically the constructor may use a wooden form made from a piece of $1\frac{1}{4}$ inch diameter wood or bakelite rod. Two $\frac{1}{4}$ inch wide by $\frac{1}{2}$ inch deep grooves are cut in a piece of this rod, the grooves being $\frac{1}{2}$ inch apart. In one groove wind 1,200 turns of No. 36 S. S. C. wire "scramble" wound (helter skelter fashion, i. e., not in even layers). In the second groove 500 turns of No. 36 S. S. C. wire are wound.


The choke consists of 45 turns of No. 40 D. S. C. copper wire on a slotted form with three slots. The overall length of the form is about $\frac{3}{4}$ inch.

R. F. Filter Used in Battery Leads

There are four entering leads and in each of these a radio-frequency choke was inserted, consisting of 20 turns of No. 18 enameled wire, wound on a threaded victron (or other) form $\frac{1}{2}$ inch in diameter. The thread pitch was 16 to the inch. In addition the chokes were each by-passed to ground with .005 mf. condensers. All four chokes and all four condensers were placed in a separate shielded compartment and the battery leads were shielded back to the batteries.

This filter helps to eliminate battery lead pick-up and constitutes a considerable improvement.

—Short Wave Craft, June 1933.

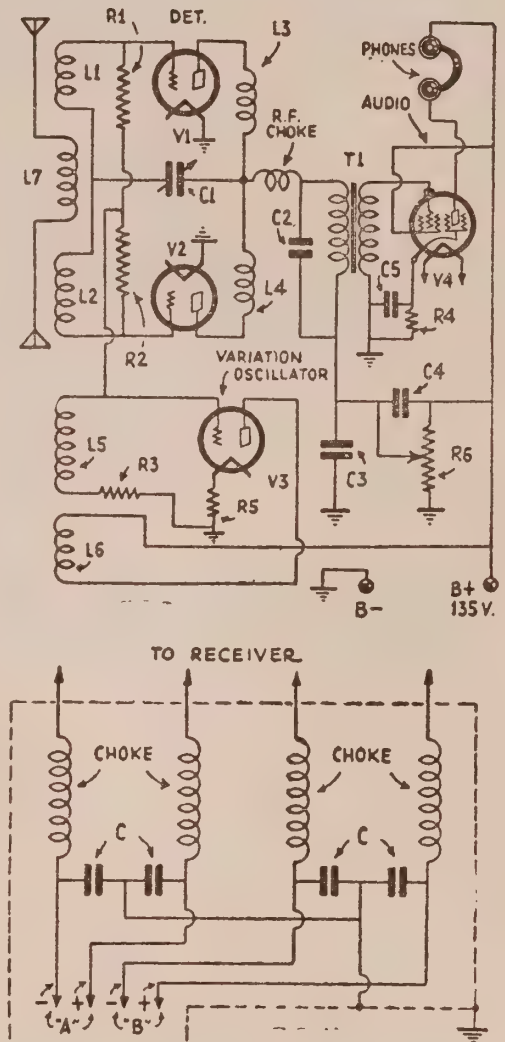

A 2-Volt 3-Tube "Ham" Set

Coil Table for Receiver


Grid	Primary-			
Met.	coil	Wire	tickler	Wire
L-2	L-3		coil	L-3
20	5	No. 30 DSC	4	No. 30 DSC
40	12	No. 28 DCC	11	No. 30 DSC
80	26	No. 30 DCC	21	No. 30 Enamel
				9/16"

Values

C1—.006 mf.
C2—.006 mf.
C3—.0001 mf.
C7—.005 mf.
C6—.00004 mf.
C8—1 mf.
R1—2 megohm.
R2—2 megohm.
R3—50,000 ohm Potentiometer.
T—Pilot Audio Transformer.
RFC—Pilot Short Wave Choke
C4—.0001 mf. Pilot Midget.
C5—.0001 Pilot midget, cut down to four plates.

For antenna coil L1 for use on the 80 meter band, wind a special coil containing 55 turns of wire.

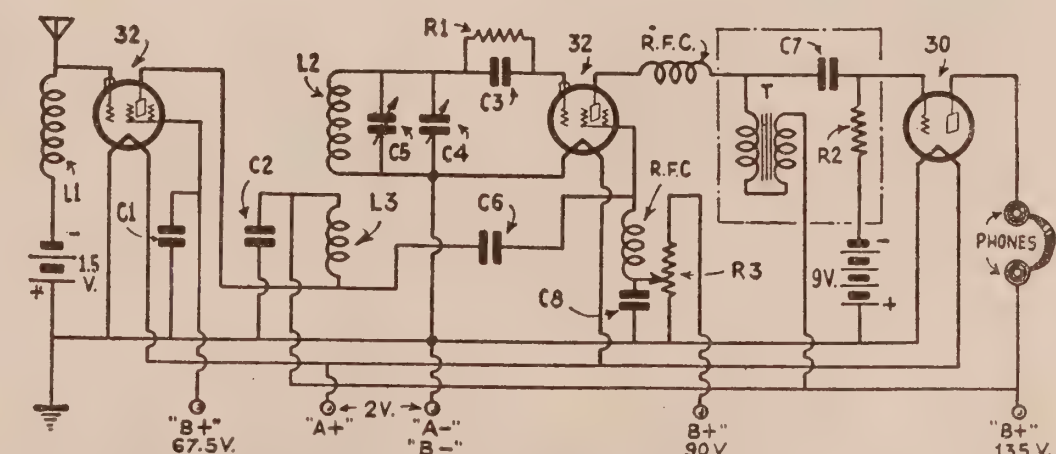All coils are close-wound except the twenty meter one, on which the spacing must




be found by experiment. The forty meter primary-tickler coil spacing should also be varied some in order to find the best value.

It should be noted that the coil L3 in this receiver is a combination tickler coil

for the detector and a primary coil which is connected in the plate circuit of the R.F. amplifier tube. This coil thus serves a double purpose.

—Short Wave Craft, May, 1933


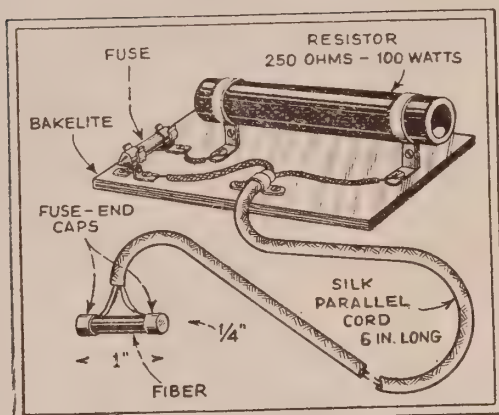
The Overseas 1-Tube 110-220 Volt A.C.-D.C. Receiver



Adapter for using the "portable" on 220 volts. When the fiber adapter is snapped into the fuse terminals, the 250 ohm resistor is in series with the circuit.

List of Parts

One Gen-Win, type WH litz-wound "all-wave" coil kit (for 140 mmf. tuning condenser), L1.
 One Sun type WH short-wave choke, RFC
 One Hammarlund type MC-140M, 140 mmf. midget condenser, (C1).
 One Hammarlund type MC-100 M, 100 mmf. midget condenser, C2.
 One Hammarlund type EC-80, 20 to 80 mmf. mica equalizer condenser, C3.
 One Aerovox type D1018 Hi-Farad 8 mf. dry-electrolytic condenser, C5.
 One Aerovox type E5-TD Hi-Farad 4 mf. dry-electrolytic condenser, C6.
 Two Aerovox type 381-T5, 0.1-mf. non-inductive paper condensers, C7, C8.
 One Ratco Polymet type NM-1271, 150 mmf. mica condenser, C4.
 One National, type BM-D vernier dial.
 One Clarostat type CLD volume-control resistor, R1.
 One Lynch type LF-4½, 6 meg., ½-watt resistor, R2.
 Two Electrad type B-1, 100 ohm, 25 watt resistors, R3, R4.
 One Electrad type C-2, 200 ohm, 50 watt resistor, (with three extra clips); R5-R6-R7.
 One Kenyon type KC-350, 30 hy. filter choke, Ch.
 One twin tip-jack, panel-insulated, J.
 One Eby binding post marked ANT., (with bakelite or hard rubber washers and bushing—not fiber or spaghetti), A.
 Two Blan type KK black knobs (one for ¼-in. shaft of C3 and one for 3/16-in. shaft of R1).
 Two RCA-Radiola dynamic reproducer dry-rectifier stacks, Radiola part No. 5898, (Sun Radio Co.), R.
 One Littelfuse ¾-A. fuse, F.
 Two Ratco fuse clips.
 One Ratco UY-type socket for V.
 One Ratco UX-type socket for L1.
 One pair Ratco type Erpees, No. 1693 featherweight headphones.
 One Ratco carrying case, 4¼x6½x11" long.
 One Ratco line-plug, P.
 One Ratco twin-conductor, No. 18 lamp-cord cable, 5 ft. long, (with male and female plugs).

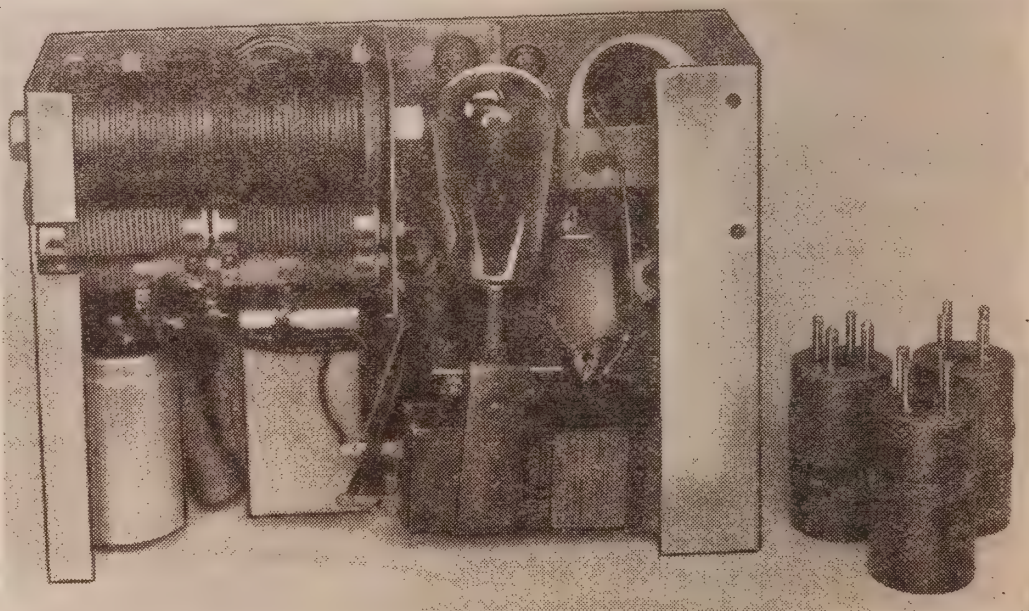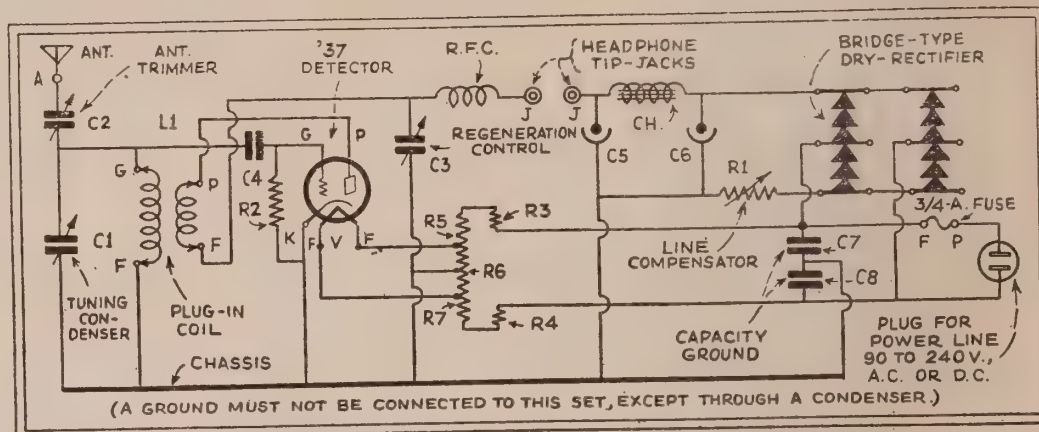

Side view of the universal A.C. or D.C. portable 1-tube receiver for short or broadcast wave reception, showing the "dry-disc" rectifier clearly at the left.

One Sylvania type '37 tube (with solid plate), V.
 One bakelite sub-panel (for fuse clips and plug P), 2½x2x1/16" thick.
 One Blan sheet-aluminum chassis, 16¾x6½x1/16" thick.
 One aluminum strip (for bracket of V), 3¼x1½x1/16" thick.
 One aluminum strip (for bracket of L), 5¼x¾x1/16" thick.
 One aluminum strip (for bracket of rectifiers), 2¾x4¾x1/16" thick.

It should be noted that the filament of the tube must be electrically grounded.

As we are not permitted to directly ground the filament (and only in rare instances, where the power line is not supplied with its own ground, through a condenser), since it connects directly to the light-line, we are forced to resort to a subterfuge—the capacitive ground; the center-tap of condensers C7, C8 affords this connection to the chassis. At the same time, these condensers act as filters to prevent light-socket key-clicks, refrigerator

and furnace thermostat noises, etc., being fed into the set, to make a "hash" of our signals.

Resistors R3, R4, R5, R7 must pass the current required by the combined value of the filament of V and resistor R6 in shunt. Without center-tapped resistor R6 (actually a portion of one resistor composed of R5, R6, R7), a very fine grade of "hum" will be heard (when the set is A.C. operated); with it, a graveyard is bedlam compared to the between-station silence when the contact clips are correctly set (as a matter of fact, only static or "strays" will indicate that the set is working, when the tuning dial is set off-tune.)

A good design of filter choke and 12 mf. of capacity in the plate-supply filter system furnish adequate filtration of the output of the full-wave rectifier, despite the fact that the efficiency of the dry-disc rectifier is relatively low. Putting R1 in the negative leg of the plate supply slightly increases the efficiency of the filter system.

—Short Wave Craft, Jan., 1934

"XP-53"
LOW-LOSS
COILS and
COIL FORMS

USERS

Say:

"HAMMARLUND

Short-Wave

EQUIPMENT

*Gives Greater Distance,
More Stations, Sharper
Tuning and Louder Signals
Than Any Other."*

THE reputation of Hammarlund Coils, Coil Forms, Condensers, Chokes, I.F. Transformers, Shields and Sockets—and the record-breaking COMET "PRO" Receiver is not accidental. It is the result of more than 33 years of engineering experience, embracing the entire history of radio.

Hammarlund Radio Equipment is internationally known and praised by amateurs, professionals, and the radio trade.

And it is modern.

Try



For Your
Needs

45 VESEY STREET

New York

**LARGEST SUPPLY OF TRANS-
MITTING PARTS IN NEW YORK**

**Complete Line of General Radio Parts
in Stock**

Racks, panels, bases, boxes, freqmeters, power supplies, analyzers, 5 meter gear, mixing panels, modulators, wave-meters and many special items. Our bulletin B-73 tells all; 5c brings it to you post haste.

A thin dime brings our bulletin B-73 and 25 manufacturers folders. There is a wealth of information of interest to builders in this collection of data. Send for yours today.

DEPT. H.U.

**Learn to Send and Read
RADIO CODE** At Home in
Half Usual Time
with **Instructograph**


Code Teacher

No experience or talent necessary. Instructograph provides the practice—and Book of Instruction explains each step, just like an instructor would do. You simply listen and imitate.

Available Day or Night



4-Tube S-W "Space Explorer"

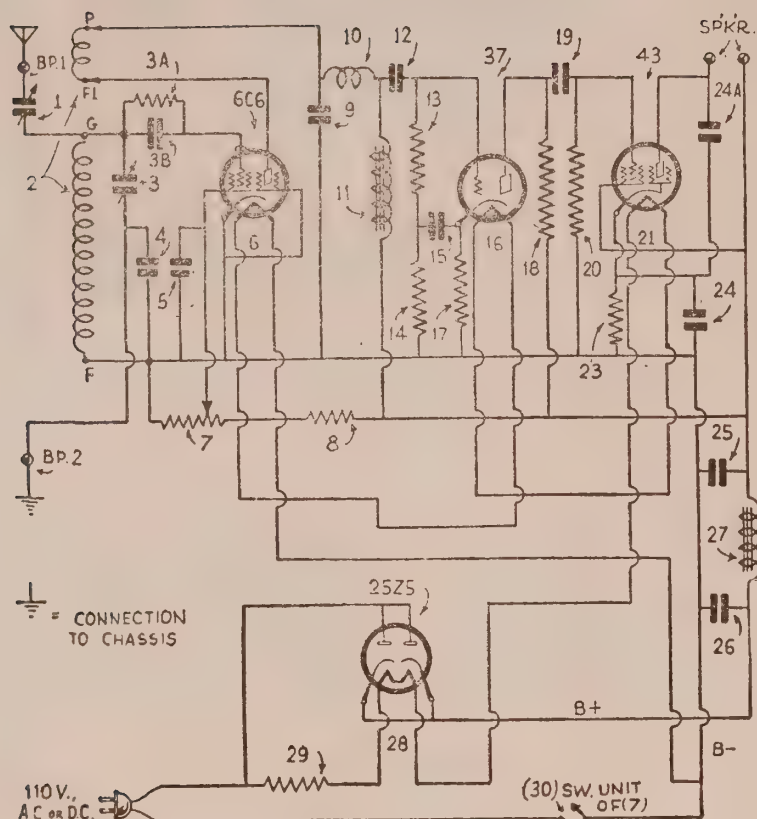

Schematic wiring diagram, which makes it a very easy matter to build up the short wave "Space Explorer" here described by Mr. Cisin.

Parts List

- 1—Hammarlund Variable Condenser, .00014 mf., type MC-140-M (3).
- 1—Hammarlund Ant. Trimmer Condenser, 3 to 35 mmf., type EC-35 (1).
- 1—Hammarlund Tube Shield, type TS-50 (6).
- 1—Set of four Na-Ald Short Wave Coils, type 704-SWS, 15 to 200 m. (2).

- 1—50,000 ohm Potentiometer (7) with Switch (30).
- 1—200 ohm, 75 watt Resistor, Slider Set at 190 ohms (29).
- 1—600 ohm Flexible Resistor (23).
- 1—1,500 ohm Flexible Resistor (17).
- 1—Mica Condenser, .0001 mf. (3B).
- 1—Mica Condenser, .00025 mf. (9).
- 1—Cartridge Condenser, 1 mf. (15).
- 1—Cartridge Condenser, 2 mf. (5).

- 1—Metal Case Container, .5 mf. (4).
- 1—Cardboard Tube Condenser, 10 mf., 25 volts, (24).
- 2—Double Section Cardboard Container Electrolytic Condensers, 8 mf. per section (25, 26). Each dual condenser should have sections connected in parallel to total 16 mf. each.
- 1—15,000 ohm, ½ watt Resistor (8), Lynch.
- 1—30,000 ohm, 1 watt Resistor (18), Lynch.
- 2—150,000 ohm, ½ watt Resistors (13, 14), Lynch.
- 1—500,000 ohm, ½ watt Resistor (20), Lynch.
- 1—1 meg., ½ watt Resistor (3A).
- 1—Na-Ald 5-prong Moulded Sockets (16).
- 1—Line Cord and Plug.
- 1—Na-Ald 4-prong Moulded Socket (2).
- 3—Na-Ald 6-Prong Moulded Sockets (6, 21, 28).
- 1—Vernier Dial; 1 Knob.
- 1—Twin Binding Post (BP1, BP2).
- 1—Find-All R.F. Choke (10).
- 1—Find-All Plate Impedance (11).
- 1—30 henry, 250 ohm Audio Choke (27).
- 1—6C6 Tube (6); 1—37 Tube (16). R.C. A. Radiotrons.
- 1—43 Tube (21); 1—25Z5 Tube (28). R.C. A. Radiotrons.
- 1—Trutest Magnetic Speaker (22).
- 1—Roll Hook-up Wire, Solid Core.
- 1—Noise Eliminating Lead-in System.
- 1—Metal Chassis, 10x8x2 inches high. Blan; Insuline.
- 1—.005 mfd. paper condenser (24A).
- 2—.01 mfd. paper condensers (12, 19).

The popular A.C.-D.C. circuit simplifies the construction by eliminating the power transformer. Furthermore, it makes the set more flexible, permitting operation in either changeably on alternating or direct current.

A 25Z5 rectifier is used. The filaments of all four tubes are connected in series with a wire-wound resistor, which serves the purpose of bringing the voltage down to the correct values required by the tubes.

—Short Wave Craft, Aug., 1934

1 Tube "Rab"

REAL RECEIVERS!!! LOW PRICES!!

THE HARRISON ORIGINAL 12,500 Mile Two Tube Sets



Here's the set that everyone is talking about! We have sold thousands since we first introduced this excellent receiver over two years ago. Every S.W. station in the world has been received with these sets!

The remarkable performance, neat appearance, and low cost make this the outstanding value today! No skimping! The finest parts throughout!

Heavy chassis—audio transformer—four coils 15 to 260 meters—vernier dial—modern, efficient design. The simplicity of construction and ease of operation make it the ideal Beginner's Set!

Battery Model uses two type 30 tubes and inexpensive long life dry batteries.


AC Model uses two 27 or 56 tubes.

Either Model **COMPLETE KIT—\$4.45**
Set of two Sylvania Tubes—\$1.10

AC-DC ALL-ELECTRIC MODEL

The world famous Harrison 12,500 mile set with a built-in hum free power pack supplying all necessary heater and plate voltages. Entirely self-contained! No batteries—Just plug into the 110 volt house line.

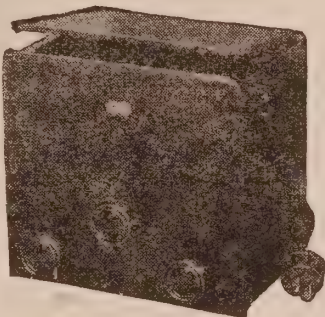Complete kit including drilled metal chassis, all parts, and clear picture diagrams. **\$5.95**



HARRISON For Value!

Complete Stock of Receiving and Transmitting Parts and Accessories
Lowest Prices

Prompt Service To All Parts of the World

More than eight years experience as the leading Short Wave Distributors and Manufacturers.

Your assurance of complete satisfaction with every transaction.

Many Other Sets In Stock

Send For Up-To-Date Literature

ANY KIT IN THIS AD ASSEMBLED, WIRED, and TESTED **\$1.25**

Deposit required with all orders.

The FULTONE "DUETTE" ALL-ELECTRIC TWO-IN-ONE 4"x4"x5 1/2"

2 1/2 pounds complete A powerful handful of radio that will surprise you with its volume and reception ability. European S.W. Broadcast stations are easily picked up with excellent headphone volume! Uses the new two-in-one type 12A7 Tube! High gain pentode detector and power rectifier. A



real, powerful two tube receiver! This set is certainly no toy!

Smooth acting friction drive vernier dial—Front panel adjustment for sensitivity — Built-in power supply providing all voltages needed (Set plugs into any 105 to 130 volt AC or DC house line)—Attractive, durable metal chassis and cabinet. Easy construction kit includes all necessary parts, drilled chassis and cabinet, 15 to 200 meter coils and simple instructions — **\$4.45**
Sylvania 12A7 \$0.95; 200 to 625 meter coils \$1.25

SPECIAL COMBINATION OFFER

Complete Kit, tube, and B.C. coils **\$6.25**

FULTONE "DUETTE" BATTERY MODEL

Uses the new type 19 tube—two separate tubes in one bulb! Detector and one stage audio amplifier. Works on two dry cells and one or two B batteries.

Complete easy construction kit as above **\$3.75**
Complete Kit, tube, and BC coils **\$5.50**

HARRISON RADIO CO.

142 LIBERTY ST., Dept. 101 NEW YORK CITY



SPECIAL OFFER!

SHORT WAVE CRAFT

Contains the "largest" and most "correct" short-wave station call list, and important constructional articles on receivers and transmitters, including "picturized" diagrams easily understood by anyone.

Send \$1.00 (\$1.25 Canada and foreign) and we will send you SHORT WAVE CRAFT for Eight months. **DO IT NOW.**

SHORT WAVE CRAFT

99-101 Hudson Street,

Dept. 101,

New York

— HEADQUARTERS —

FOR SHORT WAVE PARTS AND SUPPLIES
SINCE 1924


No Catalogue — BUT — Lowest Prices Always

BLAN THE RADIO MAN INC.

177 Greenwich St.,

New York, N. Y.

An A.C. S-W Converter

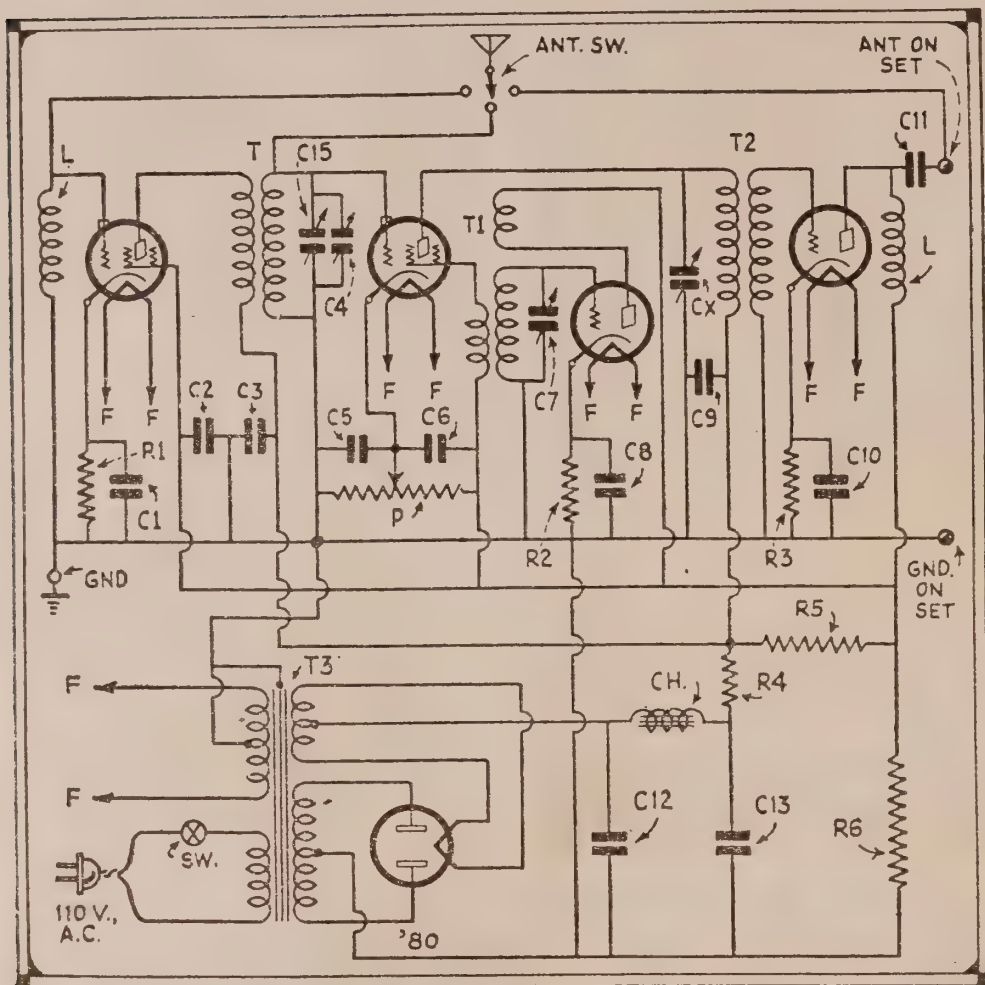

Coil Data

20 METER BAND

Modulator coil:

Primary 1 turn.

Secondary 4 turns.

Oscillator coil:

Primary or pick-up 1 turn

Secondary 5 turns.

Tickler 3 turns.

40 METER BAND

Modulator coil:

Primary 4 turns.

Secondary 8 turns.

Oscillator coil.

Pick-up 3 turns.

Secondary 9 turns.

Tickler 7 turns.

Coils for other bands may be wound at will. The size of the wire is not so important; anything between No. 20 and No. 26 will be satisfactory.

List of Parts for Converter

T—Set of modulator coils as described.

T1—Set of oscillator coils as described.

T2—1 to 1 ratio R. F. coil for midget condenser.

T3—Power transformer.

Ch—30 henry choke.

L—2-85 millihenry chokes.

C1, C2, C3, C5, C6, C8, C9, C10—Eight .1 mf. by-pass condensers.

C4, C7—Two .00015 mf. tandem tuning condensers.

C15—midget condenser across C4, approximately .00005 mf.

C11—.00025 mf. fixed condenser.

C12, C13—Two 4 mf. electrolytic filter condensers.

CX—Small tuning condenser, such as a trimmer.

R1—300 ohm bias resistor.

R2, R3—Two 1000 ohm bias resistors.

R4, R5—Voltage divider tapped at 3400 ohms. Total value 17,900 ohms.

R6—One 17,900 ohm bleeder resistor.

P—25,000 ohm potentiometer with A.C. switch.

6—UY sockets.

1—UX socket.

1—Dial (vernier type).

2—'24A tubes.

2—'27 tubes.

1—'80 tube.

4—binding posts.

Hardware.

1—25 foot roll "pushback" hook-up wire.

—Short Wave Craft, Dec., 1932.

A 2-Tube Portable All-Wave Receiver

Coil Data

Secondary


20 meters	7 T. No. 22 D. C. C.
20 "	9 " ditto
40 "	17 " ditto
80 "	21 " ditto
80 "	28 " ditto
Broadcast	90 T. No. 36 S. S. C.

Primary

6 turns	No. 32 D. C. C.
7 "	ditto
8 "	ditto
7 "	ditto
7 "	ditto
10 turns	No. 22 D. C. C.

When the author operates this set at his home station, a .0005 mf. condenser in parallel with a 25 turn 1½" coil is put in series with the antenna.

Any type triode tubes may be used in

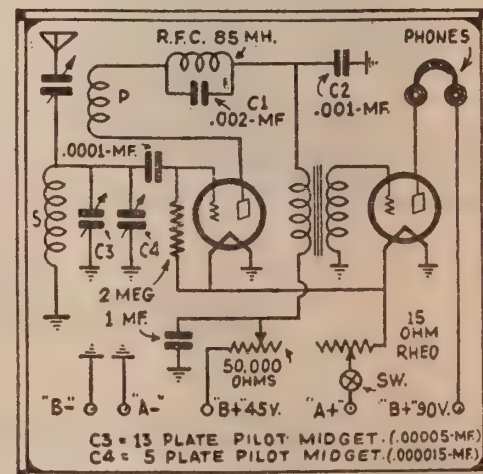


this set, but the author recommends 30's. The antenna is coupled to the set through a small trimmer condenser, fastened directly to the antenna binding post.

—Short Wave Craft, Feb., 1933.

If it's a **POWERTONE** Receiver You are assured the **BEST** Short Wave Reception


Universal AC-DC S.-W.

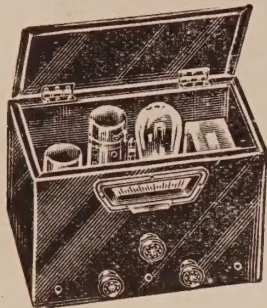Receiver
Complete
Kit**\$7.95**

Hum-free reception. Tubes: '78, '43 and 25Z5. Tunes from 15 to 550 meters.


Shielded Metal Cabinet \$1.00
Wired and Tested, extra 2.00
RCA Licensed Tubes 2.36
Bruno Broadcast Coil 59

REGENT 4 Tube A.C. S-W Receiver

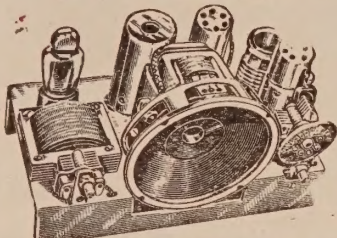

A complete receiver with built-in dynamic speaker. Will tune from 15 to 550 meters. Tubes: 2-'58's, 1-'80 and 1-2A5 power pentode output.

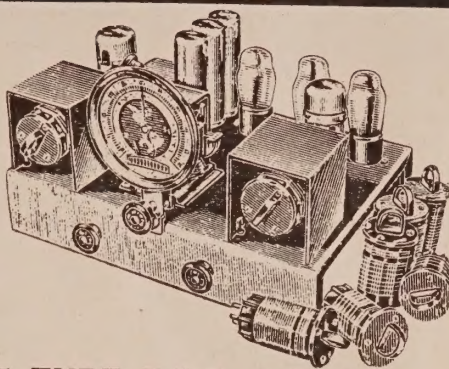Complete Kit, with speaker \$11.50
Wired, extra 2.00
Modernistic Cabinet 1.50
RCA Licensed tubes 2.36
Bruno Broadcast Coil 59



5 TUBE T.R.F. A.C. Operated Short-Wave Receiver

This most modern short-wave receiver is extremely efficient. It will receive foreign stations with great consistency.

The tubes used are of the latest design—a '58 R.F. stage for amplification, a '58 detector, two 2A5's for the push-pull stage and an '80 rectifier.

Kit of Parts with 8 Bruno coils \$17.95
Wired and tested, extra 2.00
Kit of RCA licensed tubes 2.95
Special Shielded Metal Cabinet 1.75

192 Page Radio Manual


Full of articles and construction stories on Short-Waves, Public Address, Testing Devices, etc. The most complete book of its kind at such a low price **50c**

Send for 184 page catalog.

TRY-MO RADIO CO., Inc.

85 Cortlandt St., N. Y. C.
179 Greenwich St., N. Y. City

Duo-Wonder S.-W. Receiver

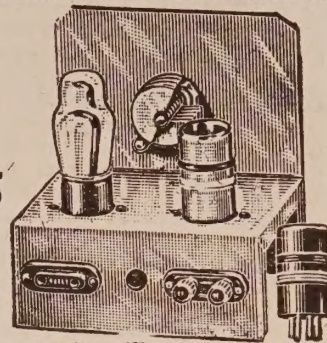Kit of
Parts
\$2.95

This simple circuit will give beginners a splendid course in radio construction and operation. Uses '19 tube.

RCA licensed tube \$.71
Wired, extra 1.00
Broadcast Coil 39

"SCOUT" Portable AC-DC Receiver

Covers the short - wave range from 15 to 550 meters. Powertone is the first to use the new '79 tube. Extremely light in weight.



Complete Kit of Parts \$5.95
Carrying Case 1.00
RCA Licensed Tubes 1.65
Wired, extra 2.00

THE ALL-WAVE LISTENER'S NEWEST NECESSITY! OFFICIAL SHORT WAVE LISTENER MAGAZINE



An entirely new magazine for the short wave listener, such as has not existed before. This magazine is totally different in get-up and contents from any other—nothing like it has ever been published before.

It has a four-color cover, and it is beautifully printed throughout. It contains a great variety of material, all of which is essential today to the short wave listener.

IT IS NOT A TECHNICAL MAGAZINE. It is designed for the short wave listener only. ASK YOUR DEALER FOR A COPY OF THIS MAGAZINE

25c the Copy. Well Illustrated.
CONTENTS OF A TYPICAL ISSUE!

Over 800 short-wave stations in various parts of the world await the touch of a finger on the tuning dial of your "short" or "all wave" receiver.

Photos and descriptions of short wave broadcasting stations in various parts of the world, with photos of short wave studio artists.

Where to find the important short-wave "DX" stations on the dial of your receiver.

Verification cards—what they are and how to get them.

Up-to-the-minute grand list of short-wave stations of the world with call letters and frequencies, including "Police," "Television" and short-wave stations.

Special list of the best or star short-wave stations, with their frequencies and call letters.

Valuable hints to the "short-wave listener"—how to locate the "weak" distance stations, etc.

Different time zones in various parts of the world, together with a map showing the location of short-wave stations of the world.

How To Use Earphones on Standard Receivers.

Short-Wave Fiction Story—"Short Waves by Heart"—by Hugo Gernsback.

WIXAL's S-W Educational Programs.

Fading and Skip Distance Explained.

How to identify short-wave stations by their "musical note" signatures.

Question and Answer department for the Short-Wave Listener.

Notes on "foreign" as well as "domestic" short-wave programs, meaning of foreign language phrases spoken in stations, etc.

How to erect special types of short-wave antennas, etc., SILVER CUP TROPHY for best photo of readers' listening "Posts."

If you cannot get the magazine at your newsstand due to sell-out, send 25c in cash, stamps, or money order, and we will send the magazine to you direct, prepaid.

OFFICIAL SHORT WAVE LISTENER MAGAZINE
99 HUDSON STREET DEPT. 101 NEW YORK

5 Meter Transmitter and Receiver

MARCUS L. POTTER

Parts List Transmitter-Receiver Receiver

- L1 5 turns No. 14 wire space wound $\frac{1}{2}$ inch diameter.
 L2 4 turns No. 14 wire space wound $\frac{1}{2}$ inch diameter.
 L3 Interruption frequency oscillator: primary or grid coil 1,400 turns: secondary or plate coil 900 turns honeycomb type of windings.
 VT1 type 30 tube, R.C.A. Radiotron (Arco).
 VT2 type 31 tube, R.C.A. Radiotron (Arco).
 VT3 type 49 tube, R.C.A. Radiotron (Arco).
 C1 .000035 mf. Hammarlund midget receiving variable condenser.
 C2 .0005 mf. fixed condenser.
 C3 .002 mf. fixed condenser.
 C4 .01 fixed condenser.
 C5 .002 mf. fixed condenser.
 C6 .00005 mf. Pilot midget variable condenser.
 R1 1 megohm 1 watt resistor Lynch.
 R2 30 ohm fixed resistor (Amperite).
 AT audio transformer.
 OT output transformer
 VC 50,000 ohm volume control with "on-off" switch.
 RFC 50 turns No. 30 D.S.C. wire close wound on $\frac{3}{8}$ " rubber rod.

Transmitter

- L5 Antenna coils, each 1 turn No. 14 wire 1" diameter, $\frac{1}{8}$ " spacing.
 L6 Plate tank coil, 5 turns No. 14 wire 1" diameter, $\frac{1}{8}$ " spacing CT.
 L7 Grid coil 11 turns No. 14 wire $\frac{1}{2}$ " diameter space wound CT.
 C7 Plate tank tuning condenser. Ham-



- marlund .000035 mf. each section.
 R3 15 ohm fixed resistor (Amperite).
 R4 100,000 ohm 1-watt grid leak Lynch.

Modulator and Speech Amplifier

- MT Acme single button microphone transformer.
 IT class B input transformer, for type

- 49 tubes.
 OT2 class B output transformer, for type 49 tubes and 5,000 ohm load.
 MA C-100 D.C. milliammeter.
 C7 1 mf. Aerovox fixed bypass condenser.
 C8 .002 mf. Sangamo fixed condenser.
 SW Off-on switch.

—April, 1934, Short Wave Craft.

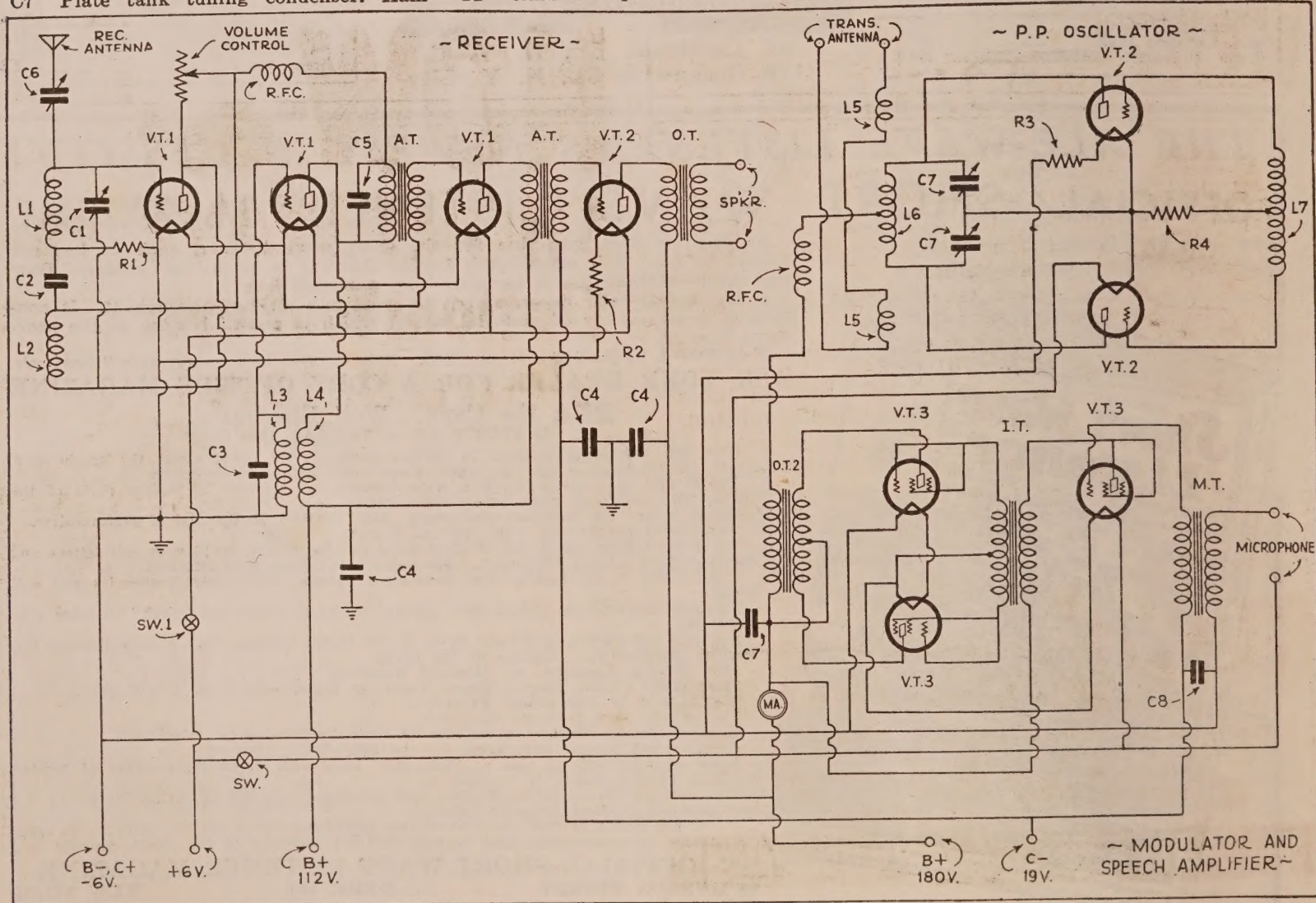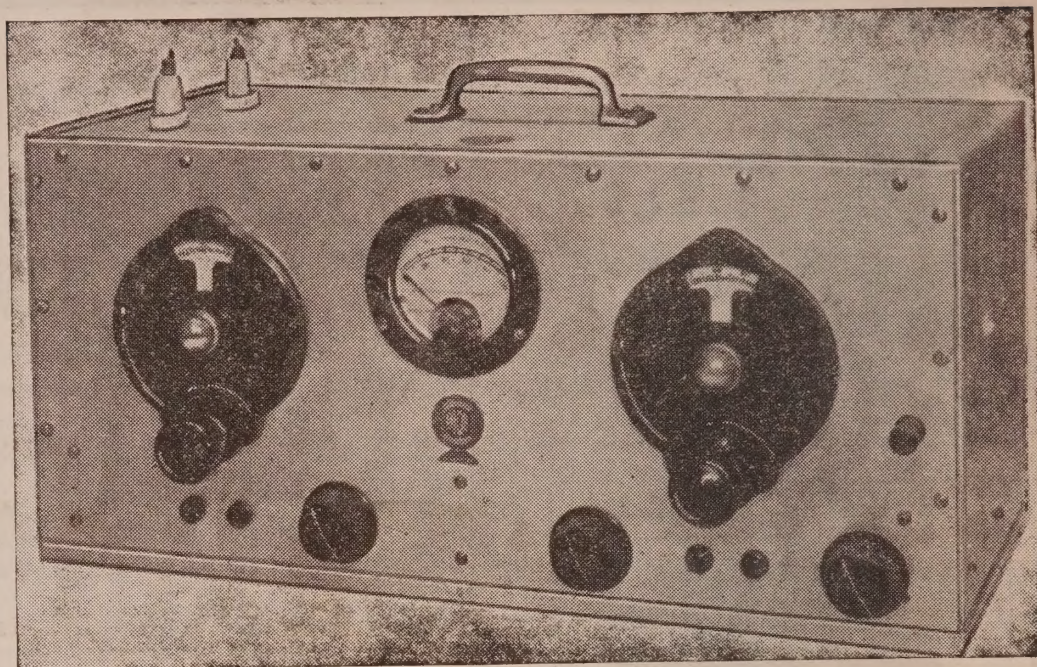

BOB HERZOG'S PRIZE WINNER

WON THE SHORT WAVE CRAFT PRIZE — JUNE ISSUE 1934

You Change
Your Wave
Band in
a Jiffy

The specially constructed chassis and black crackle panel with airplane dial and Gothic recesses make the

DeLUXE
RGH-4

Bob Herzog's latest Short Wave sensation a convenience as well as a joy.

Marvelous World-Wide Reception — Dynamic Speaker \$2.00 extra.

**NEVER
BEFORE**
Foreign Reception
Like This!

**ALL WAVE
RECEIVER**

Complete Kit of
Highest Quality
Parts, including
8 Short Wave
Coils.

\$11.95

**MARVELOUS SELECTIVITY
EASY TO WIRE**

Dynamic Speaker
\$2.50 extra

Complete Kit of
Highest Quality
Parts, including
8 Short Wave
Coils.

\$12.95


Kits Shipped
Ready Mounted
For Easy
Wiring

THOR RADIO
CORP.

167 GREENWICH ST., NEW YORK CITY

Mail Orders
Filled
Send For Free
Technical Data

Ahit 7-POINT MIKE

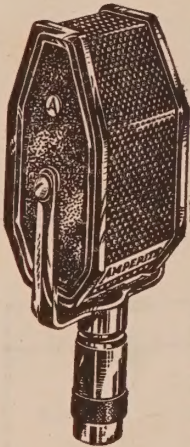

Here's why the Amperite Velocity Microphone gives you the best in quality and value . . . (1) Higher output. (2) No hum pickup. (3) Wider frequency range; no peaks, no distortion. (4) Directional quality makes it easy to eliminate acoustical feedback. (5) Wider area of coverage. One Amperite Vel. Mike will replace several diaphragm types. (6) Not affected by temperature, weather conditions or age. (7) Rugged construction. Fitted with swivel bracket. Fully guaranteed for one year against service costs.

PRE-AMPLIFIERS

Amperite Humless A.C. Pre-amplifier, Model APP, 40-10,000 cycles (1db). Hum level -100 db. (below audibility).

Write for Bulletin SW-1

NEW

AMPERITE for 2V Tube



A new series of Amperites. Automatically regulates filaments of tubes. Enables 2 volt set to operate on air cell, dry cell, storage battery, etc. Increases life and efficiency of the set.


Write for Bulletin SW-3.

AMPERITE Corporation 561 BROADWAY
NEW YORK

**NOW-Get NOW
SHORT WAVE \$1
Stations You Never
Heard Before!**

Amazing New
Sharp Tuner
Dial Gets
MORE Sta-
tions. Tunes
ALL Clearer!

**NEW
SPLIT-
HAIR
TUNER**

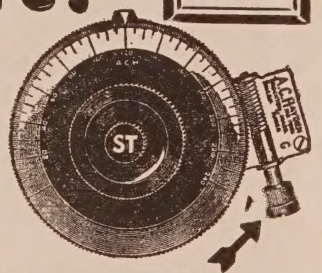

Try this remarkable new Micrometric Tuning Dial for 5 days AT OUR RISK! Slips on to short-wave receiver in jiffy. Makes tuning quick, easy, amazingly selective. Brings in stations you never dreamed possible! Makes every station clearer. Fits either 1/4 or 5/16 inch shaft. No wiring to do. Shielded from hand capacity. Handsomely made of bakelite, aluminum and nicked brass—will last a lifetime. Its mechanical smoothness and its calibration from 1 to 240 permits accurate logging. so essential to short-wave tuning. Regularly \$5.00. Now, for limited time, ONLY A DOLLAR!

SEND NO MONEY

**NO Backlash.
Ratio of 215 to 1
TRY IT 5 DAYS
AT OUR RISK!**


ELECTRICAL LABORATORIES CO., Dept. 294

141 East 25th Street, New York City

Send Short-Wave Sharp Tuner Dial, with instructions. Will pay postman \$1, plus few cents postage. If not delighted, will return in 5 days for \$1 refunded.

Name _____
[] Check here if ENCLOSING \$1, thus saving postage charges. Same refund Guarantee applies.

5 Meter Phone Pigmy Transmitter

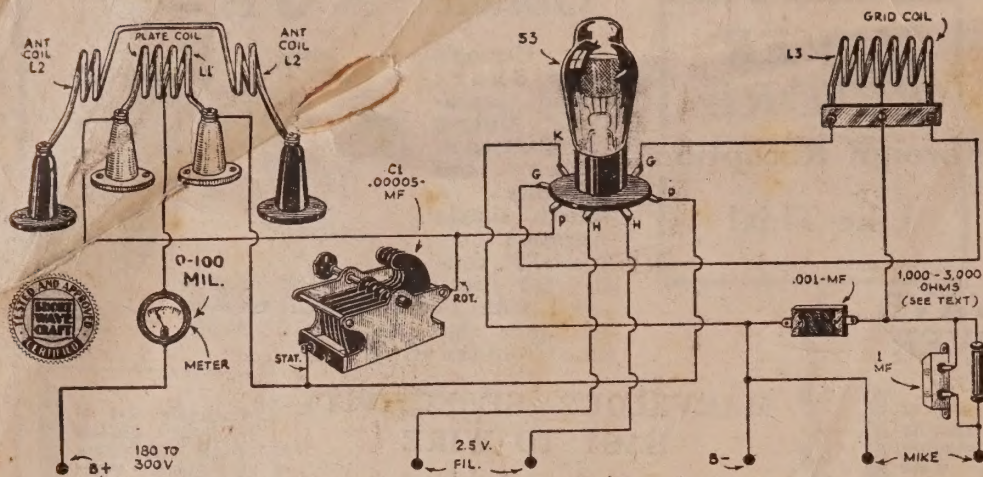

5 METER COILS

L1, PLATE COIL = 4 T. OF NO. 12 SOLID COPPER. ENAM. WIRE 1 IN. INSIDE DIAMETER.

L2, ANT. COIL = 2 T. EACH SIDE, NO. 12 SOLID COPPER. ENAM. WIRE 1 IN. INSIDE DIAMETER.

L3, GRID COIL = 6 T. OF NO. 12 SOLID COPPER. ENAM. WIRE 1 IN. INSIDE DIAMETER.

10 METER COILS

L1, PLATE COIL = 4 T. OF 1/4" WIDE COPPER STRIP 1 3/4 IN. INSIDE DIAMETER.

L2, ANT. COIL = 2 T. EACH SIDE, NO. 12 SOLID COPPER. ENAM. WIRE 1 IN. INSIDE DIAMETER.

L3, GRID COIL = 8 T. OF NO. 12 SOLID COPPER. ENAM. WIRE 1 1/4" INSIDE DIAMETER.

NOTE
GRID AND PLATE COILS MUST BE SPACED TO GIVE PROPER TUNING RANGE.

List of Parts

- 1—Variable condenser 50 or 100 mmf. Cardwell "Featherweight."
- 4—Standoff insulators, Johnson (Fleron; National).
- 1—'53 tube (Sylvania, R.C.A.).
- 1—Grid resistor (see text).
- 1—By-pass condenser, .5 mf. used only when grid resistor is used. Flechtheim.
- 1—Bypass condenser, .001 mf. For microphone; Flechtheim.
- 6—Binding posts

- 1—Base-board (wood) 6x10 inches.
- 1—Microphone and stand. Universal.

Adjusting for Maximum Output

Maximum output is obtained when the plate circuit is detuned considerably toward the high frequency side of this peak. This reduces the plate current to above 70 milliamperes, but this is still too high for continuous operation and will result in ruination of the tube. Therefore, we must provide more resistance in the grid circuit than the 200 ohms provided by

the microphone. This is done by putting a resistor of about 1000 ohms in series with the "Mike," this resistance depends upon the plate voltage. With lower voltages (around 200) no resistor will be required, however it should be large enough to limit the plate current to 60 milliamperes. This value will be still further reduced when the antenna is coupled to the transmitter; a drop of around 10 or 12 milliamperes indicates a reasonable amount of coupling.

—Short Wave Craft, Dec., 1933.

A Medium Power Transmitter

Coil Table for Transmitter

Grid coils "close wound" on 1 inch dia. bakelite tube.

- 20 meters 7 turns No. 28 D.S.C. each coil.
 - 40 meters 18 turns No. 28 D.S.C. each coil.
 - 80 meters 35 turns No. 28 D.S.C. each coil.
- Plate coils.
- 20 meters 4 turns.
 - 40 meters 6 turns.
 - 80 meters 12 turns.

Antenna coils have 4 turns each of 3/16 copper tubing wound with an inside diameter of 2 1/4 inches.

Plate coils made of 1/4 inch copper tubing inside diameter of coil is 2 1/2 inches.

Parts for Transmitter

- L—set of coils (see coil table).
- 1—.00044 to .0005 mf. transmitting condenser. National (Hammarlund; Cardwell).
- 2—.0001 mf. fixed (mica) transmitting condensers (2,000 vt.).
- 2—.001 mf. fixed (mica) transmitting condensers (2,000 vt.).
- 1—100 ohm C.T. resistor. R. T. Co.
- 1—10,000 ohm 20 watt grid-leak.
- 2—4 prong isolantite sockets. National (Hammarlund).
- 2—type 830 tubes. Sylvania.

—Short Wave Craft, Feb., 1934.

